



PROJECT REPORT

TEAM 35

Name	ID
Ammar Ahmed Wahidi	2200360
Ali Hany Zainhom	2201335
Hamza Basem Mohamed Ahmed	2200496
Omar Mohamed Hassan	2200294
Ammar Mohamed Abdelghany	2200707
Amr Ahmed Wahidi	2200429
Omar Ahmed Abd El-Kader	2200706
Youssef Emad Eldeen	2200536
Mohamed Elsayed Moustafa Hamouda	2200095
Anas Ayman Mohammed	2200325

SUBMITTED TO: PROF. SAMEH A. IBRAHIM
DATE OF SUBMISSION: 23TH MAY. 2025

ARITHMETIC AND LOGICAL UNIT DESIGN

Verilog code.....	3
Code.....	3
schematics	4
ALU Testbench Verilog Code.....	5
Arithmetic unit	7
Logical unit	9
Transistor-level/Block-diagram schematics	11
Inverter gate	11
AND gate	12
OR gate NOR gate	13
NAND gate	15
XOR gate	16
XNOR gate	17
Logical unit	18
TG.....	20
Filb-Flop	22
MUX 2x1.....	24
MUX 8x1.....	26
AOI	28
Full Adder (1 bit)	29
Full Adder Mirror (1 bit)	30
FA Mirror vs FA Basic logic	32
Carry Look Ahead 4 bit.....	34
Why CLA Not suitable in the design.....	35
Full Adder (4 bit)	36
Why use Full Adder with mux instead of Subtractor.....	37

Half Adder.....	38
Comparison between Multiplier Architecture	39
Multiplier (unsigned).....	41
Multiplier (Signed)	42
Arithmetic unit	43
ALU.....	44
.....	44
Register (4bit).....	45
Register (8 bit)	46
Capacitor.....	47
Circuit.....	47
Simulation: Operations Waveforms	48
Arithmetic unit	48
Logical unit	51
Simulation: Transient simulations with the flip-flops at max f(340 MHz)	54
Arithmetic unit	54
Logical unit	58
Regeneration stage	62
Calculations.....	65

Bonus Contributed

FBGA

Fastest design (max frequency)

Verilog code

Code

```

module ALU (
    input signed [3:0] a,b,sel,
    input clk,
    output signed [7:0] y
);

    reg signed [3:0] regA;
    reg signed [3:0] regB;
    reg signed [7:0] regY;
    reg signed [7:0] nextY;


    always @(posedge clk)
    begin
        regY<=nextY;
    end
    always @(negedge clk)
    begin
        regA<=a;
        regB<=b;
    end

    //MUX
    always @(*) begin
        case (sel[3])
            0: begin
                case (sel[2:0])
                    3'b000: nextY = regA + 1; // Increment A
                    3'b001: nextY = regB + 1; // Increment B
                    3'b010: nextY = regA; // Transfer A
                    3'b011: nextY = regB; // Transfer B
                    3'b100: nextY = regA - 1; // Decrement A
                    3'b101: nextY = regA * regB; // Multiply A and B
                    3'b110: nextY = regA + regB; // Add A and B
                    3'b111: nextY = regA - regB;
                    default: nextY = 8'b00000000;
                endcase
            end
            1: begin
                case (sel[2:0])
                    3'b000: nextY = ~regA; // Complement a (1's complement)
                    3'b001: nextY = ~regB; // Complement b (1's complement)
                    3'b010: nextY = regA & regB; // AND
                    3'b011: nextY = regA | regB; // OR
                    3'b100: nextY = regA ^ regB; // XOR
                    3'b101: nextY = ~(regA ^ regB); // XNOR
                    3'b110: nextY = ~(regA & regB); // NAND
                    3'b111: nextY = ~(regA | regB); // NOR
                    default: nextY = 8'b00000000;
                endcase
            end
            default: nextY = 8'b00000000;
        endcase
    end
    assign y=regY;
endmodule

```

ARITHMETIC AND LOGICAL UNIT DESIGN

schematics

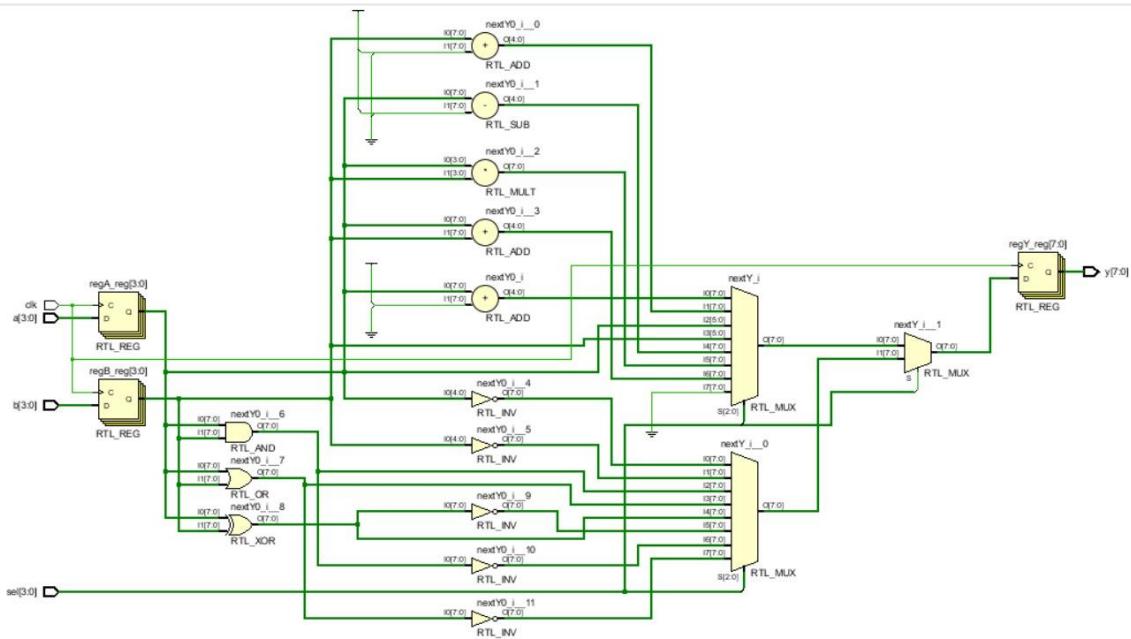

Schematic of Verilog

ALU Testbench Verilog Code

```

`timescale 1ns / 1ps

module ALU_tb;

reg signed [3:0] a, b;
reg [3:0] sel;
reg clk;
wire signed [7:0] y;

// Instantiate ALU
ALU uut (
    .a(a),
    .b(b),
    .sel(sel),
    .clk(clk),
    .y(y)
);

// Generate clock: 10ns period
always #5 clk = ~clk;

initial begin
    // Initialize
    clk = 0;
    a = 0;
    b = 0;
    sel = 4'b0000;
    #10;

    // Test Arithmetic Operations (sel[3] = 0)
    // Test Increment A: A = 3 -> Y = 4
    a = 4'd3; b = 4'd0;
    sel = 4'b0000;
    #20; // Wait 2 clock cycles

    // Test Increment B: B = 5 -> Y = 6
    a = 4'd0; b = 4'd5;
    sel = 4'b0001;
    #20;

    // Test Transfer A: A = -2 -> Y = -2
    a = -4'sd2; b = 4'd0;
    sel = 4'b0010;
    #20;

    // Test Transfer B: B = -4 -> Y = -4
    a = 4'd0; b = -4'sd4;
    sel = 4'b0011;
    #20;

    // Test Decrement A: A = 7 -> Y = 6
    a = 4'd7; b = 4'd0;
    sel = 4'b0100;
    #20;

```

ARITHMETIC AND LOGICAL UNIT DESIGN

```
// Test Multiply A * B: A = 3, B = -2 -> Y = -6
a = 4'd3; b = -4'sd2;
sel = 4'b0101;
#20;

// Test Add A + B: A = 3, B = 2 -> Y = 5
a = 4'd3; b = 4'd2;
sel = 4'b0110;
#20;

sel=4'b0111;
#20;

// Test Logical Operations (sel[3] = 1)
// Test Complement A: A = 5 -> Y = -6 (1's complement)
a = 4'd5; b = 4'd0;
sel = 4'b1000;
#20;

// Test Complement B: B = 3 -> Y = -4 (1's complement)
a = 4'd0; b = 4'd3;
sel = 4'b1001;
#20;

// Test AND: A = 5, B = 3 -> Y = 1
a = 4'd5; b = 4'd3;
sel = 4'b1010;
#20;

// Test OR: A = 5, B = 3 -> Y = 7
a = 4'd5; b = 4'd3;
sel = 4'b1011;
#20;

// Test XOR: A = 5, B = 3 -> Y = 6
a = 4'd5; b = 4'd3;
sel = 4'b1100;
#20;

// Test XNOR: A = 5, B = 3 -> Y = -7 (1's complement of XOR)
a = 4'd5; b = 4'd3;
sel = 4'b1101;
#20;

// Test NAND: A = 5, B = 3 -> Y = -2 (1's complement of AND)
a = 4'd5; b = 4'd3;
sel = 4'b1110;
#20;

// Test NOR: A = 5, B = 3 -> Y = -8 (1's complement of OR)
a = 4'd5; b = 4'd3;
sel = 4'b1111;
#20;


// Stop simulation
#10 $finish;
end

endmodule
```


ARITHMETIC AND LOGICAL UNIT DESIGN

Arithmetic unit


Increment a

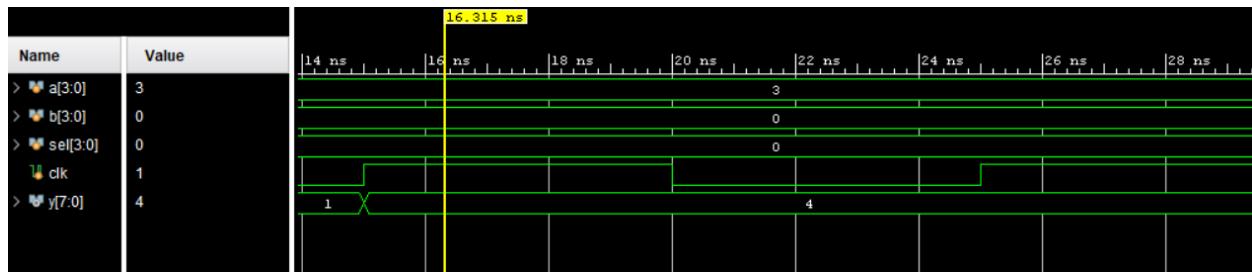

Increment b

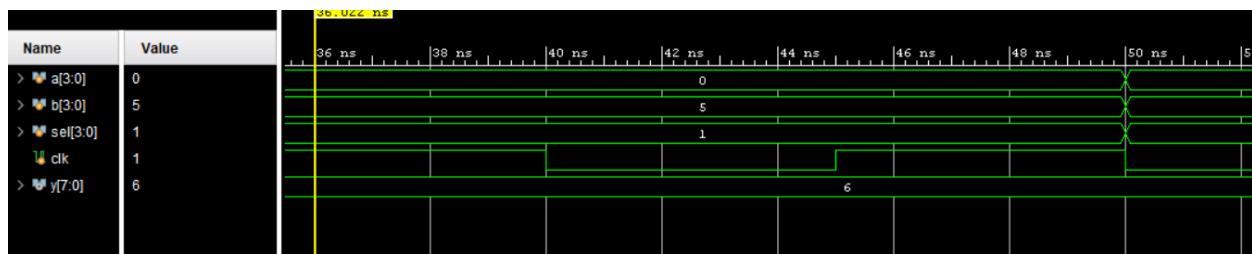

Transfer a

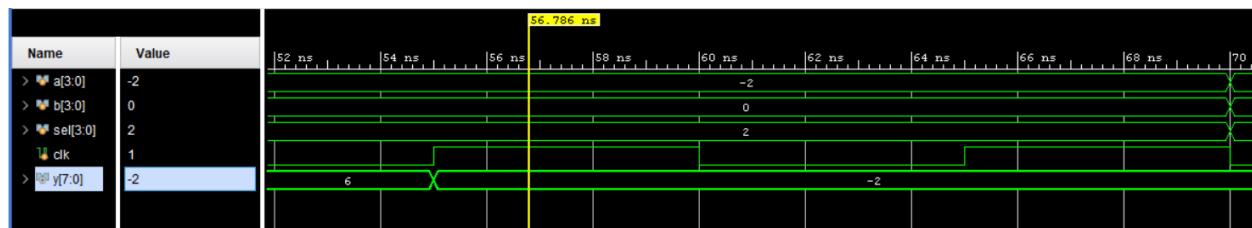


Transfer b




ARITHMETIC AND LOGICAL UNIT DESIGN


Decrement a

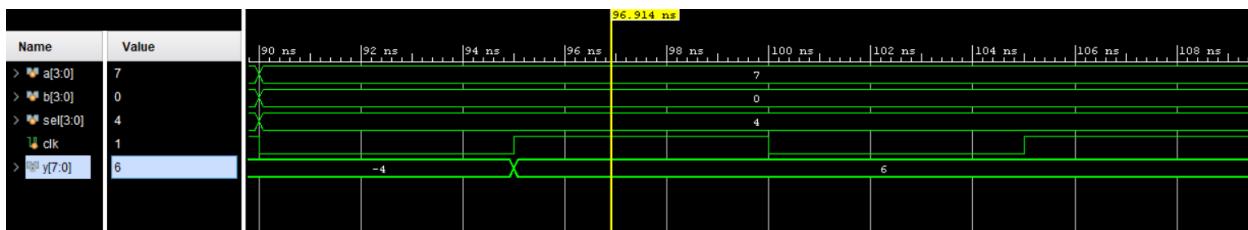


Multiply a and b

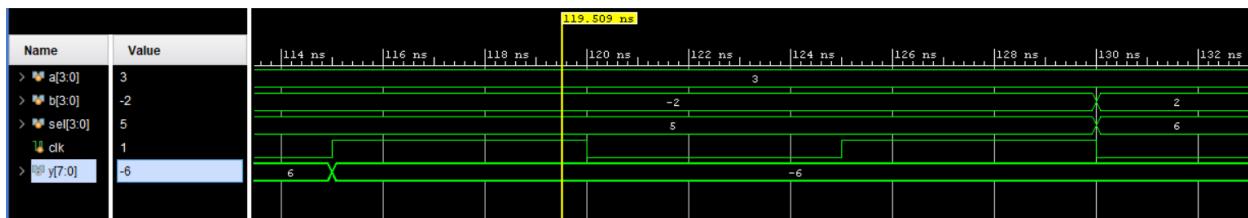

Add a and b

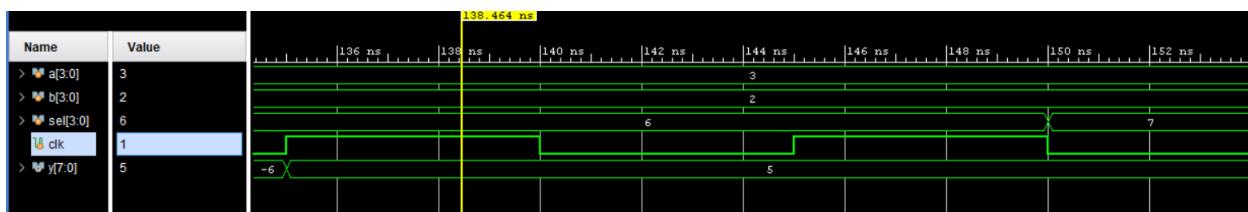


Subtract a and b

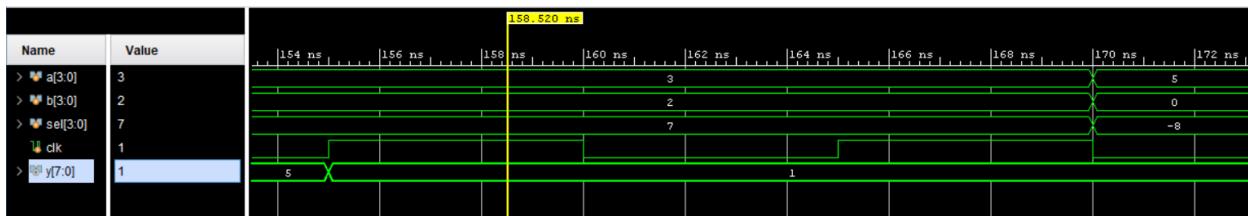


ARITHMETIC AND LOGICAL UNIT DESIGN

Logical unit


Complement a

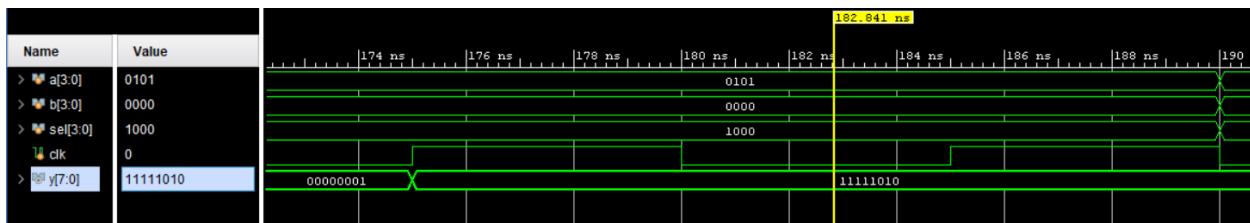


Complement b

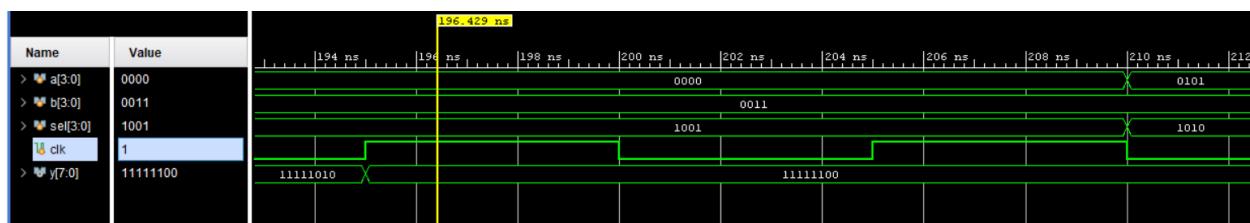

AND

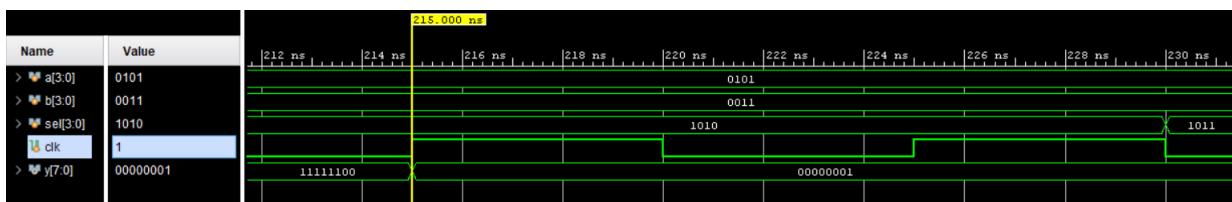


OR

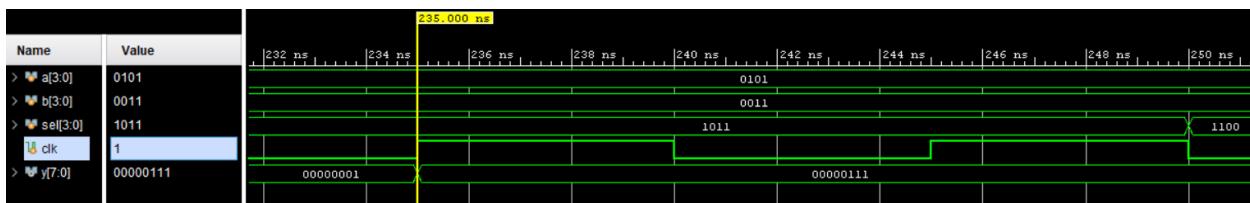


ARITHMETIC AND LOGICAL UNIT DESIGN


XOR

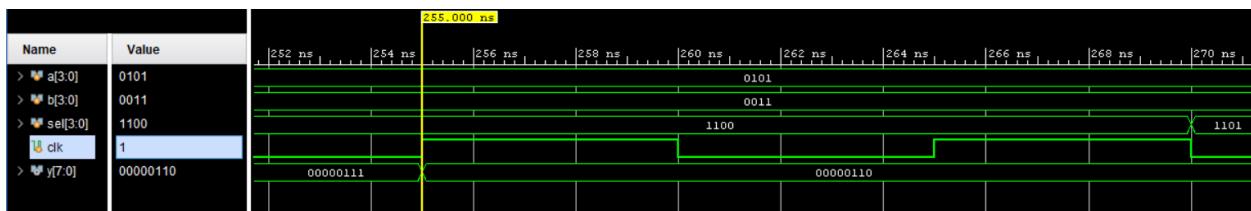


XNOR

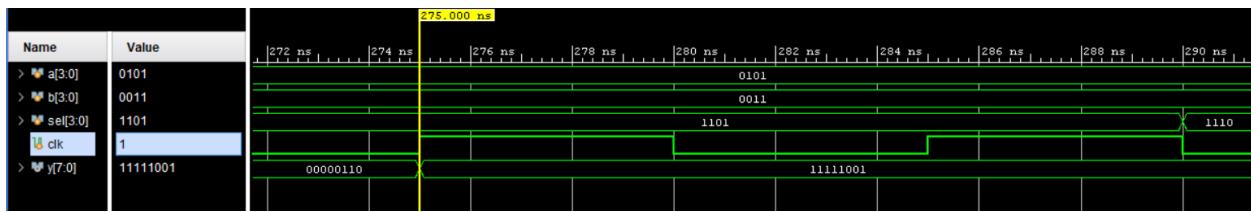

NAND

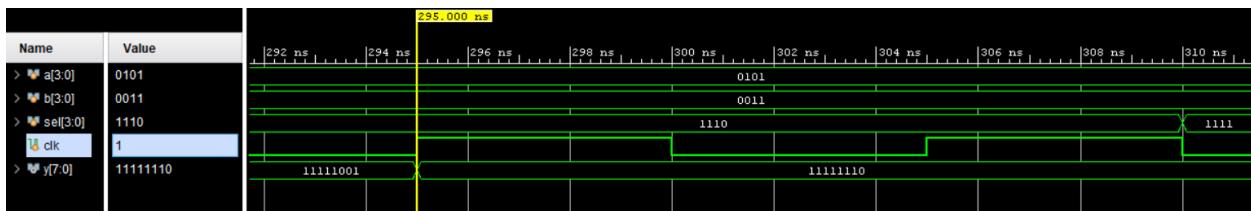


NOR

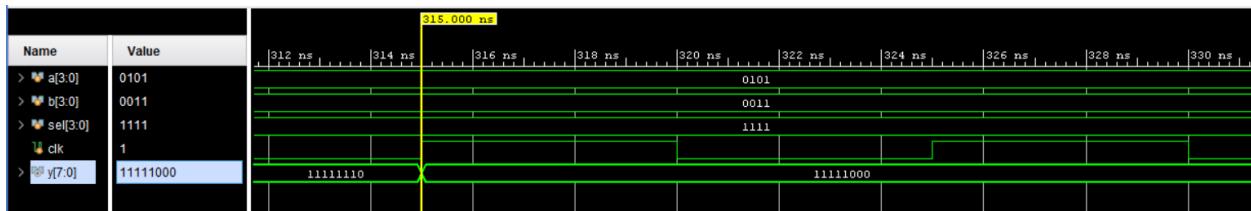


Transistor-level/Block-diagram schematics


Inverter gate

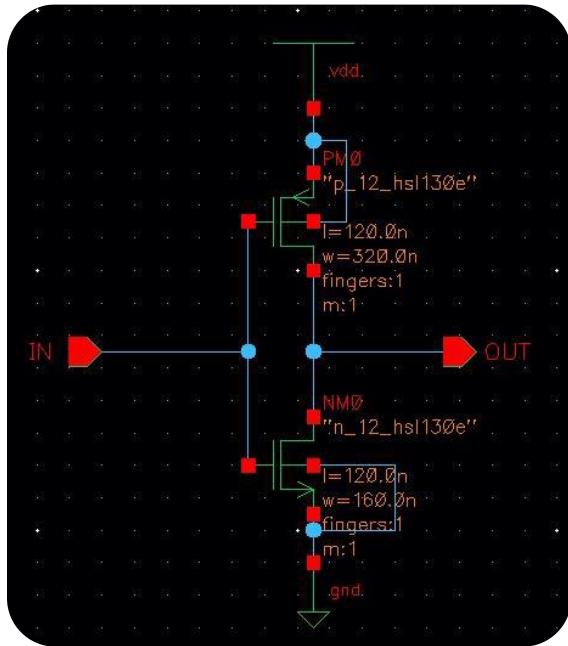

Schematic

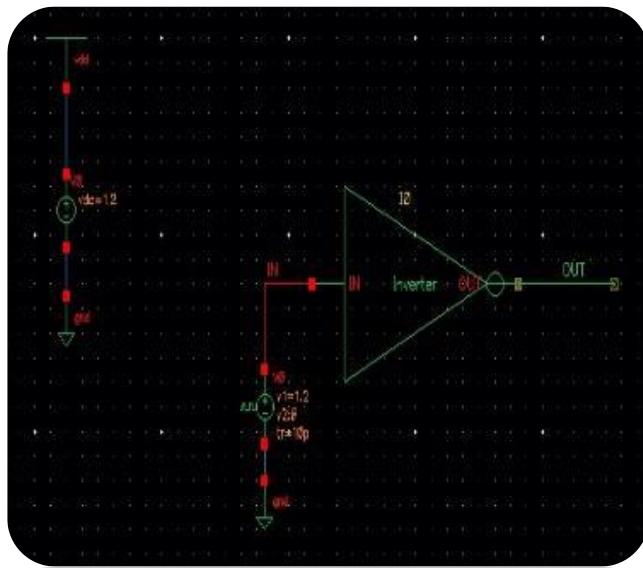


Symbol

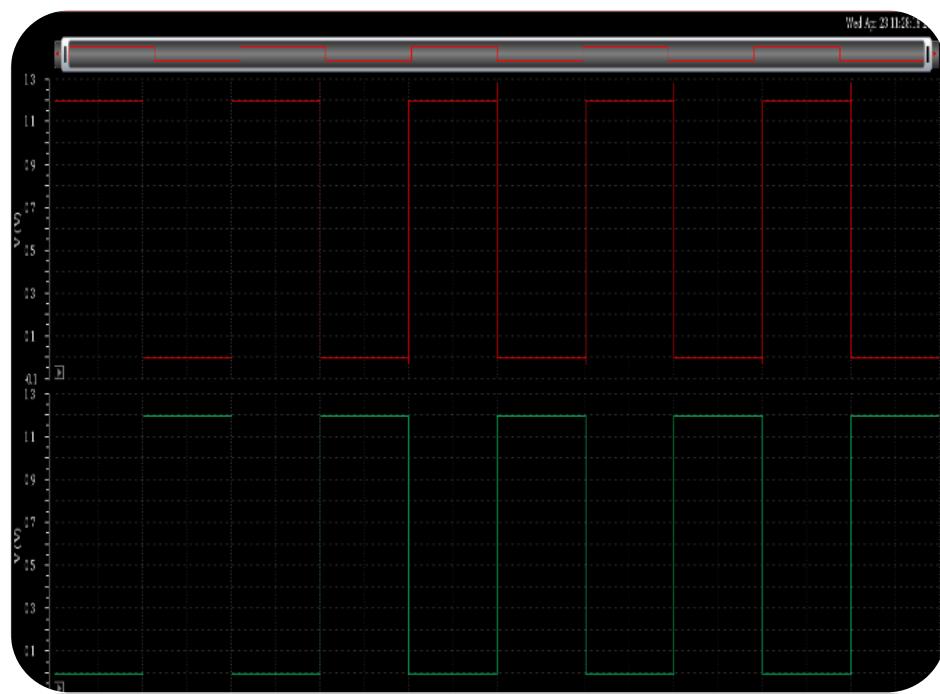


Testbench

ARITHMETIC AND LOGICAL UNIT DESIGN


AND gate

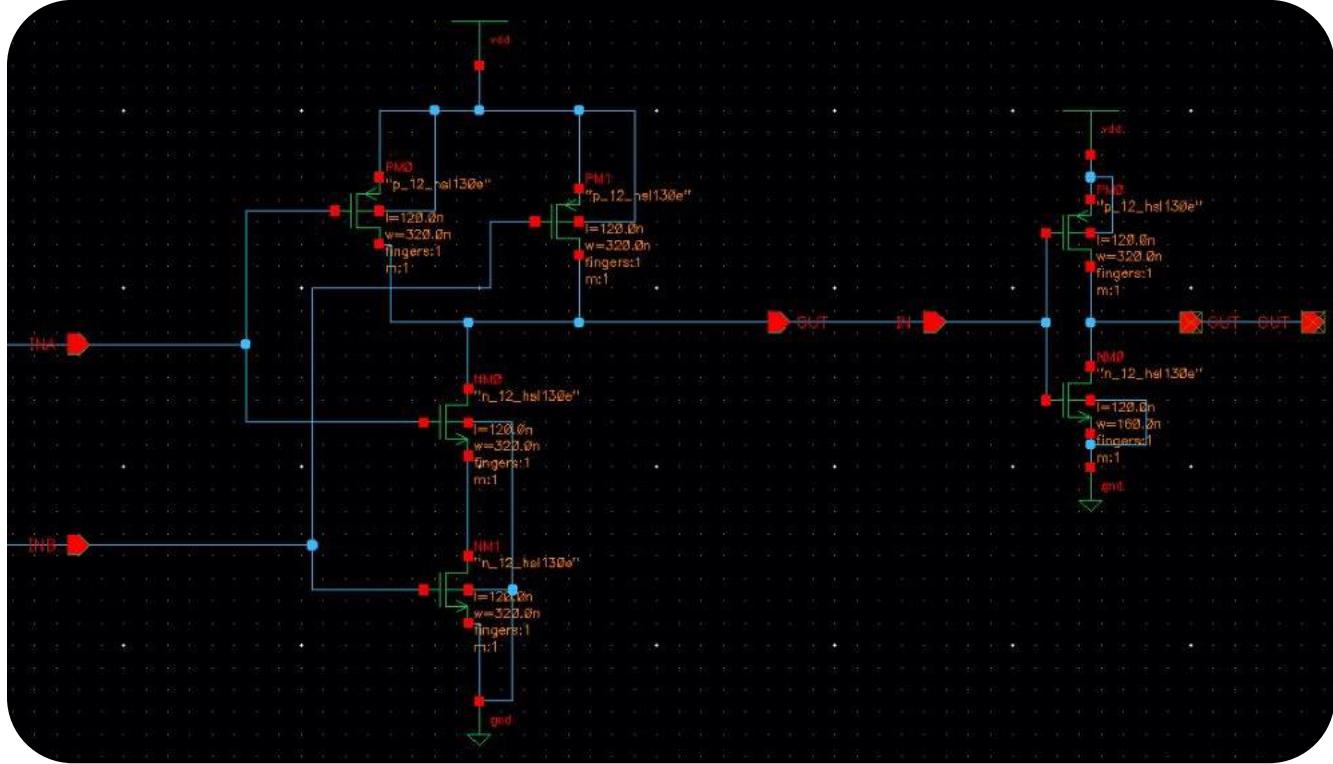

Schematic

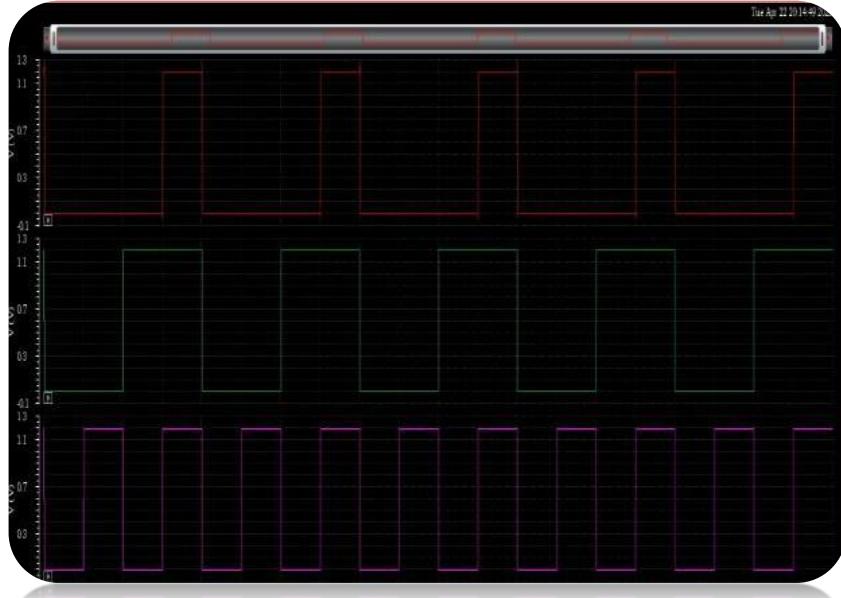


Testbench

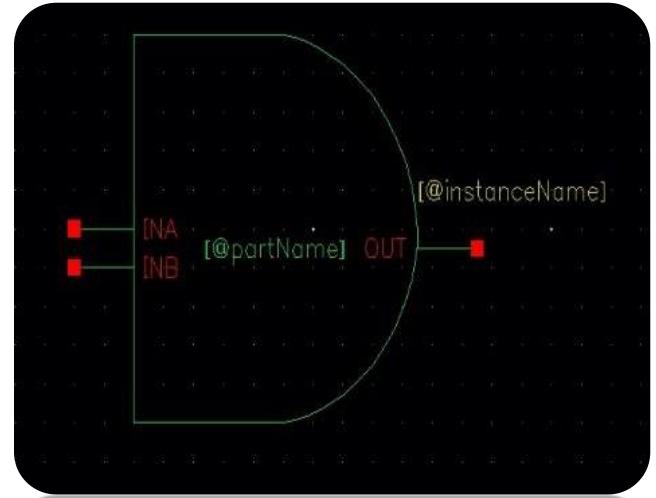


Symbol

ARITHMETIC AND LOGICAL UNIT DESIGN


OR gate

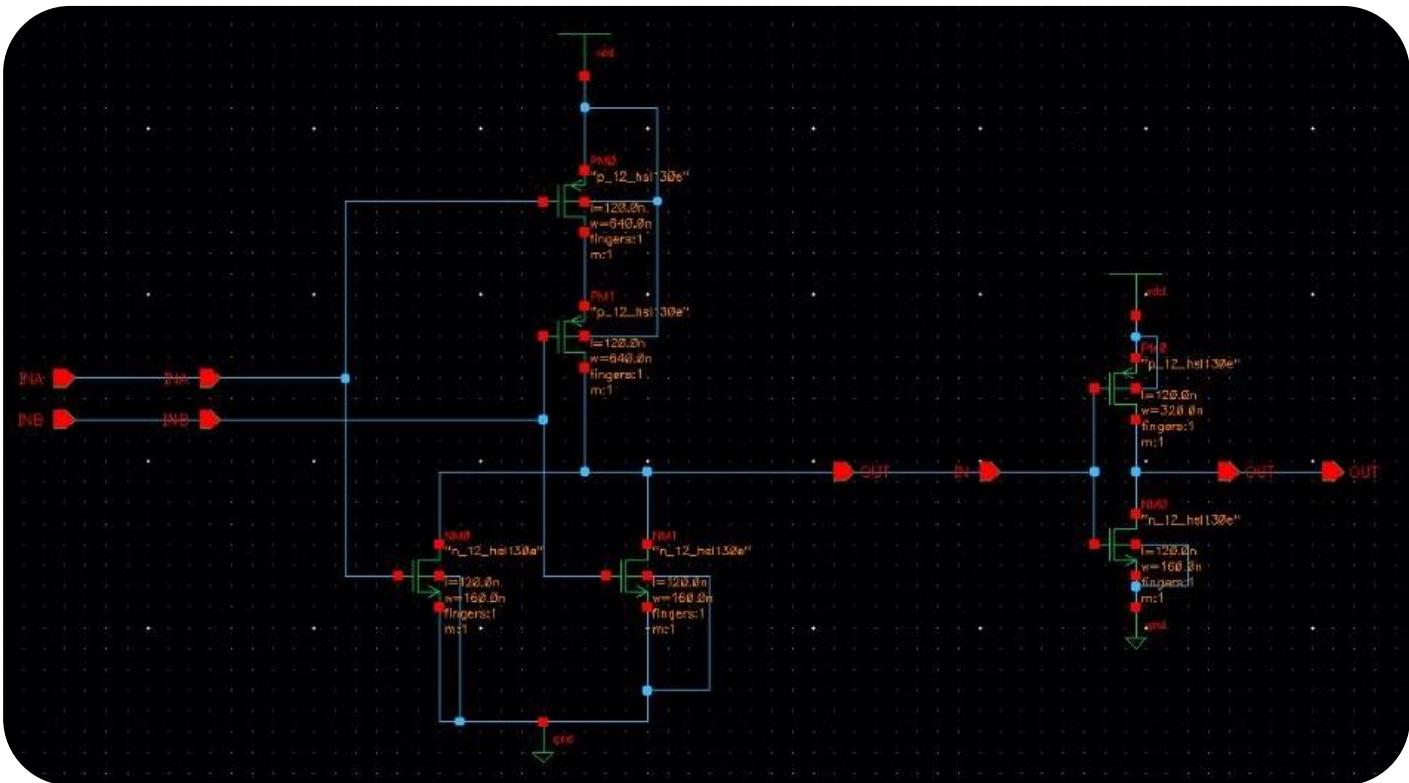

Schematic

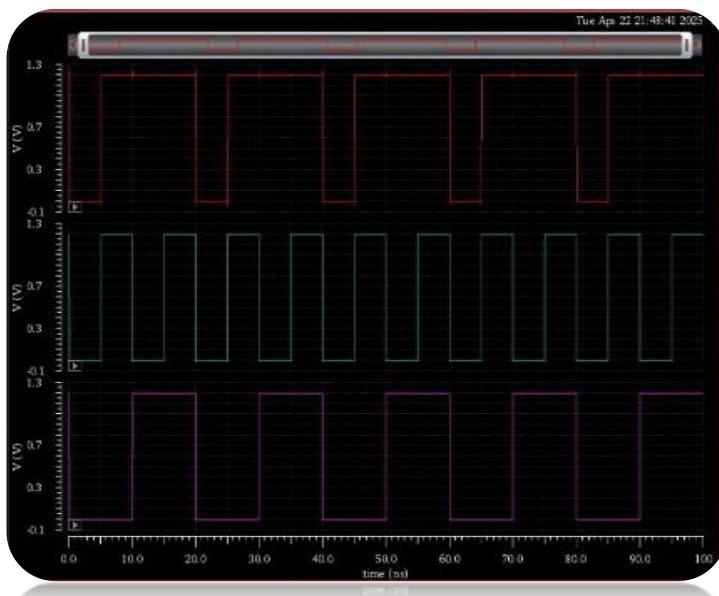


Testbench

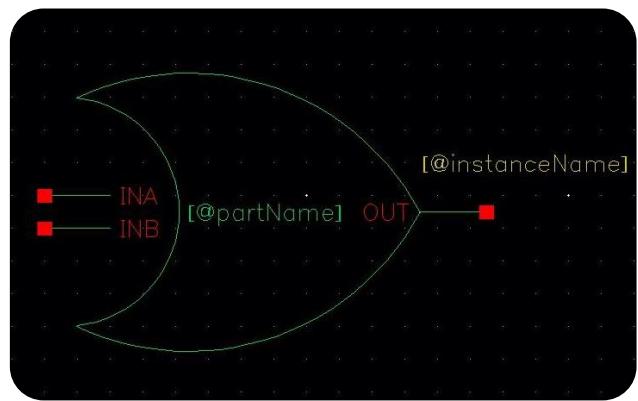


Symbol

ARITHMETIC AND LOGICAL UNIT DESIGN


NOR gate

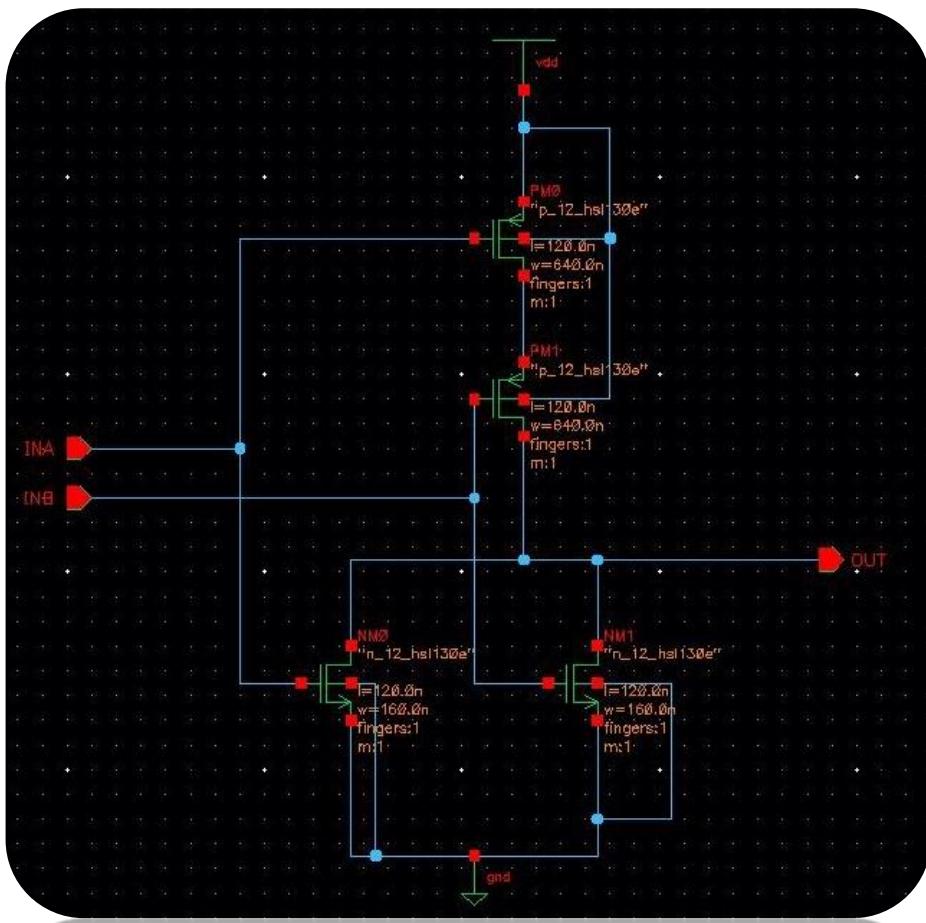

Schematic

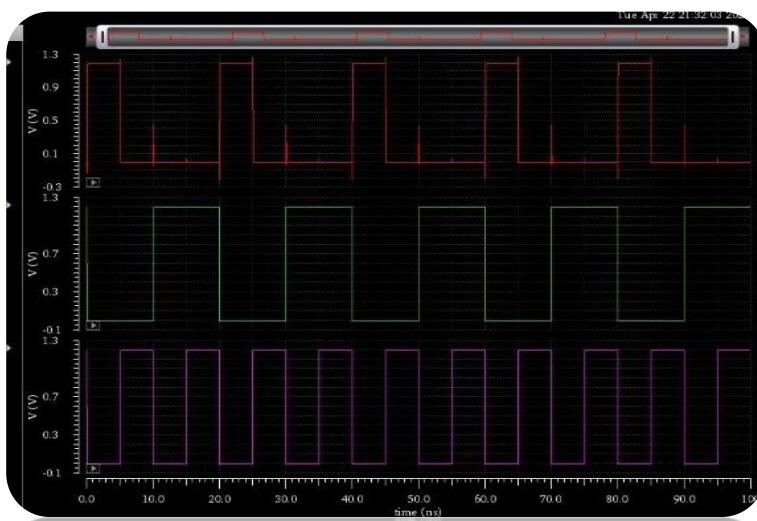


Testbench

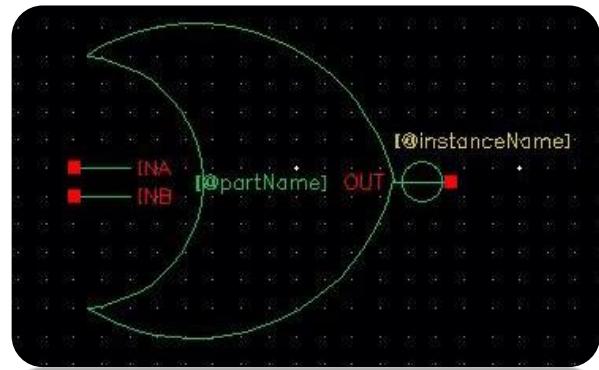


Symbol

ARITHMETIC AND LOGICAL UNIT DESIGN


NAND gate

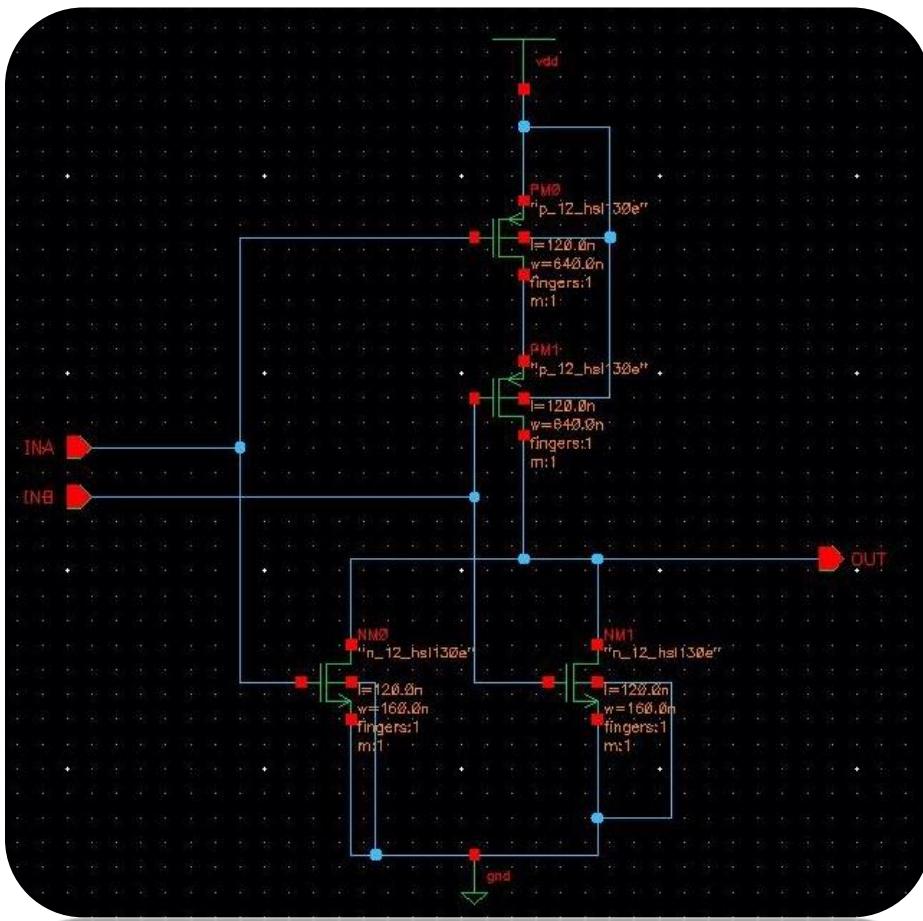

Schematic

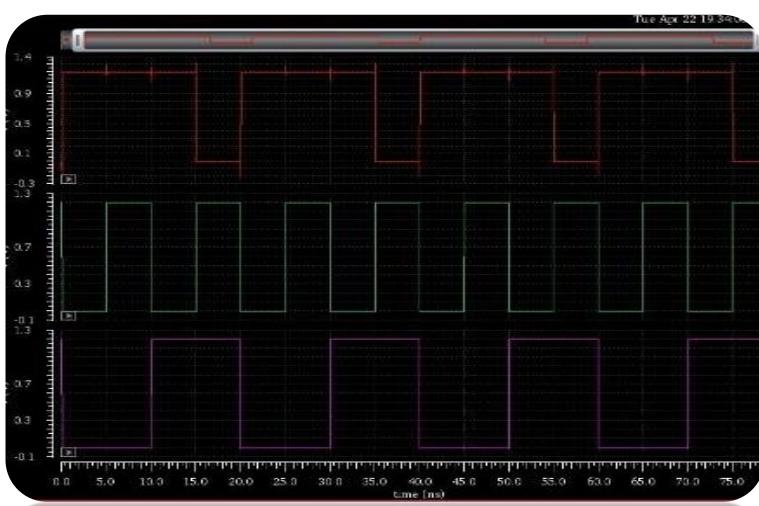


Testbench

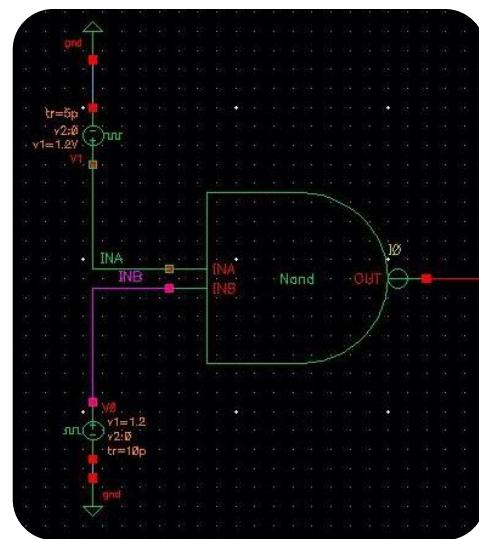


Symbol

ARITHMETIC AND LOGICAL UNIT DESIGN


XOR gate

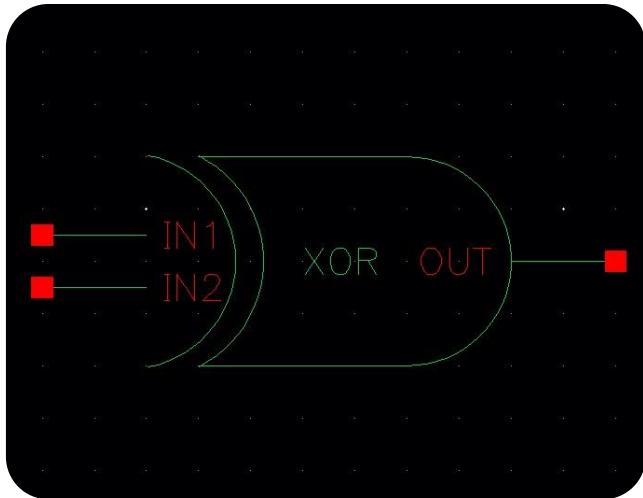

Symbol

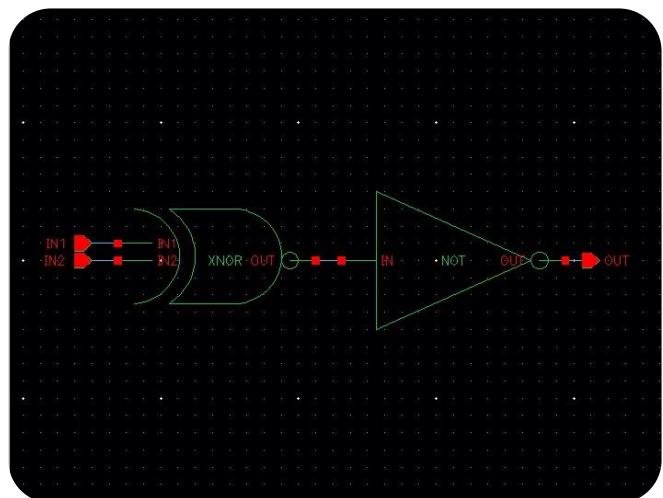


Schematic

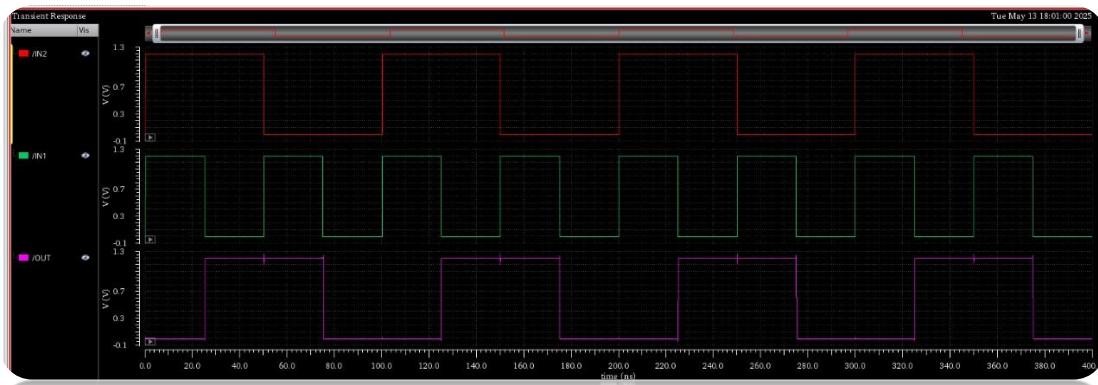


Testbench

ARITHMETIC AND LOGICAL UNIT DESIGN


XNOR gate

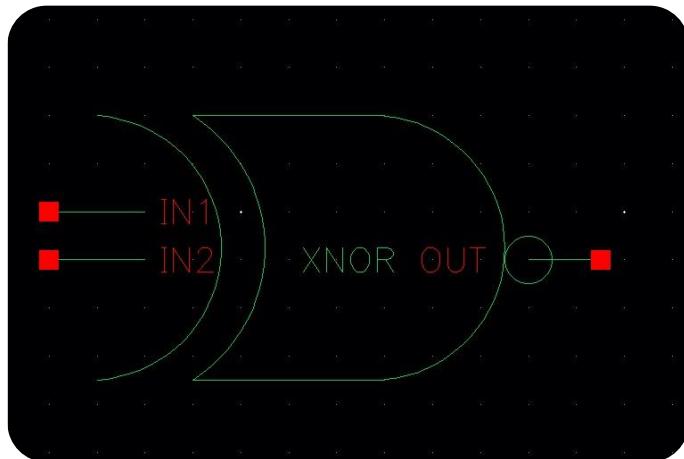

Symbol

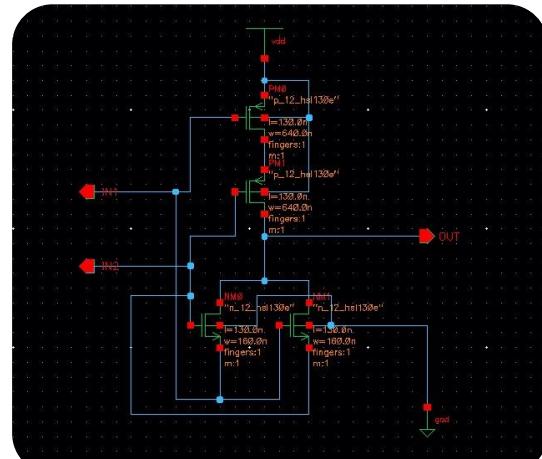


Schematic

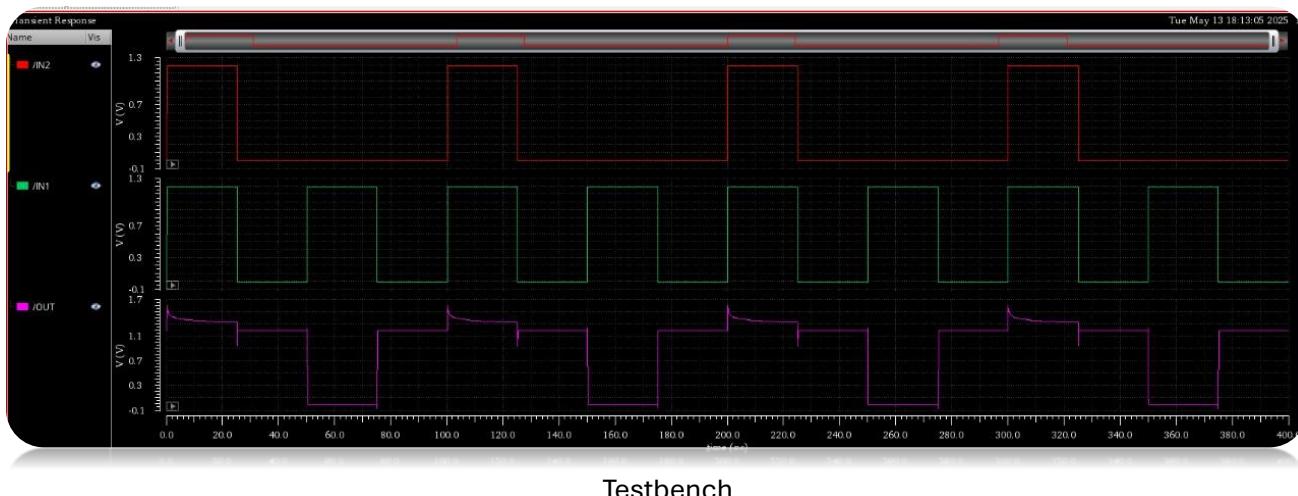


Testbench

Logical unit

Constructing 1 bit logic unit:

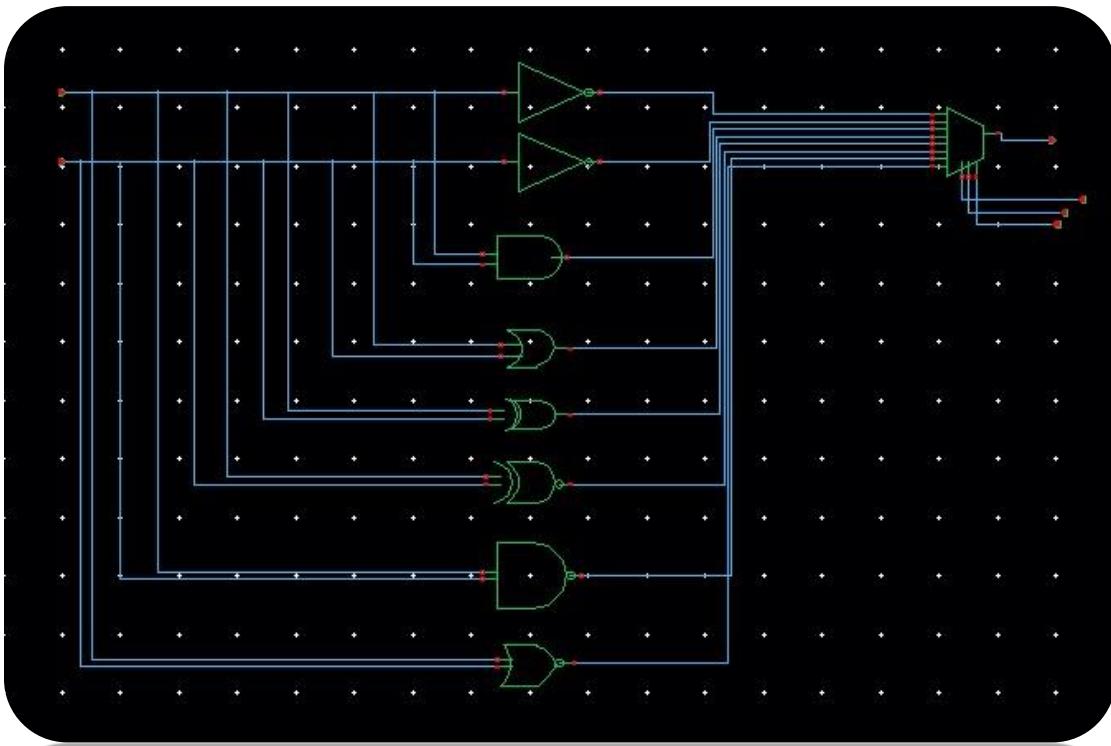


1 bit logic Symbol:

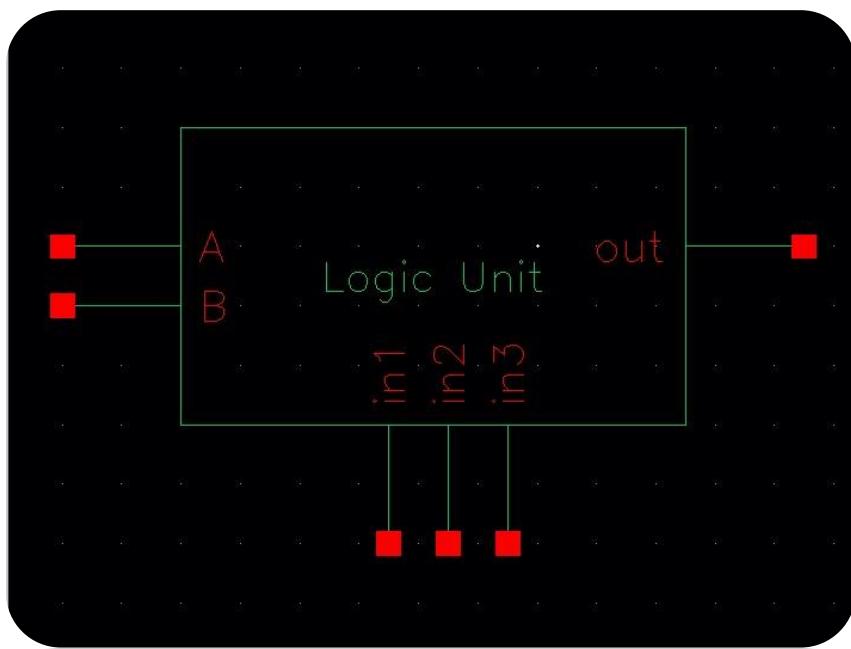


ARITHMETIC AND LOGICAL UNIT DESIGN

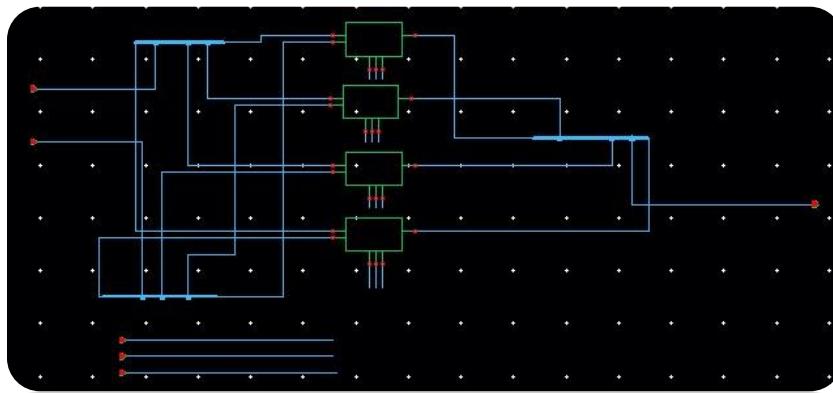Constructing four bit logic unit from the one bit:



Four bit logic unit symbol:

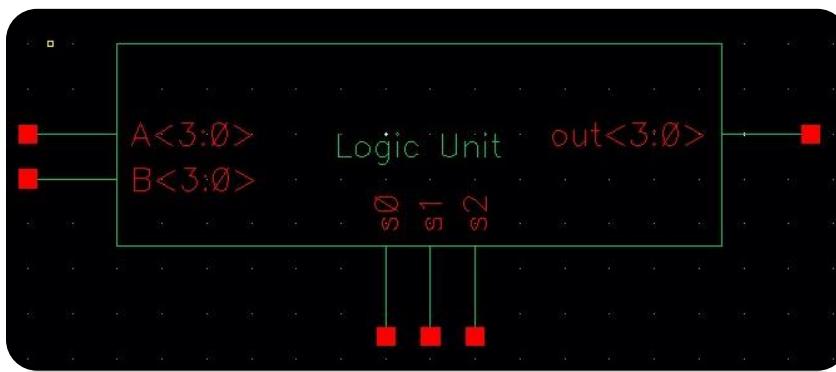


Output Waveform:




ARITHMETIC AND LOGICAL UNIT DESIGN

TG

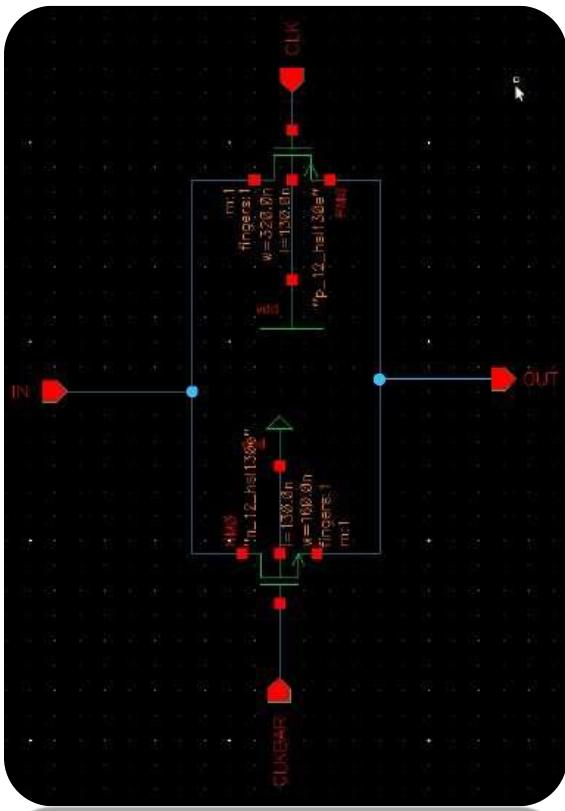


Schematic

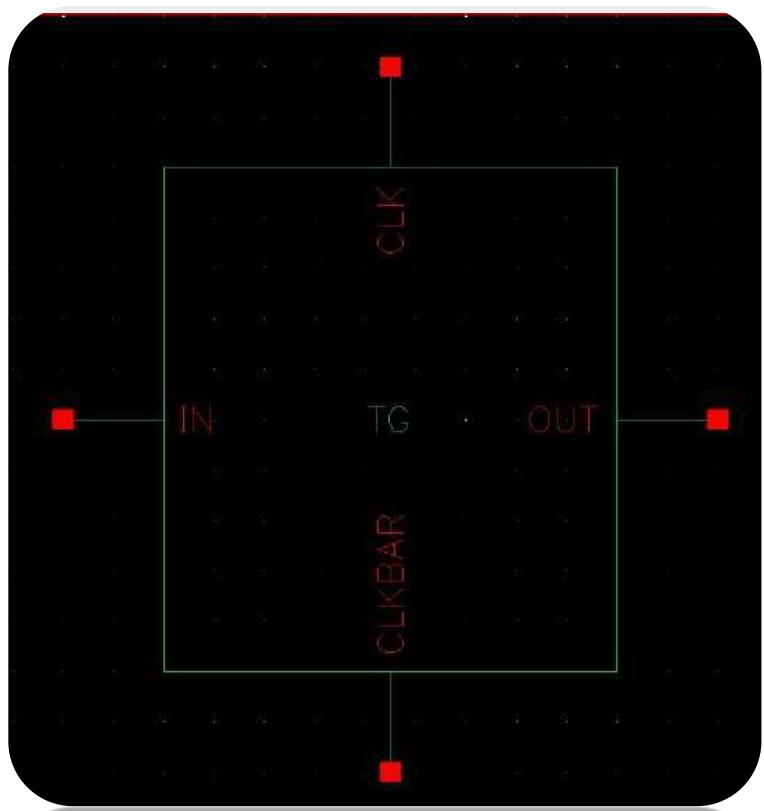

Sybmol

ARITHMETIC AND LOGICAL UNIT DESIGN

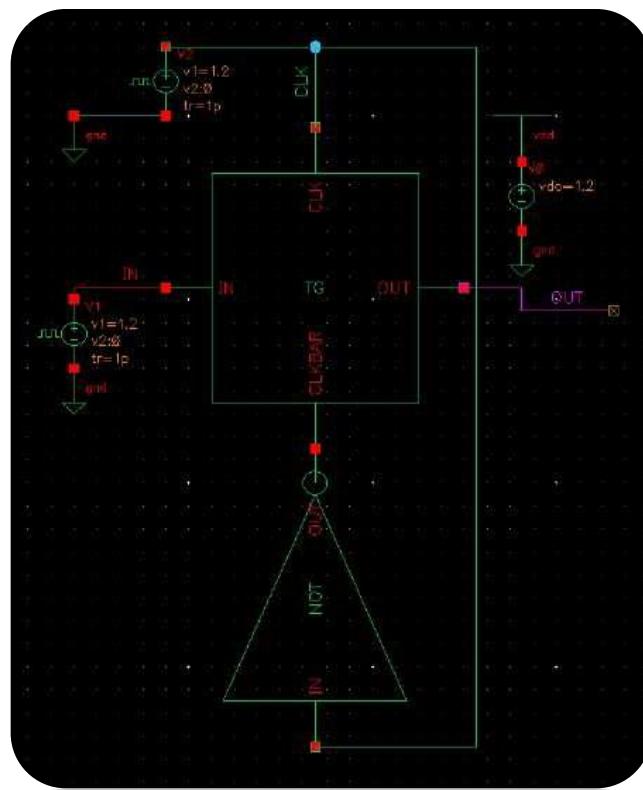


Testbench



Wavefrom

ARITHMETIC AND LOGICAL UNIT DESIGN

Flip-Flop

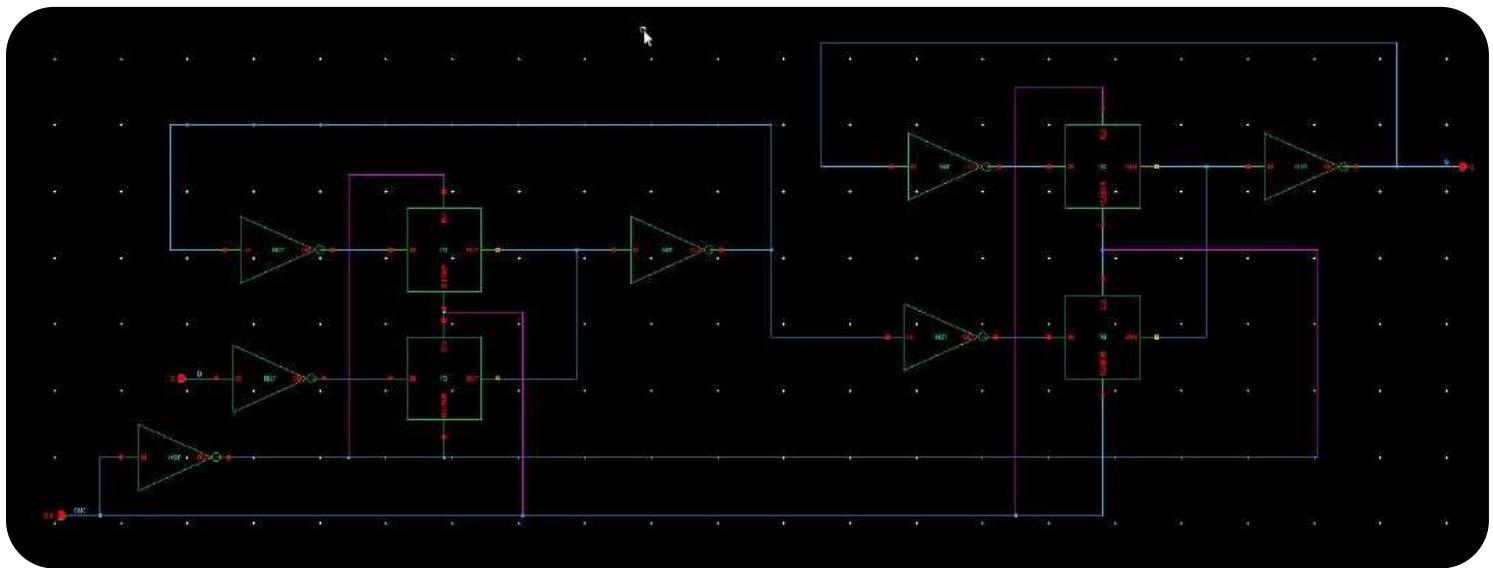


Schematic




Symbol

ARITHMETIC AND LOGICAL UNIT DESIGN

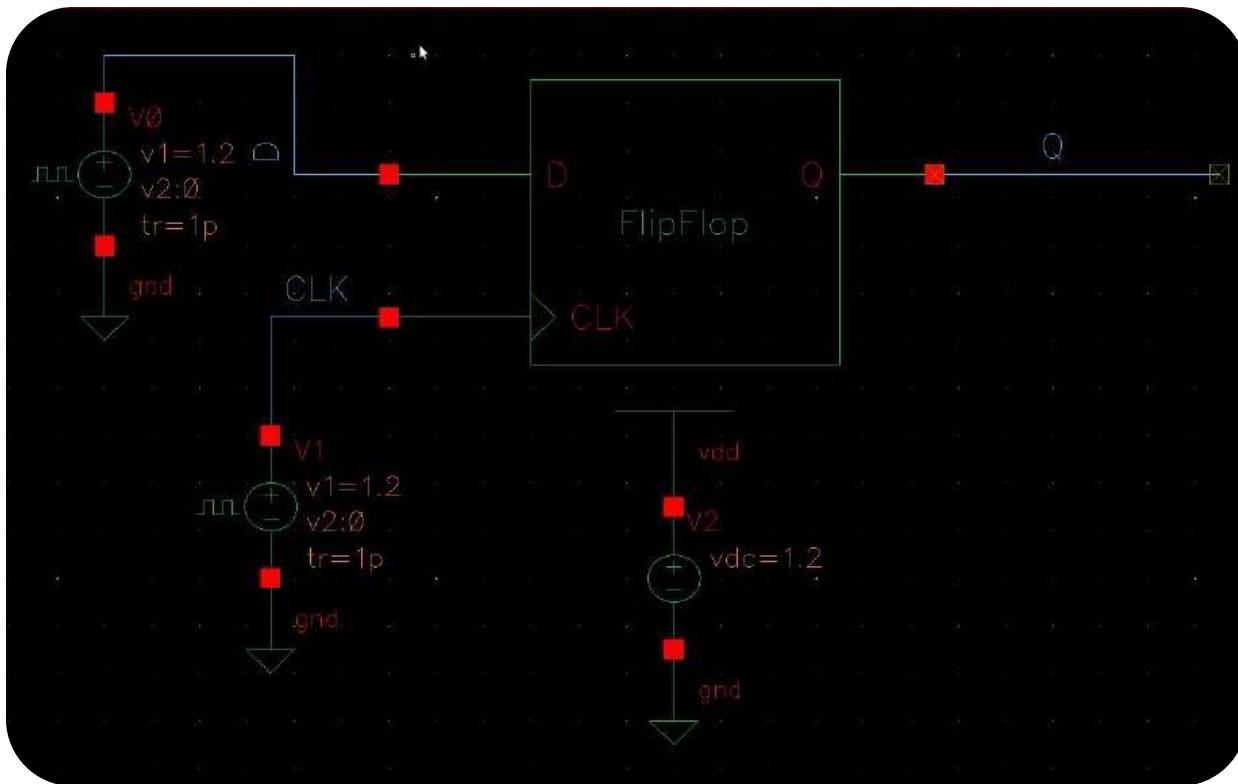

Testbench

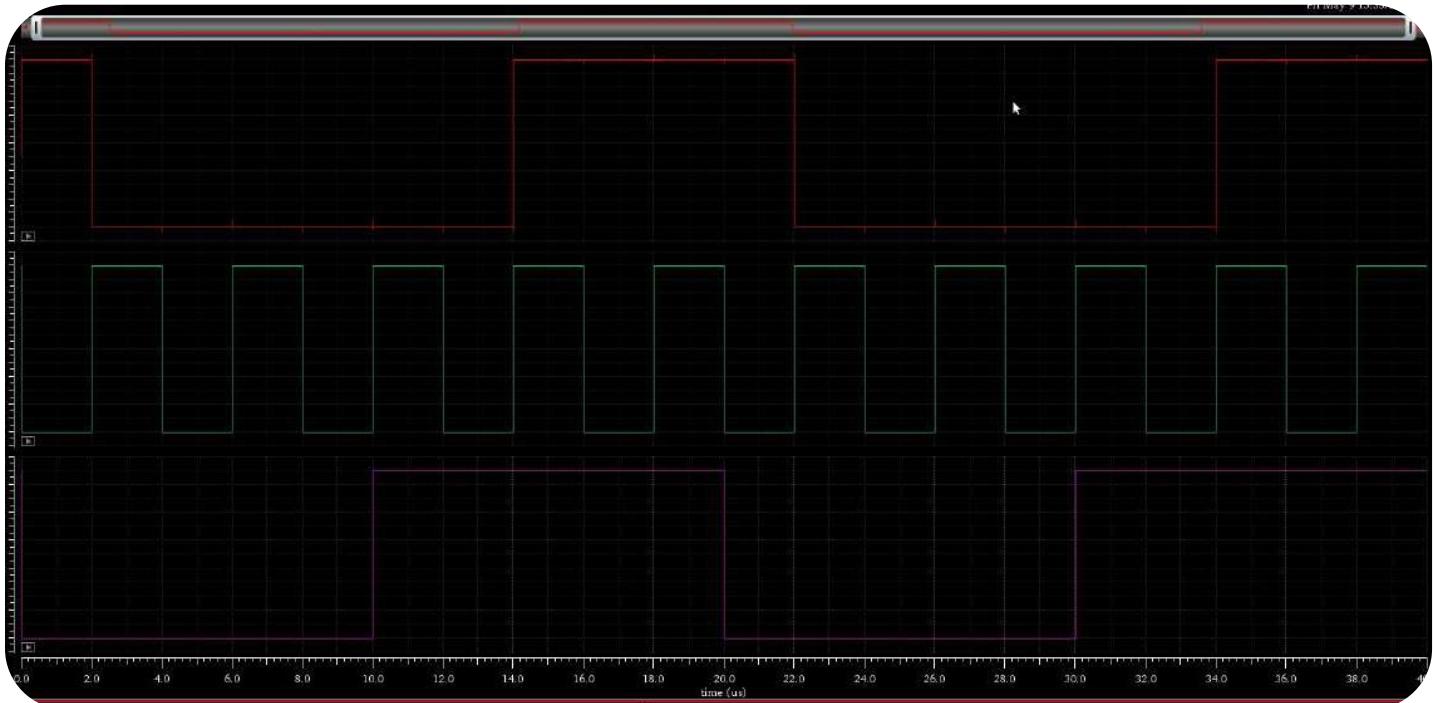


Wavefrom


ARITHMETIC AND LOGICAL UNIT DESIGN

MUX 2x1

Schematic

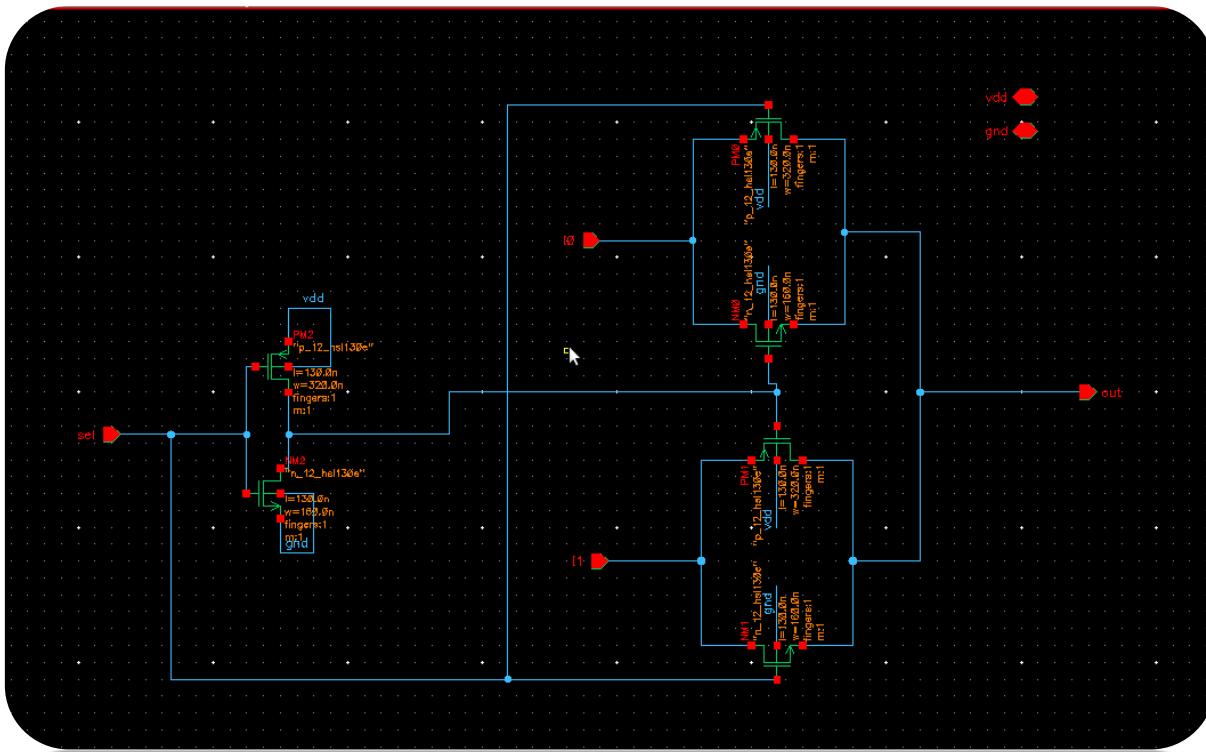


Symbol

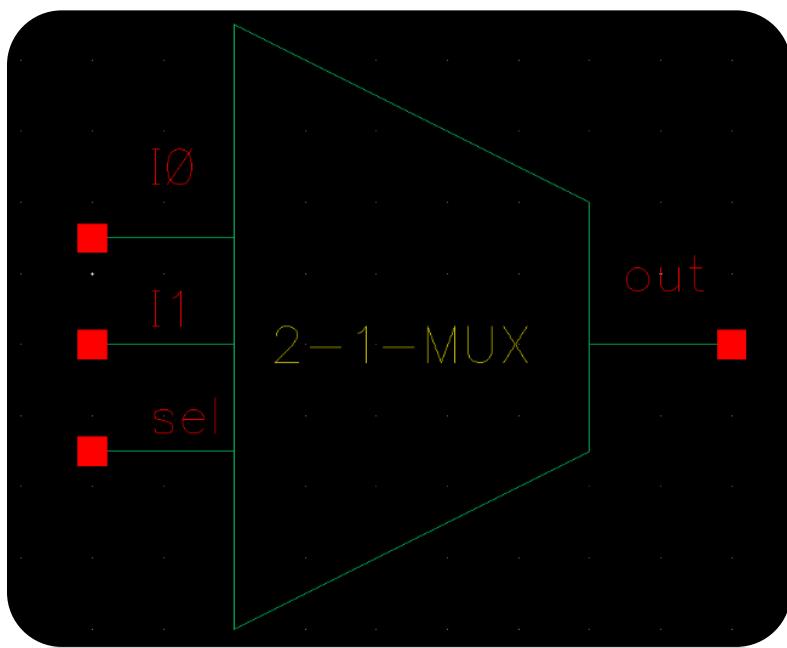


ARITHMETIC AND LOGICAL UNIT DESIGN

Testbench Cell

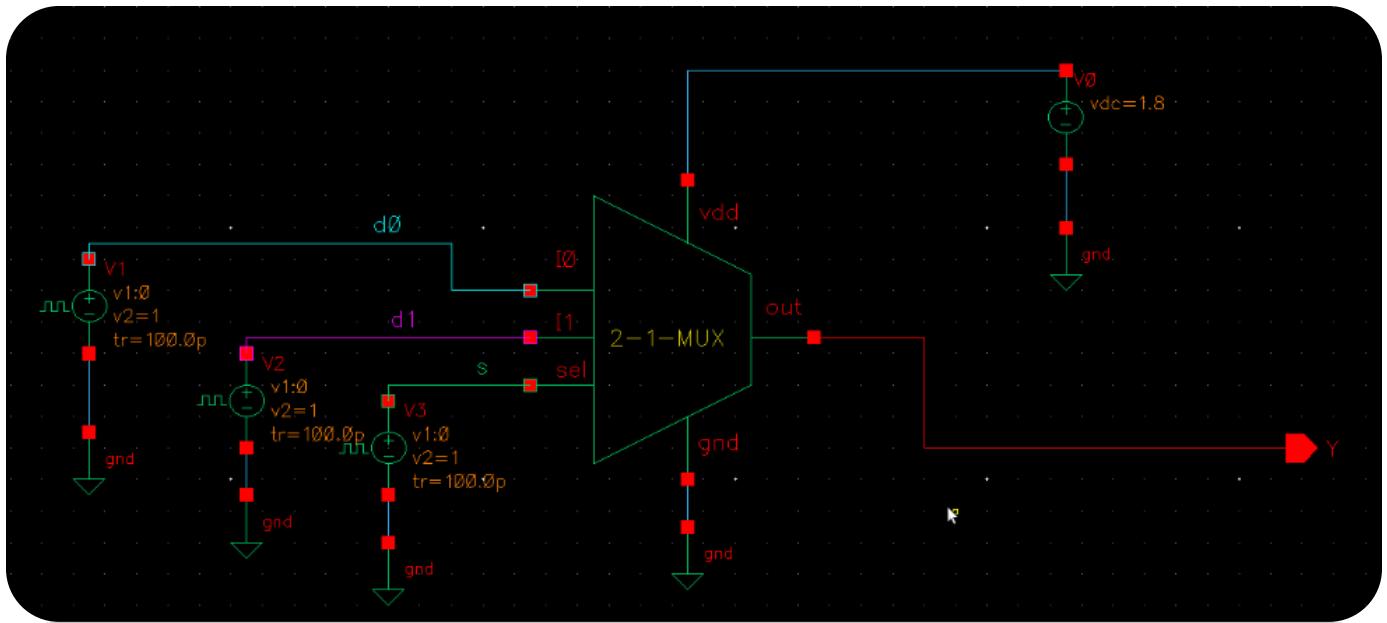


Output Waveform

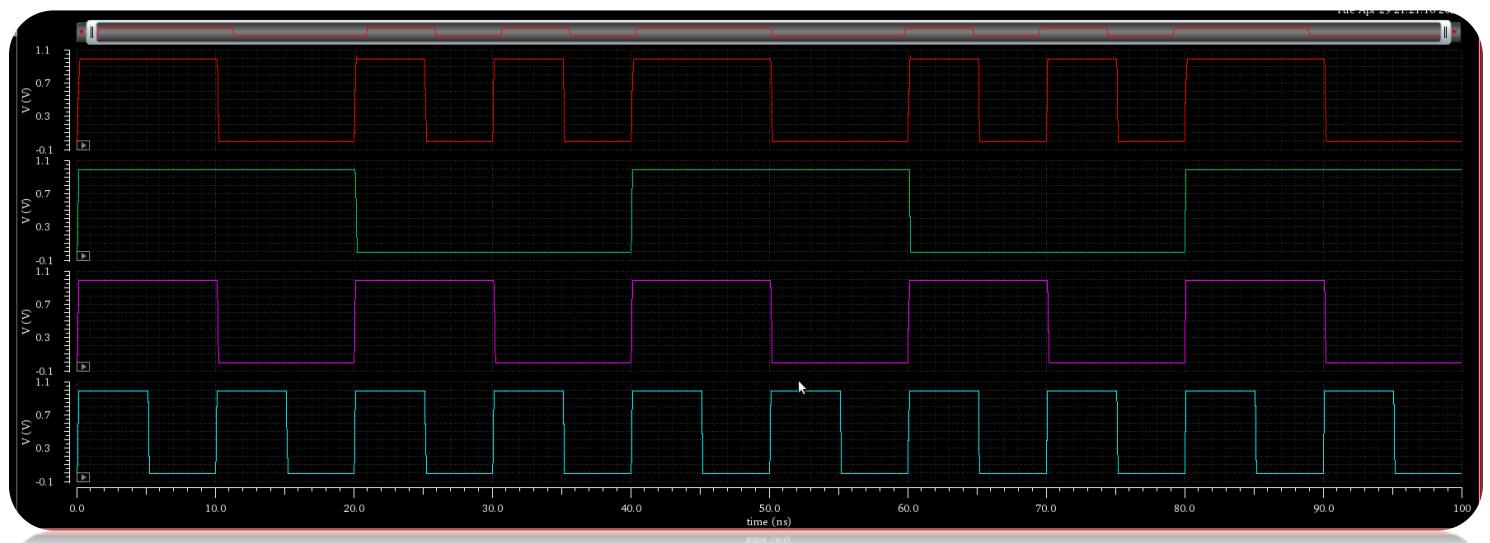


MUX 8x1

Schematic of 8-1 mux

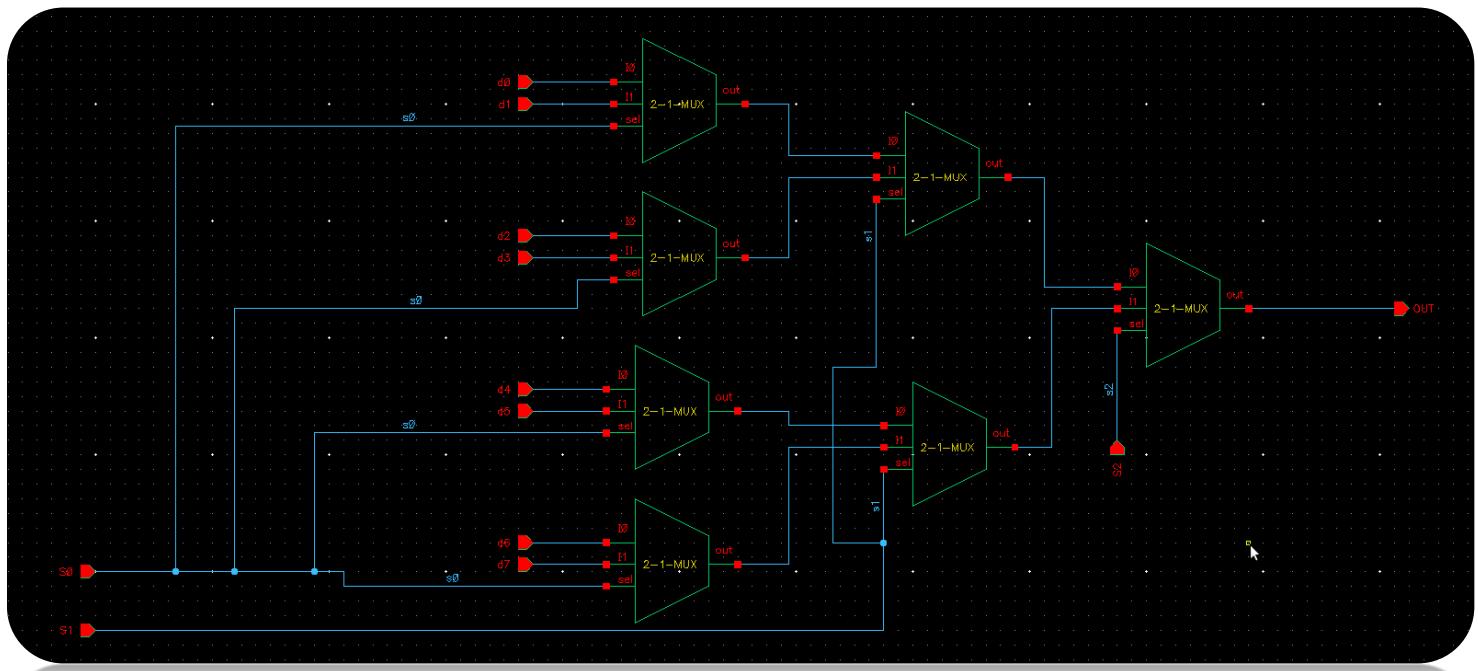


Symbol

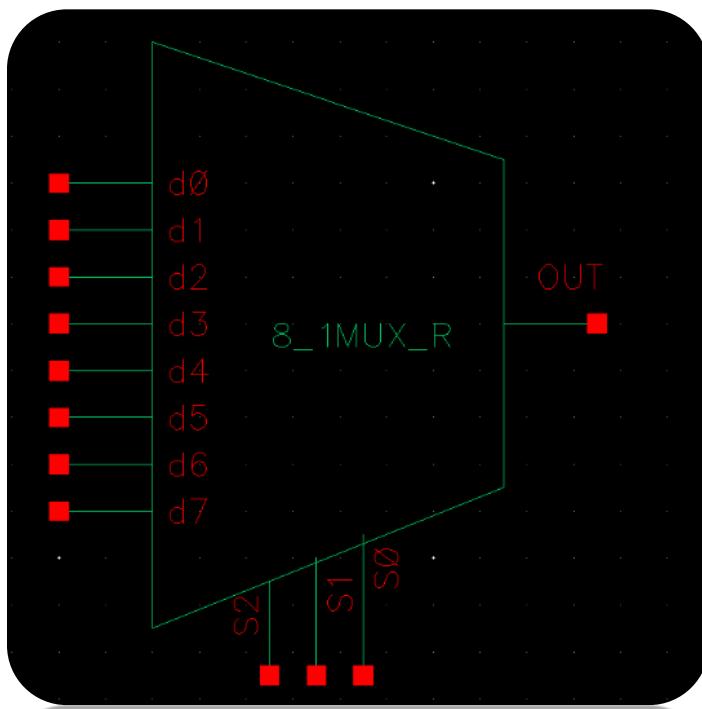


Note: The R in the symbol name refers to real because we construct a 8-1 mux using 4_1 muxs but it doesn't work smoothly as expected.

ARITHMETIC AND LOGICAL UNIT DESIGN

Testing of 8-1 Multiplexer

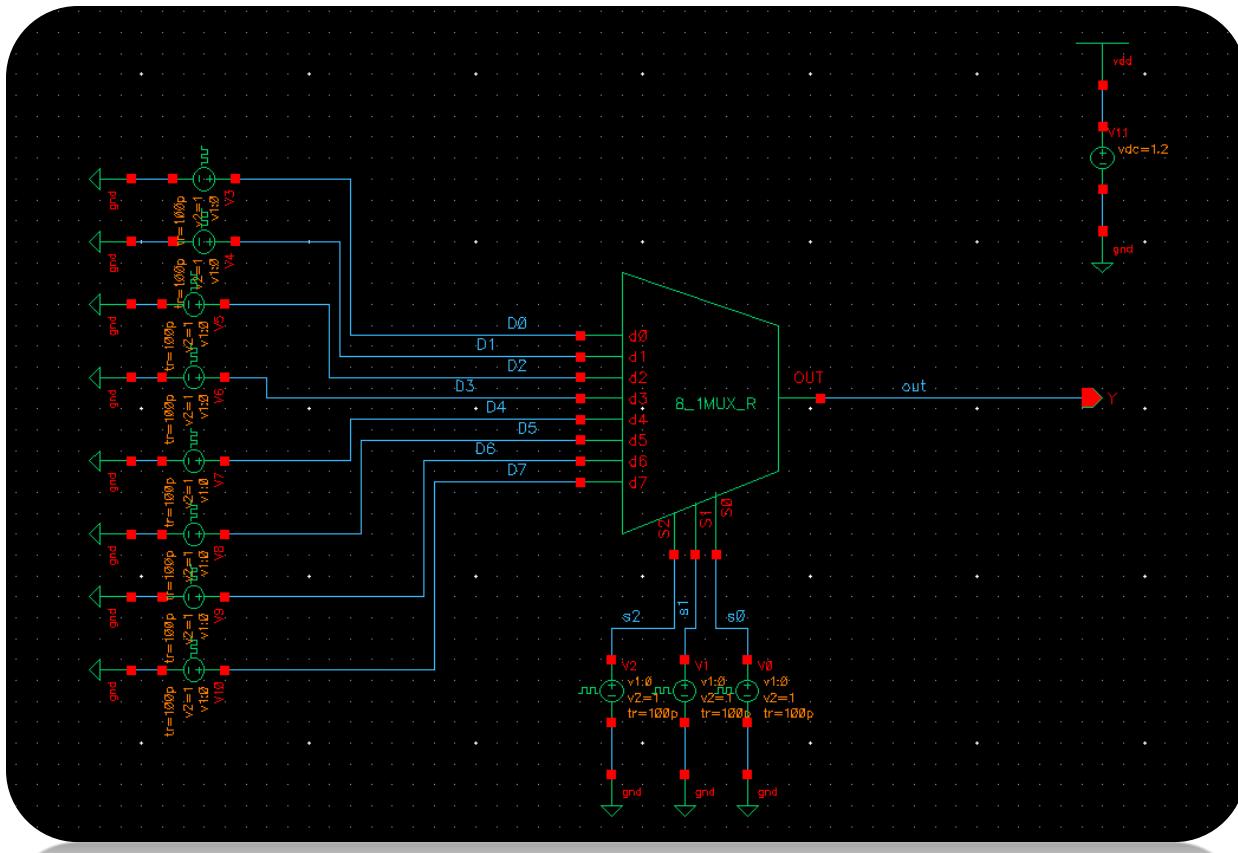


Output Waveform

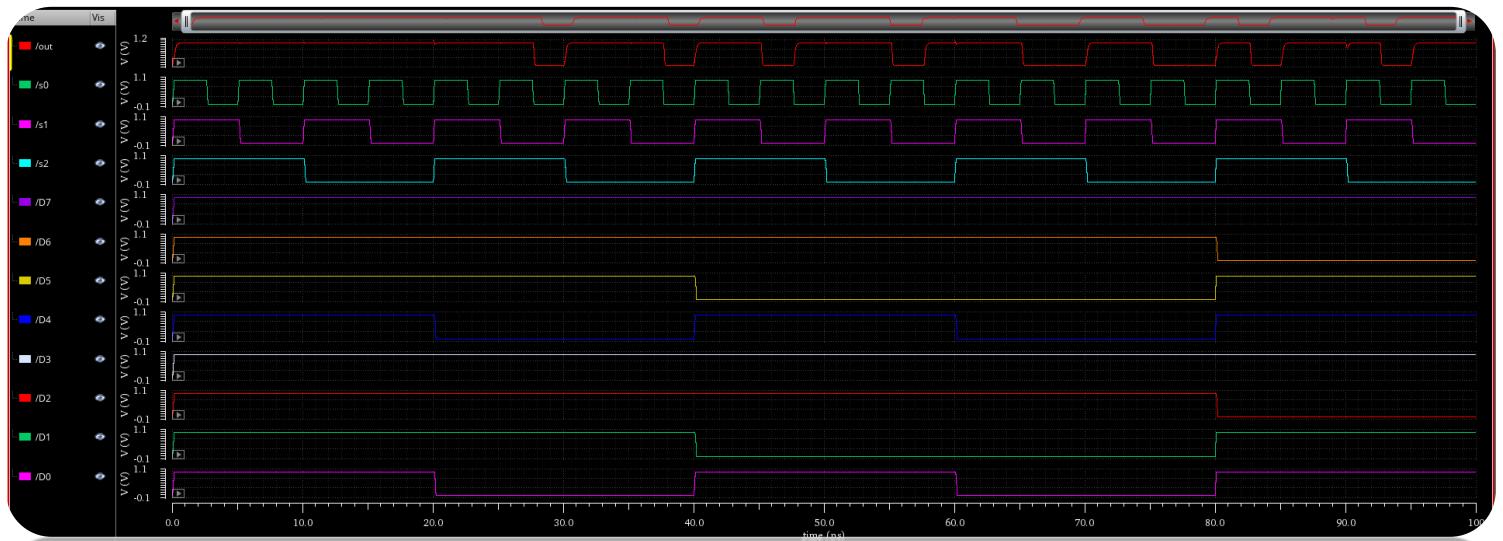


ARITHMETIC AND LOGICAL UNIT DESIGN


AOI

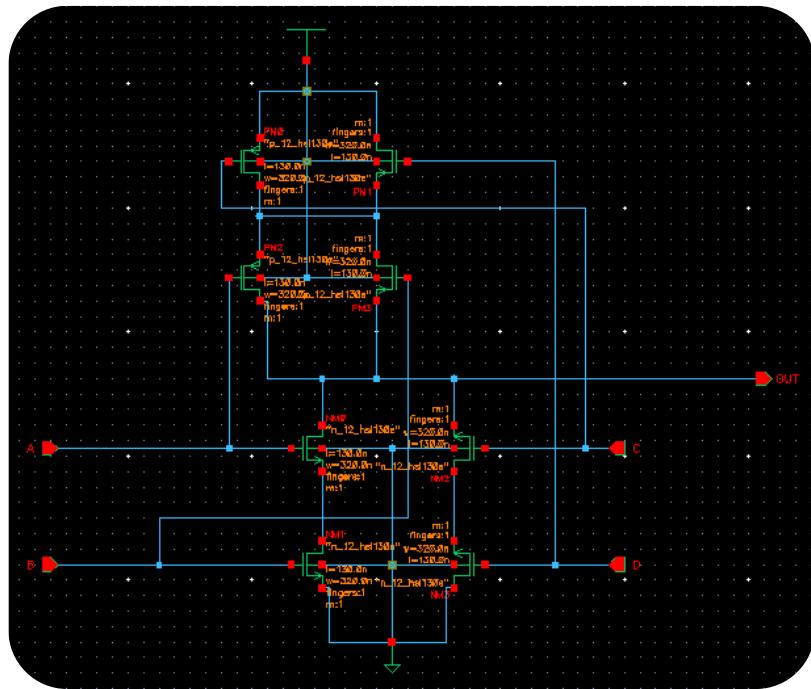

Schematic

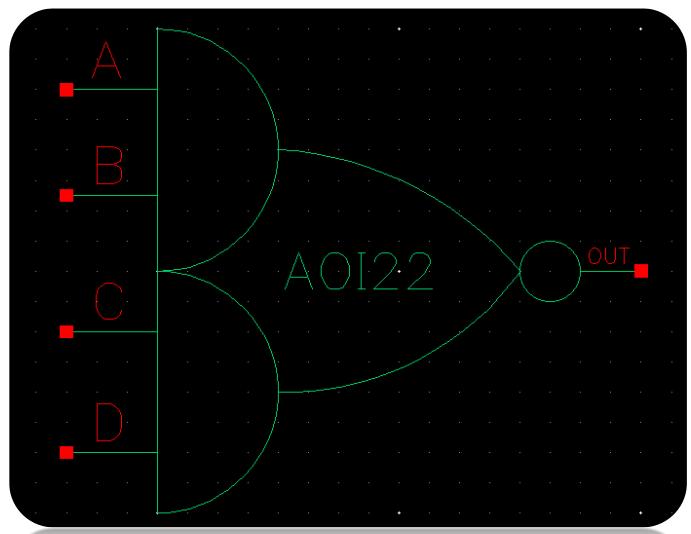


Symbol

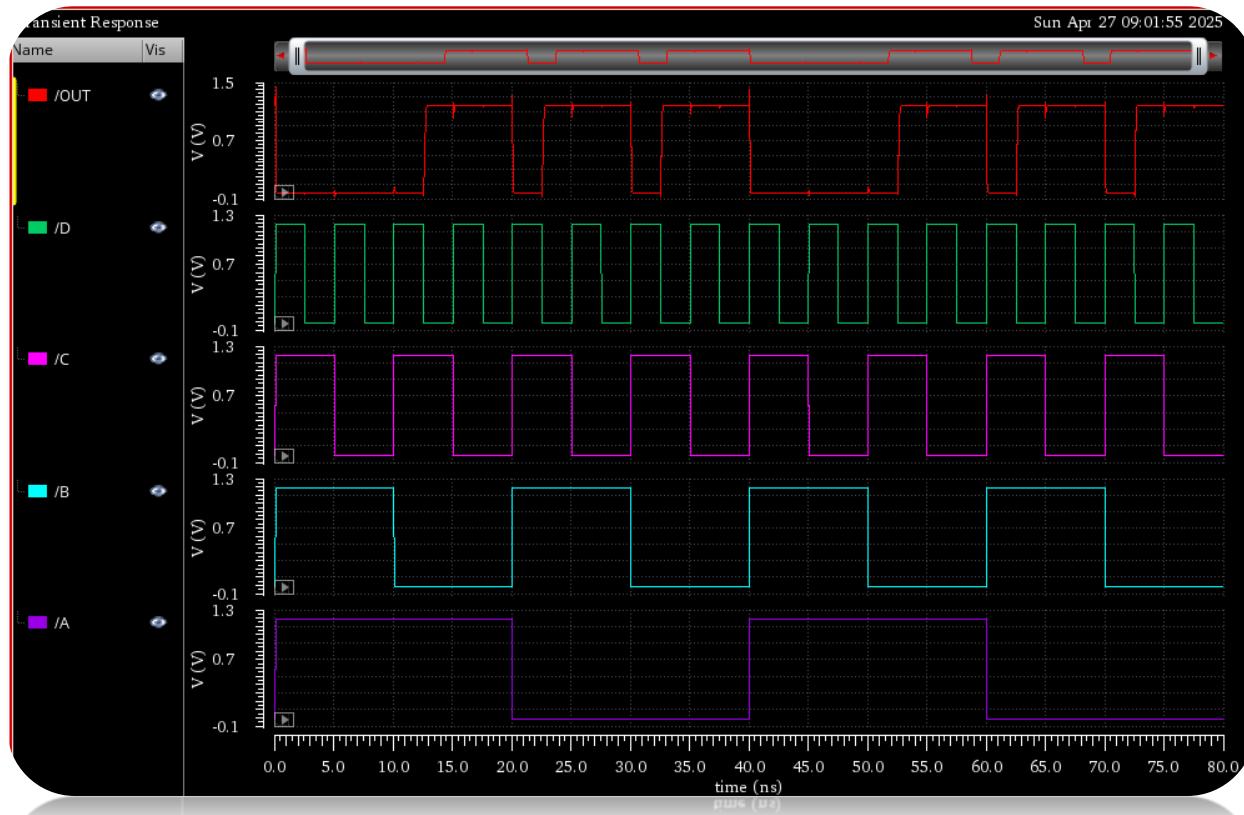


Testbench

ARITHMETIC AND LOGICAL UNIT DESIGN


Full Adder (1 bit)

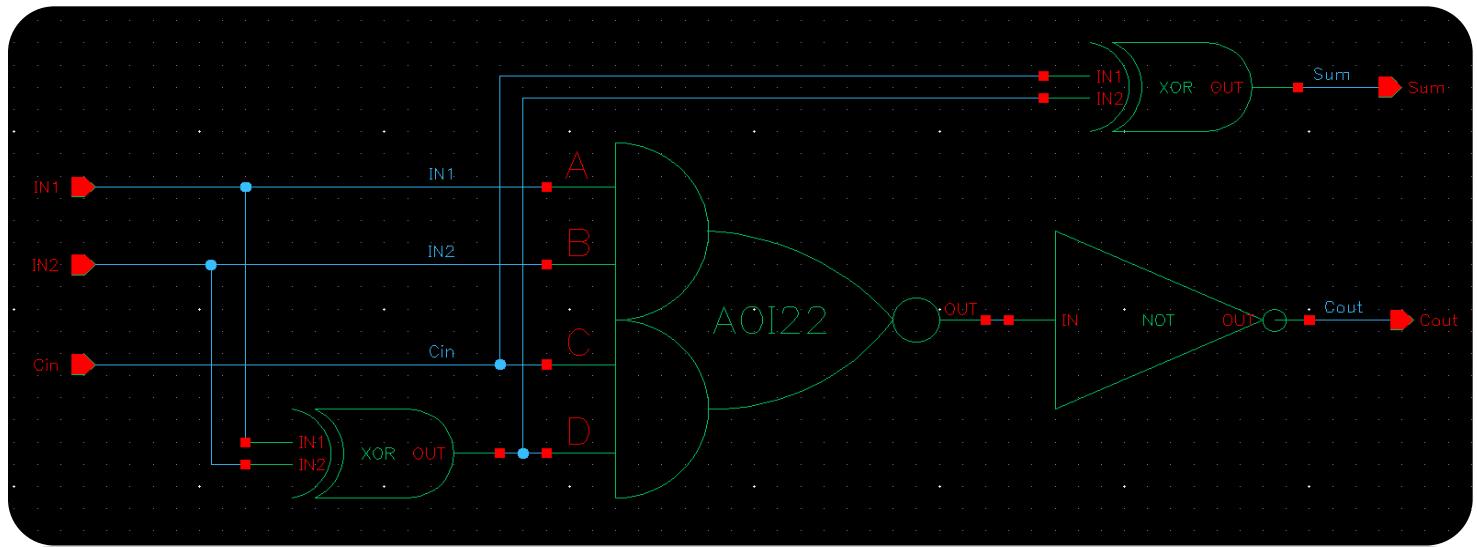

Schematic

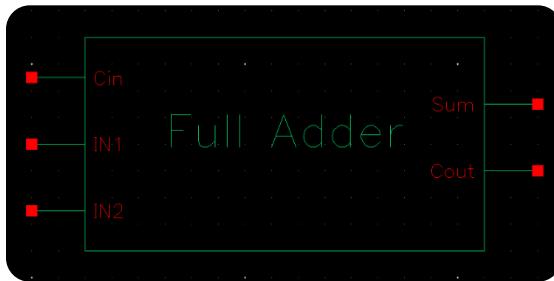

Symbol

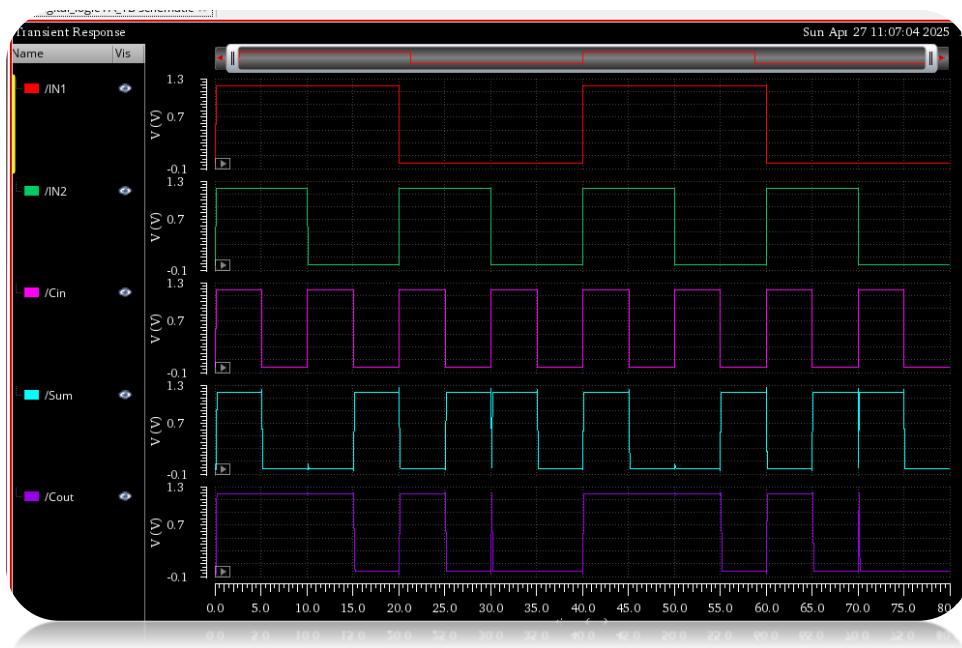


Testbench


A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

ARITHMETIC AND LOGICAL UNIT DESIGN


Full Adder Mirror (1 bit)

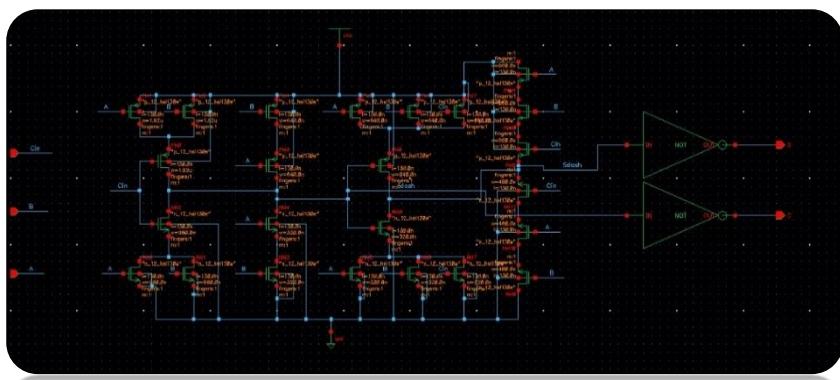

Schematic

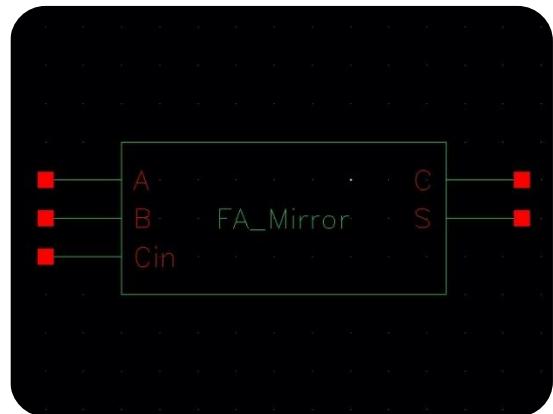


Symbol

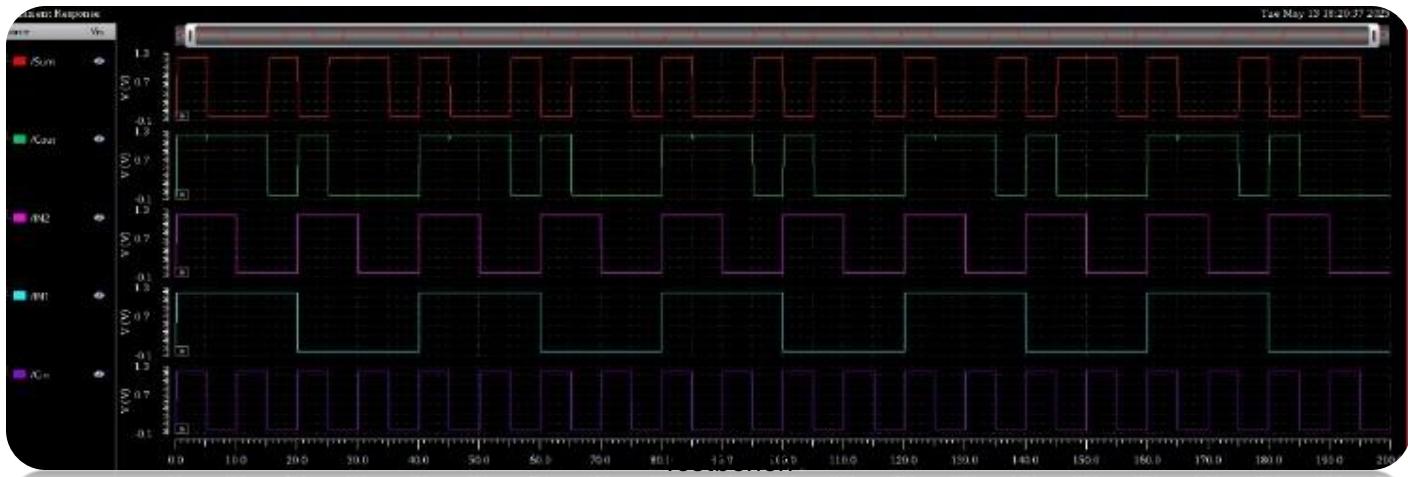


Testbench

ARITHMETIC AND LOGICAL UNIT DESIGN


Full Adder Mirror (4Bit):

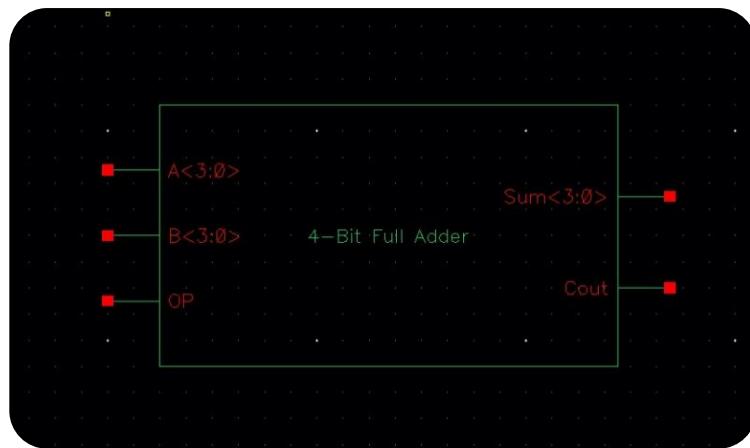

Symbol

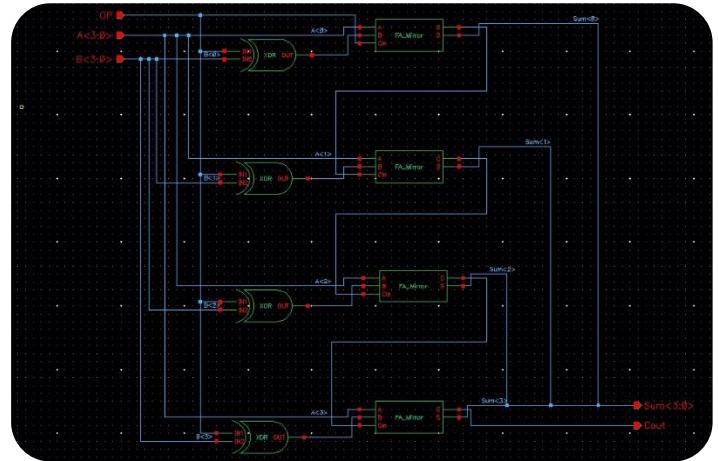


Schematic

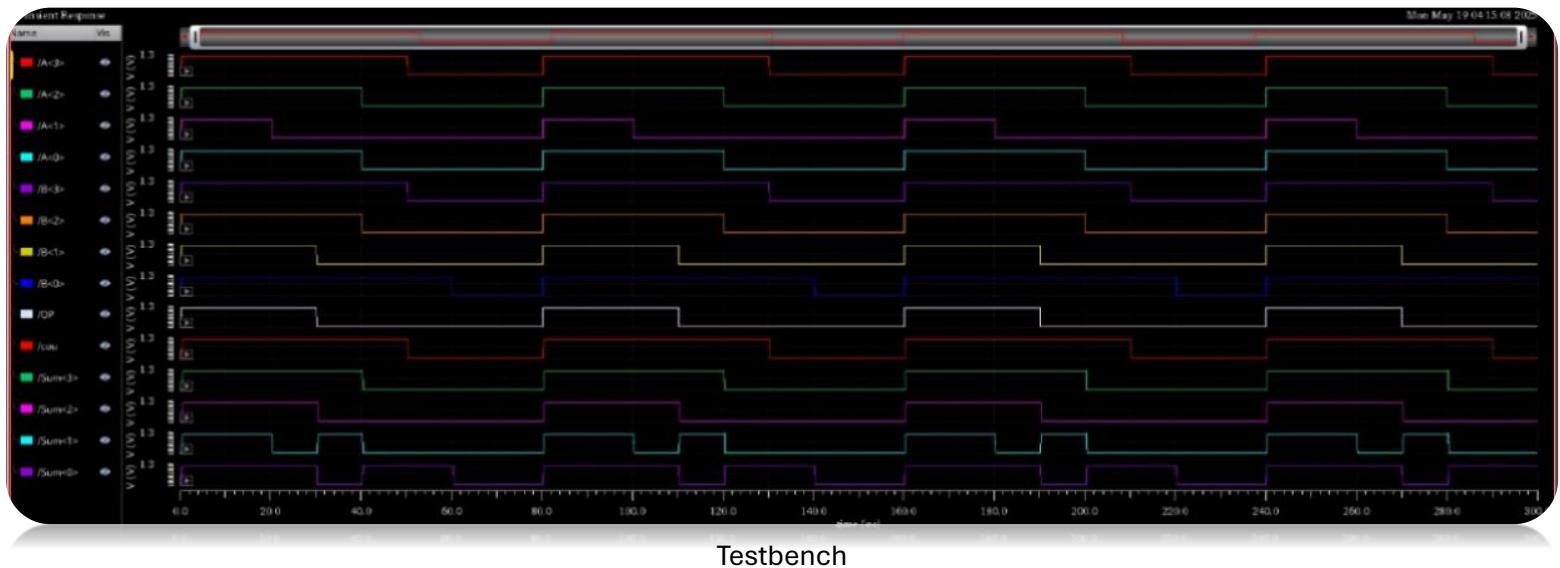


Testbench

ARITHMETIC AND LOGICAL UNIT DESIGN


FA Mirror vs FA Basic logic

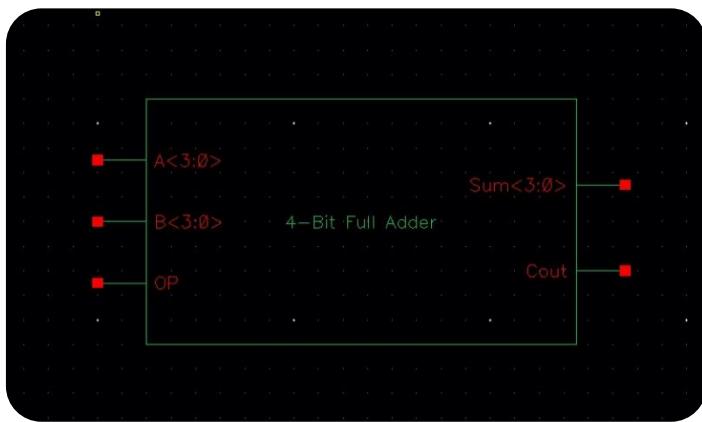

Symbol

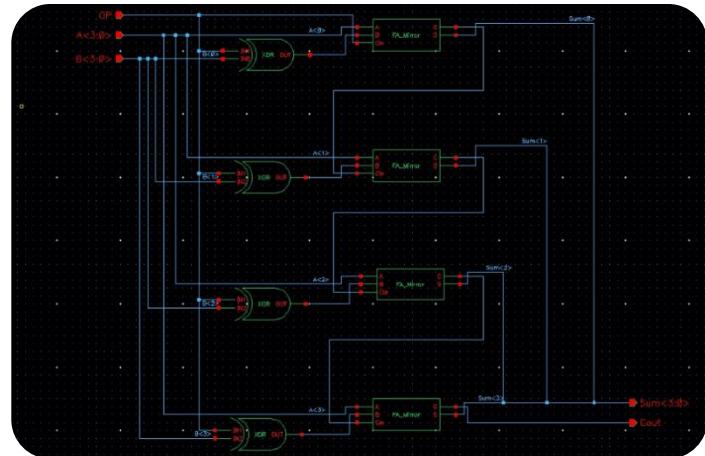

Schematic

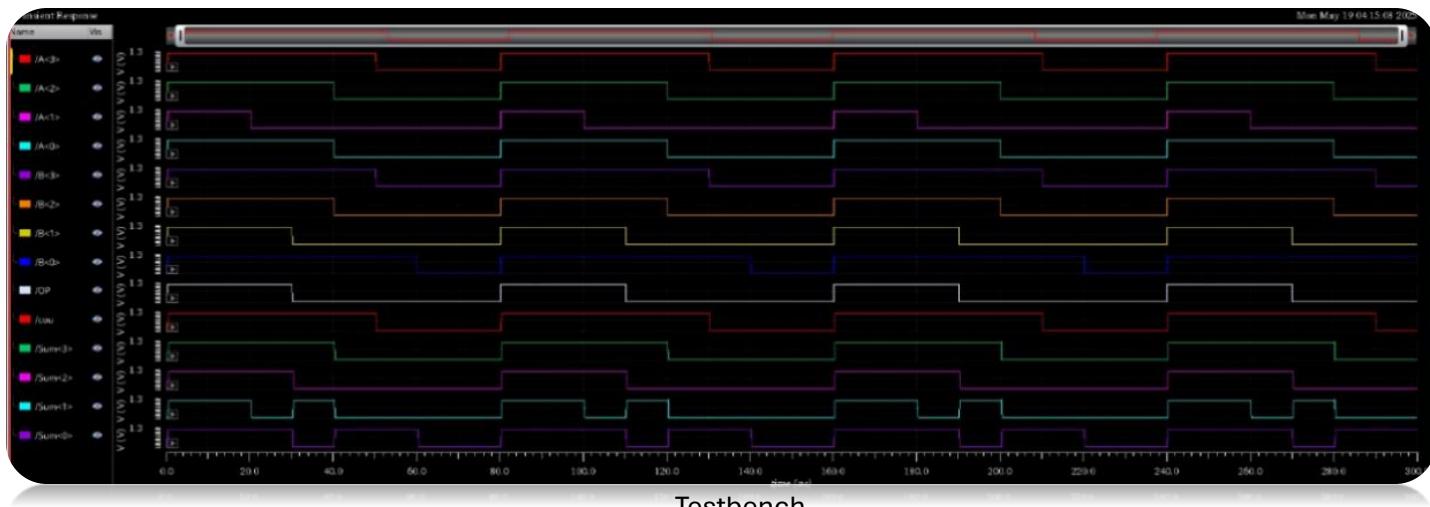

Testbench

Full Adder: Mirror Adder vs. Basic Logic

In the design of our Arithmetic and Logical Unit (ALU), we implemented and tested two types of full adders at the circuit level: the **Basic Logic Full Adder** and the **Mirror Adder**. The basic full adder is built using simple combinations of logic gates (AND, OR, XOR) directly derived from the Boolean expressions of sum and carry. While this approach is straightforward, it suffers from higher propagation delay due to longer logic paths and unbalanced signal flow.


To improve performance, we implemented the **Mirror Adder**, which is a more optimized CMOS design. It uses a symmetrical structure that ensures better signal balance and reduces the number of logic levels between input and output. We tested both designs by calculating and comparing their delay times. The **Mirror Adder showed significantly lower delay**, which translates to faster operation and better overall performance in the ALU. For this reason, we chose to integrate the Mirror Adder into our final ALU design.

In addition to the Basic Logic and Mirror full adders, we also implemented a **4-bit Carry Look-Ahead Adder (CLA)** at the circuit level. The CLA is designed to reduce the carry propagation delay by generating carry signals in parallel, rather than waiting for them to ripple through each stage. This architecture is known to provide significant speed improvements, especially for adders with large bit-widths such as 32 or 64 bits.

However, through our practical testing and delay time analysis, we observed that in the **4-bit configuration**, the CLA did **not outperform** the Basic Logic or Mirror adders. The added complexity of the carry generation logic introduces overhead that outweighs the benefits in such a small bit-width. Therefore, since our ALU is designed for 4-bit operations, we **chose not to use the CLA** in the final unit, as the **Mirror Adder provided better performance** in this specific case.

ARITHMETIC AND LOGICAL UNIT DESIGN


Carry Look Ahead 4 bit

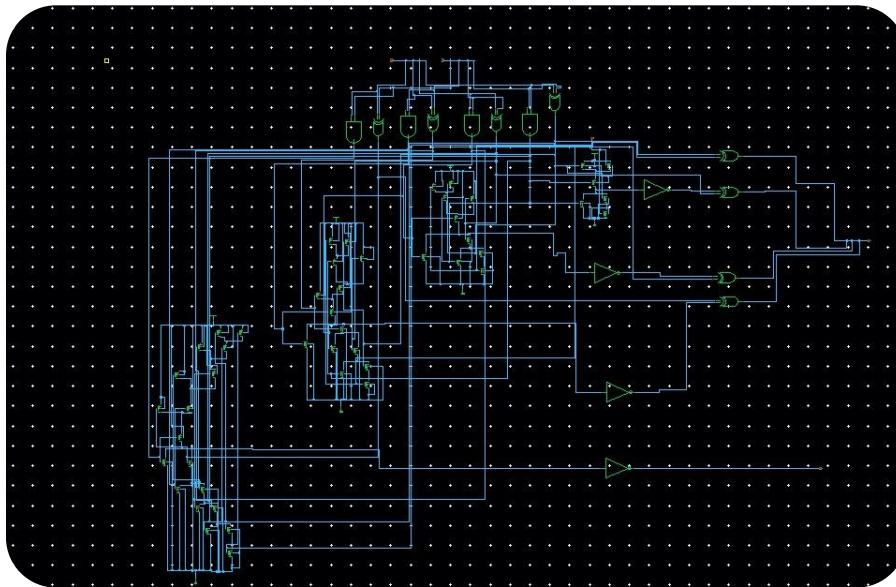

Schematic



Symbol

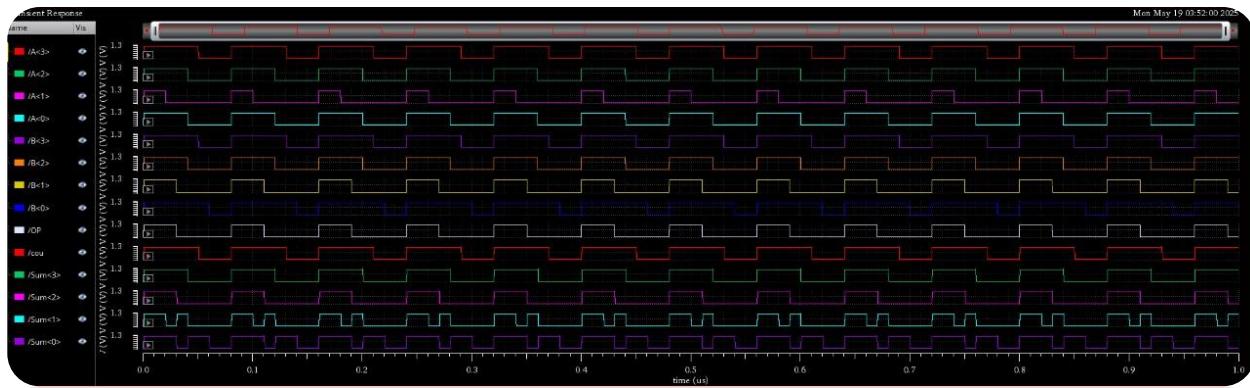

Why CLA Not suitable in the design

Although the **Carry Look-Ahead Adder (CLA)** is known for its ability to perform high-speed addition by reducing carry propagation delay, it was not suitable for our ALU design. Our unit is specifically designed for **4-bit operations**, where the carry delay is already minimal due to the small number of stages.


In practice, we implemented and tested a 4-bit CLA at the circuit level to compare its performance with the Basic and Mirror adders. Our **simulation results showed that the CLA was actually slower** than both, mainly due to the **increased complexity and gate overhead** required to compute the generate and propagate signals. These extra logic levels introduce delay that cancels out the advantage of parallel carry generation in such a small bit-width.

Furthermore, the CLA requires **more transistors and layout area**, which is not ideal for a compact 4-bit ALU. CLA's performance advantage becomes noticeable in **32-bit or 64-bit systems**, where ripple carry delay is significant—but in our case, it adds unnecessary complexity without any speed benefit.


Therefore, we concluded that the **CLA is not suitable for a 4-bit ALU**, and instead selected the **Mirror Adder** for its better performance and lower delay in this context.

ARITHMETIC AND LOGICAL UNIT DESIGN


Full Adder (4 bit)

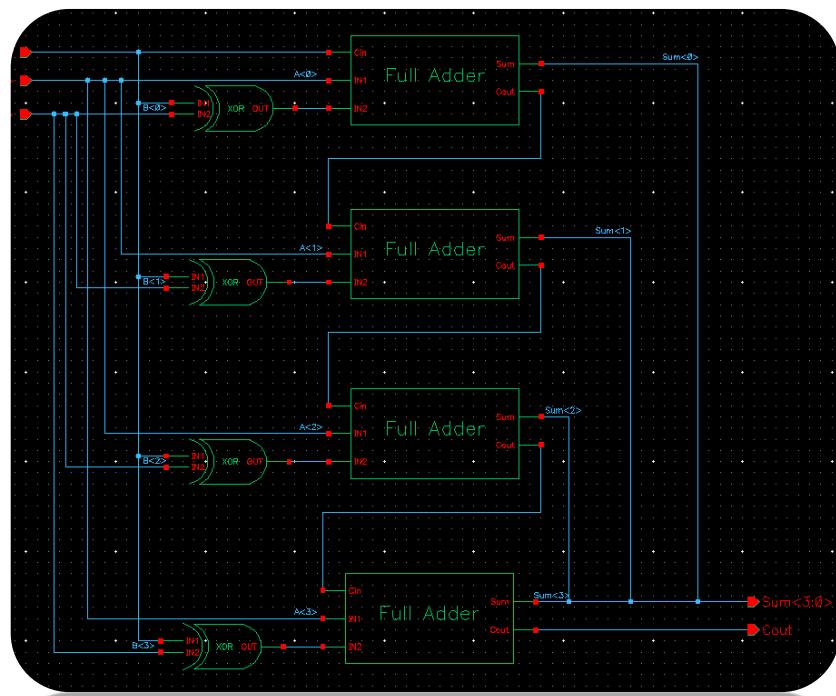

Schematic

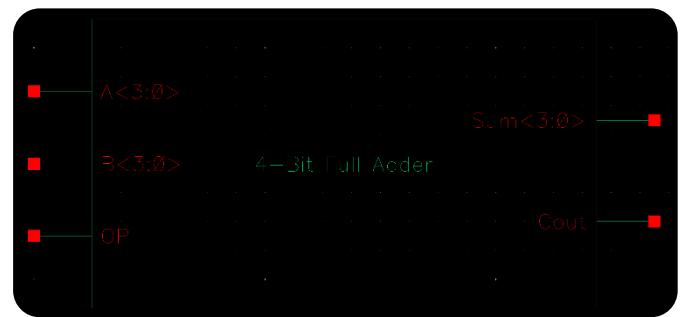

Symbol

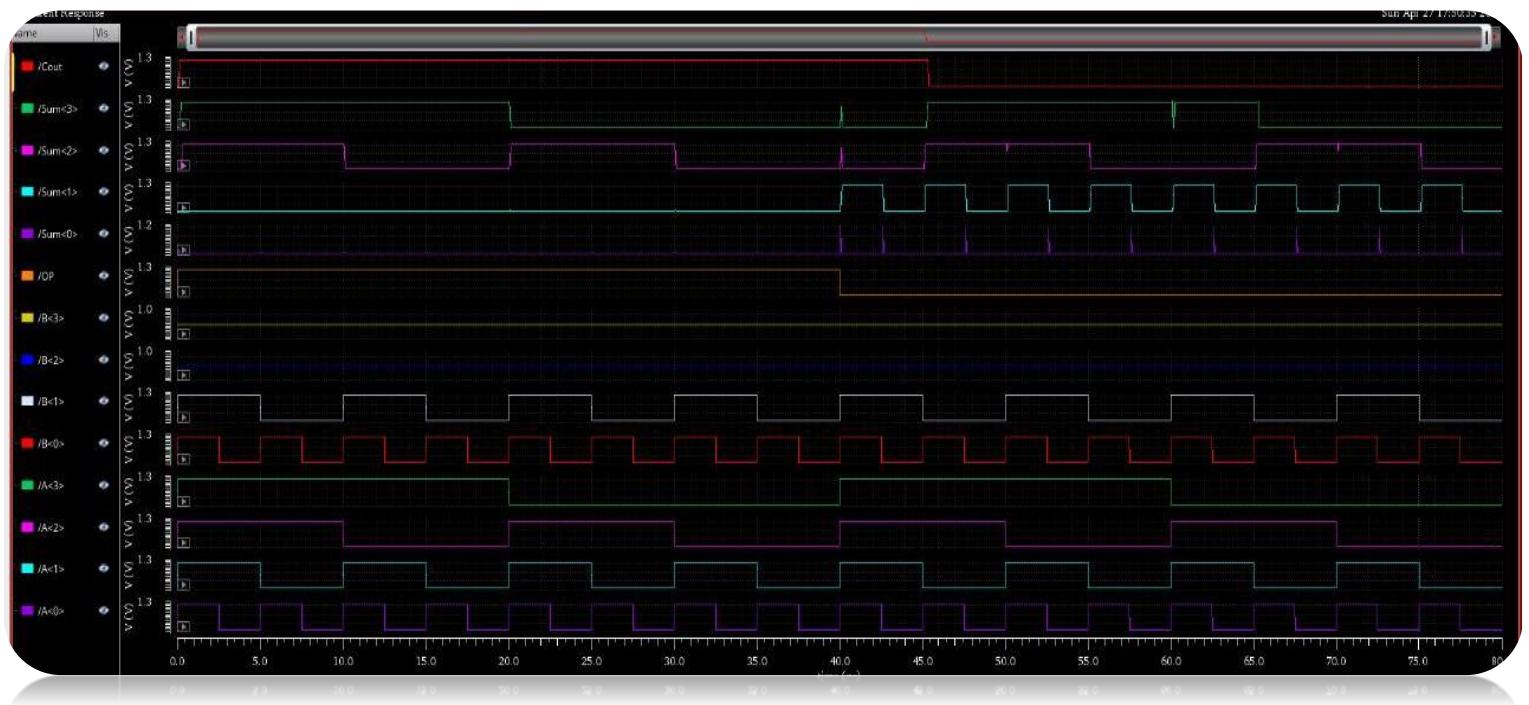

Testbench

Why use Full Adder with mux instead of Subtractor

In our ALU design, we initially implemented a dedicated **subtractor circuit**. However, after analysis and testing, we decided **not to use the separate subtractor** in the final design. Instead, we used a **Full Adder combined with a multiplexer (MUX)** to perform both addition and subtraction using the same hardware.

This approach is based on the **2's complement method** for subtraction, where $A - B$ is computed as $A + (\sim B + 1)$. By inverting the second operand (B) and adding 1 through the carry-in input of the adder, we can perform subtraction using the same full adder used for addition. A **MUX** is used to select whether the second input should be B (for addition) or $\sim B$ (for subtraction), and whether the carry-in should be 0 or 1.


The reasons for using this method are:

- **Hardware Efficiency:** Reusing the same adder circuit for both operations reduces the total number of gates and transistors.
- **Simpler Design:** Fewer separate blocks mean a more compact and manageable circuit.
- **Faster Operation:** Using a well-optimized full adder (like the Mirror Adder) with a small MUX introduces less delay compared to a dedicated subtractor path.
- **Flexibility:** The MUX-controlled design allows for easy switching between addition and subtraction through a control signal.

Therefore, to achieve a more **efficient, flexible, and faster design**, we chose to eliminate the separate subtractor and implement subtraction through a **Full Adder + MUX configuration** in our 4-bit ALU.

ARITHMETIC AND LOGICAL UNIT DESIGN


Half Adder

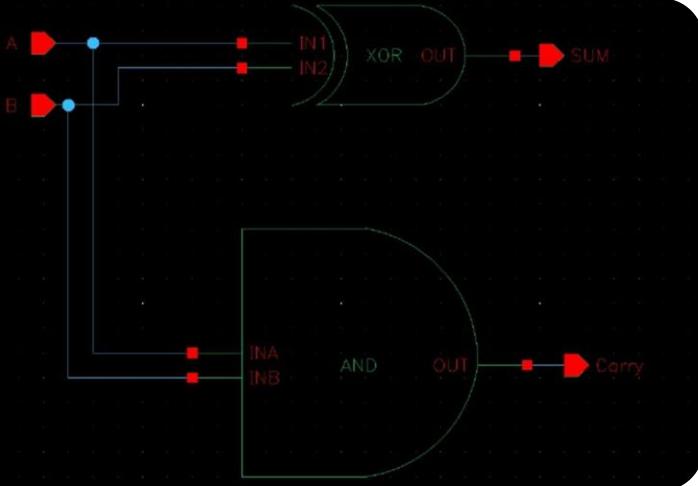


Schematic



Symbol

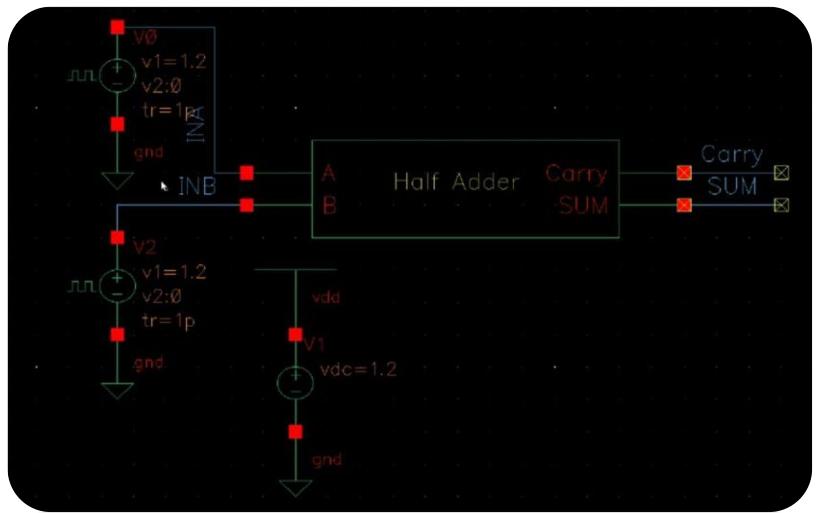

Testbench

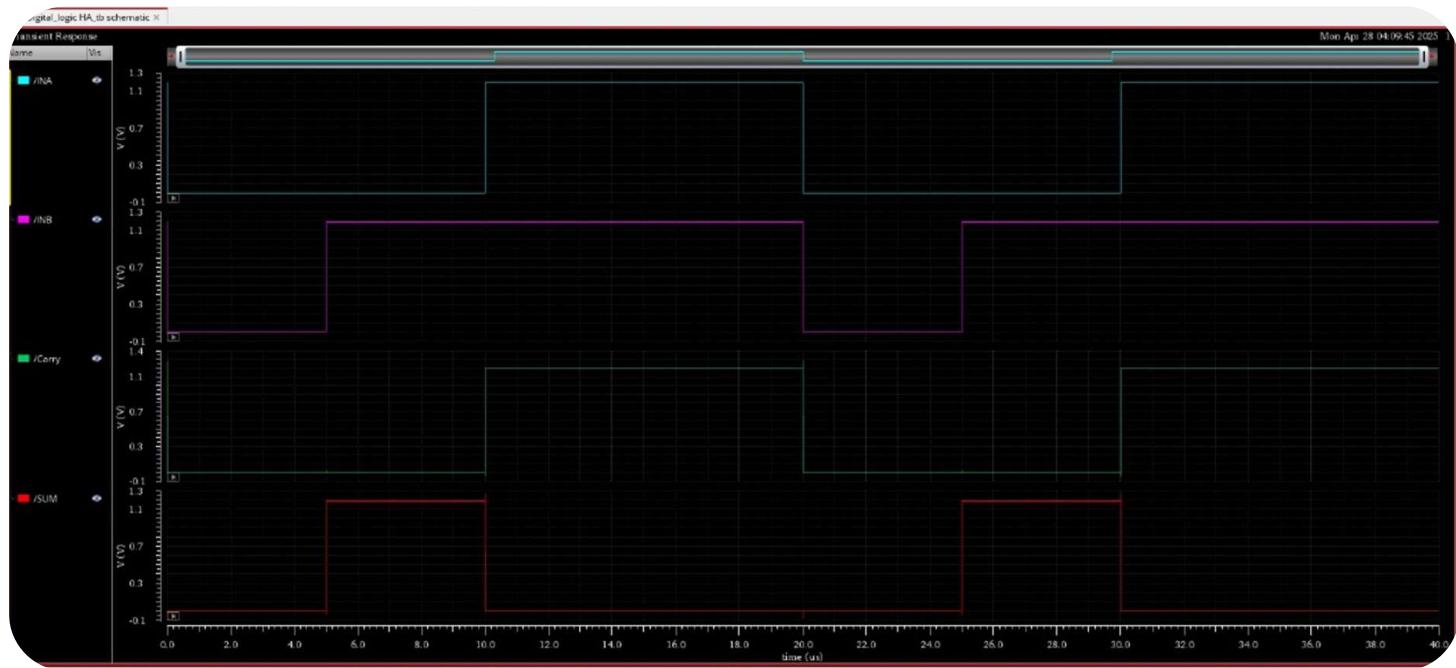

Waveform

Comparison between Multiplier Architecture

In the process of designing the multiplication unit for our 4-bit ALU, we explored and analyzed four different multiplier architectures:

1. **Array Multiplier**
2. **Wallace Tree Multiplier**
3. **Dadda Tree Multiplier**
4. **Booth Multiplier**

Each architecture offers unique trade-offs in terms of **speed, complexity, area**, and **ease of implementation**. Below is a detailed comparison:

1. Array Multiplier

The array multiplier is a straightforward structure that uses a regular grid of **half adders and full adders** to compute partial products and sum them. It is easy to design and implement, especially for small bit-widths like 4-bit. However, it has a **longer delay** compared to tree-based architecture due to its **ripple carry-like structure**.

2. Wallace Tree Multiplier

The Wallace Tree multiplier uses a **reduction tree** to compress partial products as quickly as possible using carry-save adders. It reduces the number of addition stages, resulting in **faster performance** compared to the array multiplier, but it is **more complex** to implement and wire.

3. Dadda Tree Multiplier

The Dadda multiplier is similar to the Wallace tree but uses a slightly different strategy to minimize the number of adders used, making it more **area-efficient** while maintaining high speed. It is still complex to design and better suited for larger bit-widths.

Multiplier Architecture Comparison Table


Feature / Architecture	Array Multiplier	Wallace Tree	Dadda Tree
Speed	Moderate	Fast	Fast
Complexity	Low	High	High
Area	Moderate	High	Lower than Wallace
Ease of Implementation	Easy	Hard	Hard
Best for Bit-width	Small (4–8 bits)	Large (16–64+)	Large (16–64+)

Conclusion

After analyzing all architectures and simulating their performance, we chose to implement the **Array Multiplier** for our 4-bit ALU. The **speed advantage of tree-based multipliers** like Wallace and Dadda is **not significant at 4-bit level**, and their complexity does not justify the small gain in delay. The **Array Multiplier** provides a **simpler and more practical solution** for small bit-width operations, making it ideal for our design goals.

ARITHMETIC AND LOGICAL UNIT DESIGN


Multiplier (unsigned)

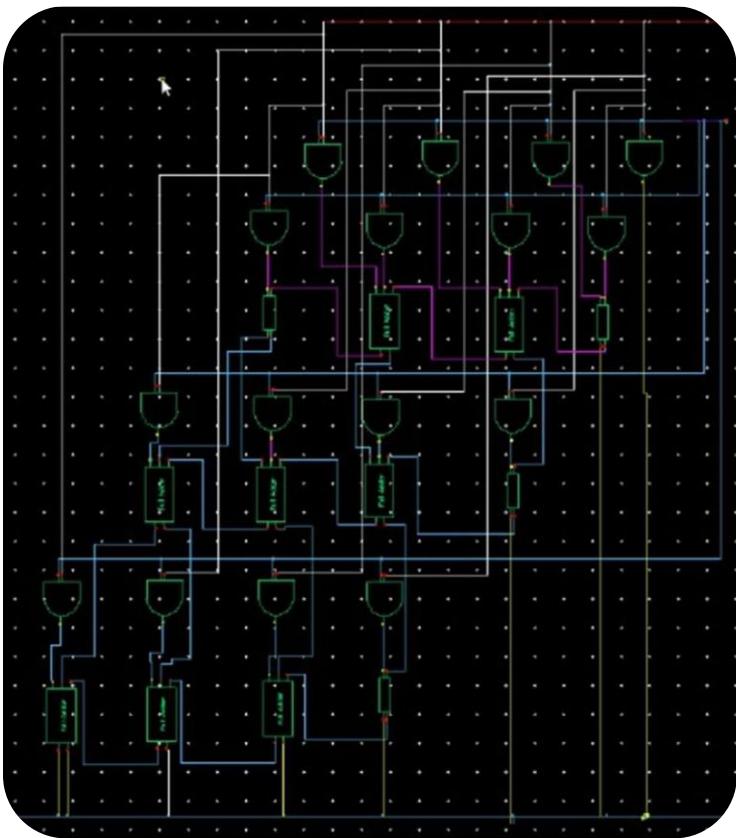


Schematic



Symbol

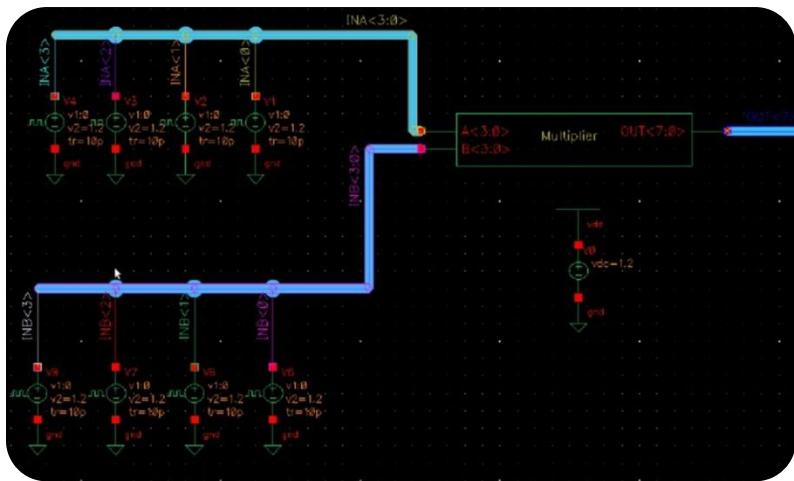


Testbench

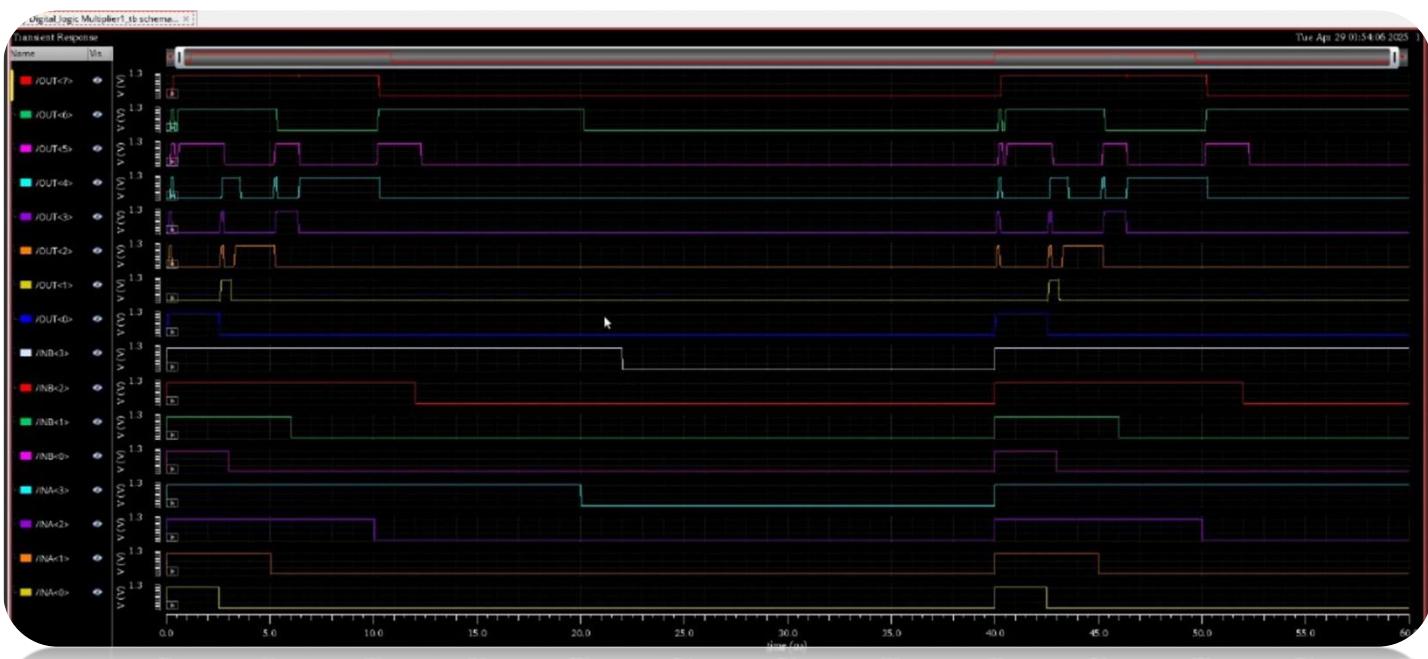

Waveform

ARITHMETIC AND LOGICAL UNIT DESIGN


Multiplier (Signed)

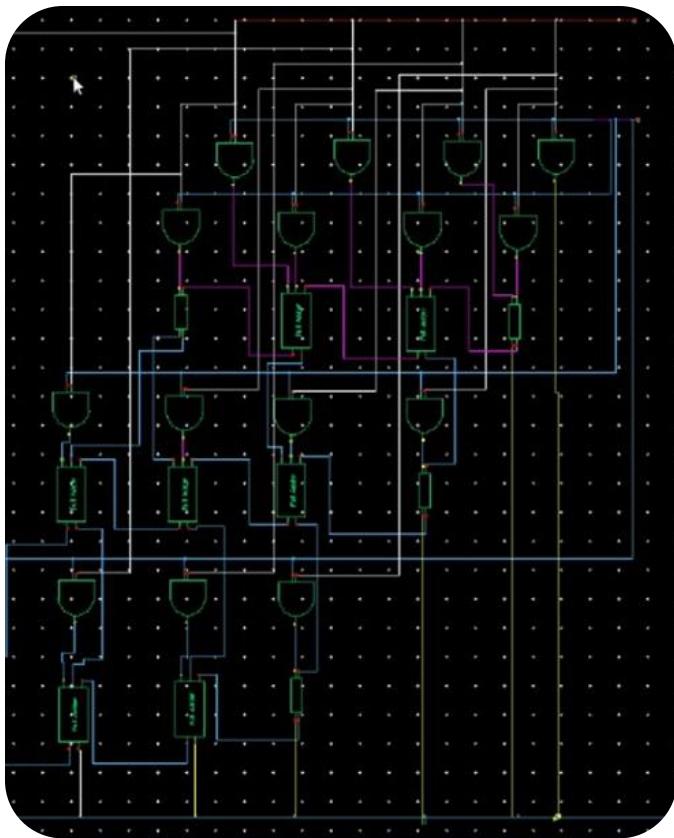

Schematic



Symbol

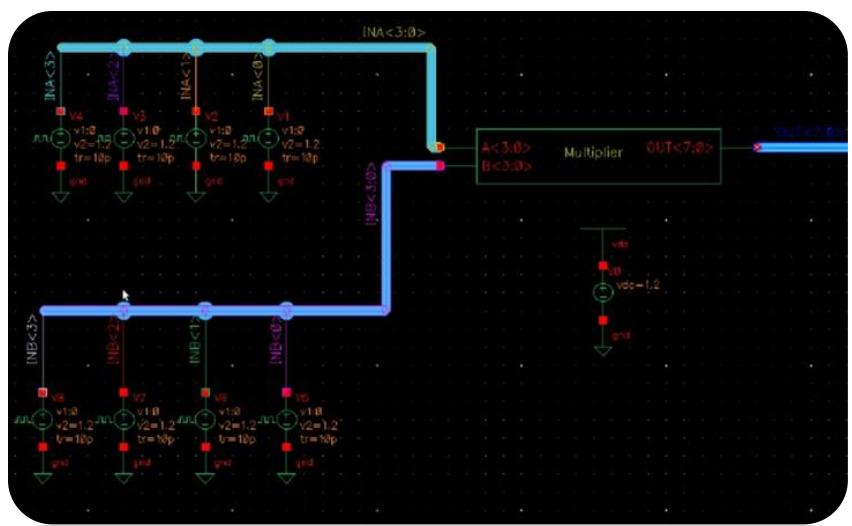




Testbench



Waveform


ARITHMETIC AND LOGICAL UNIT DESIGN

Arithmetic unit

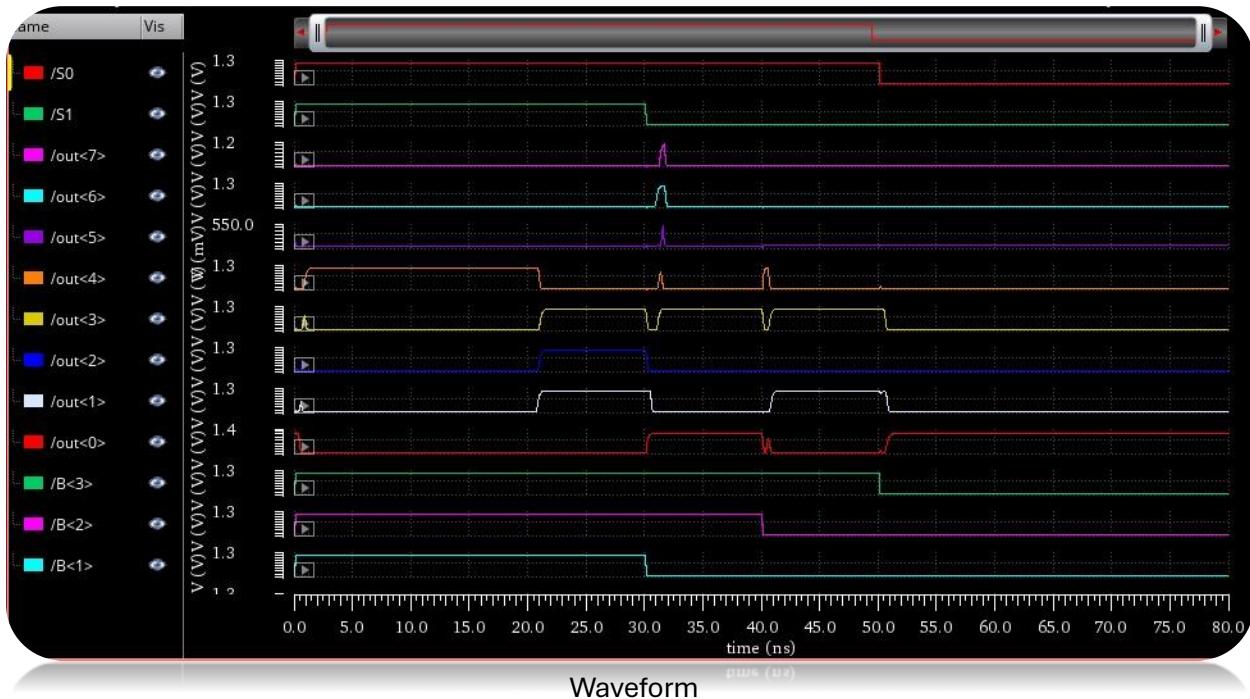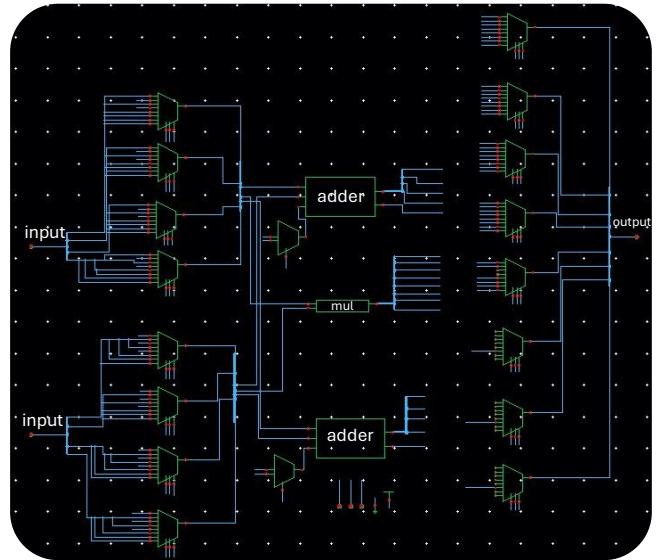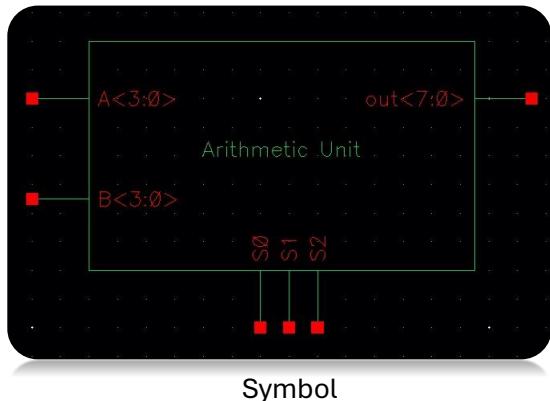


ARITHMETIC AND LOGICAL UNIT DESIGN

ALU

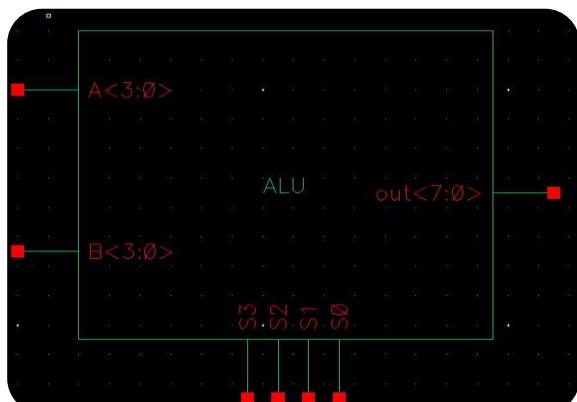


Symbol

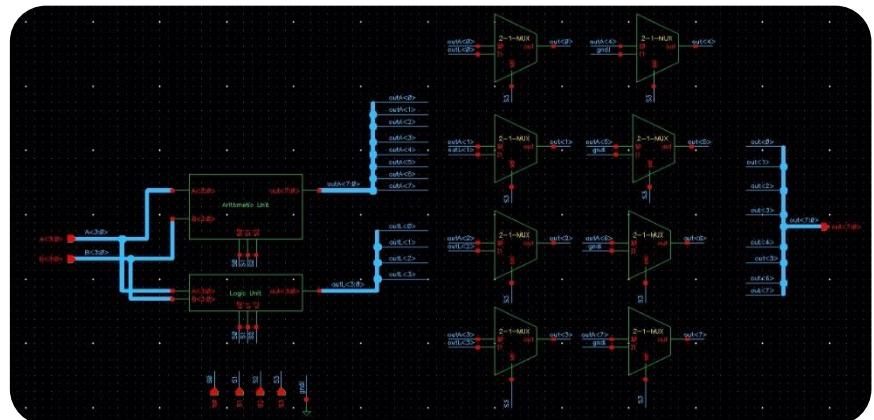

Schematic

ARITHMETIC AND LOGICAL UNIT DESIGN


Register (4bit)

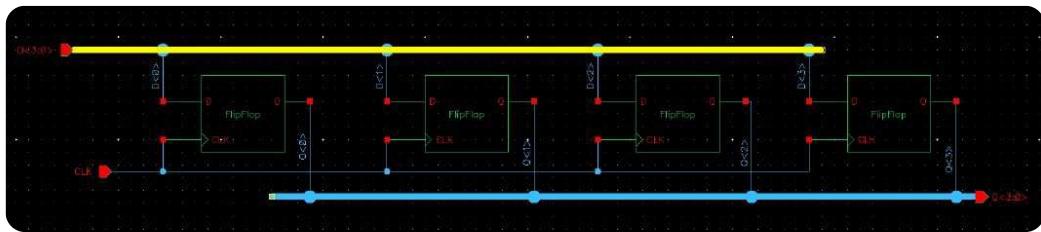


Schematic



Symbol

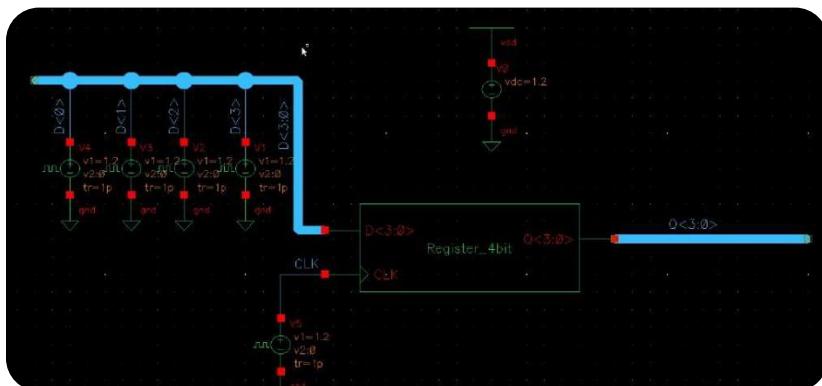


Testbench

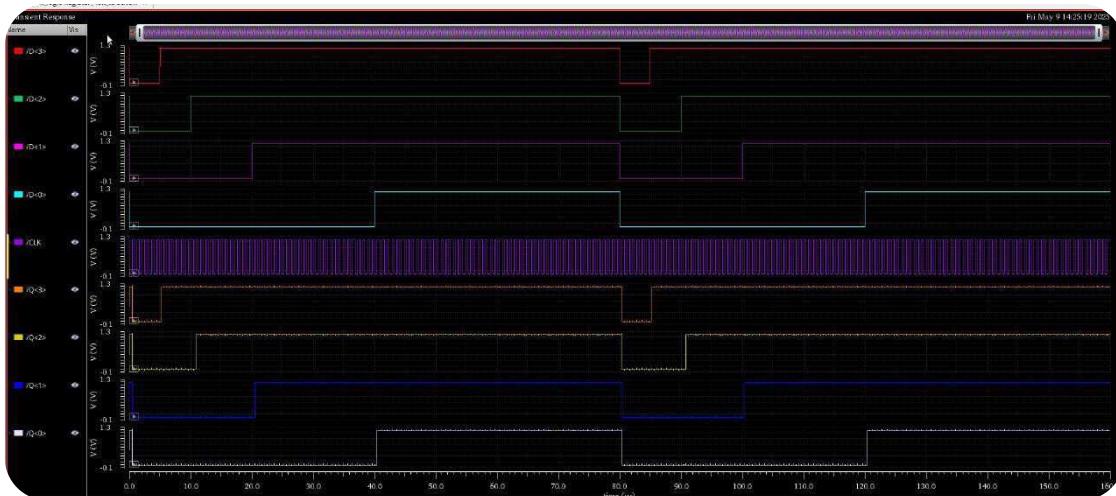


Waveform

ARITHMETIC AND LOGICAL UNIT DESIGN


Register (8 bit)

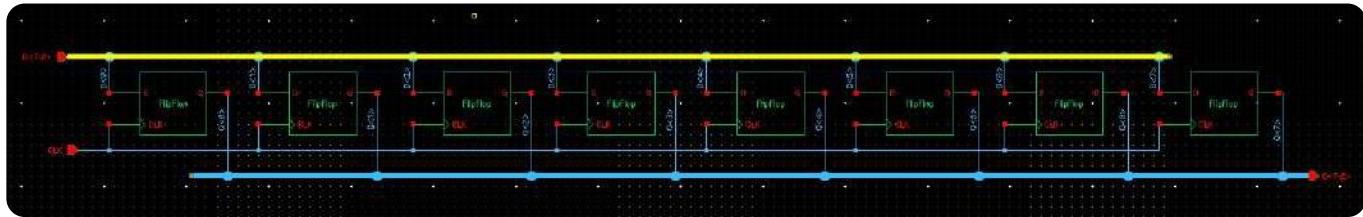


Schematic

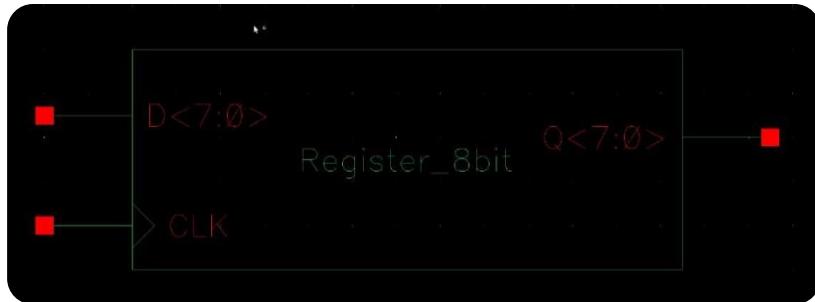

Symbol

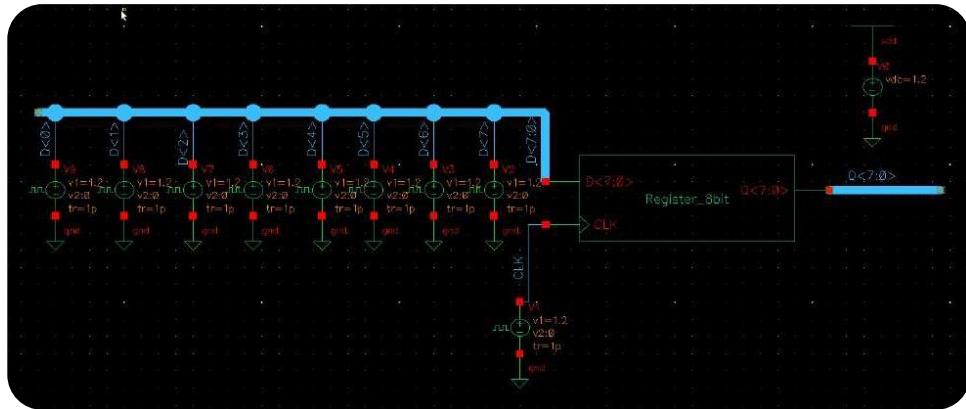


Testbench

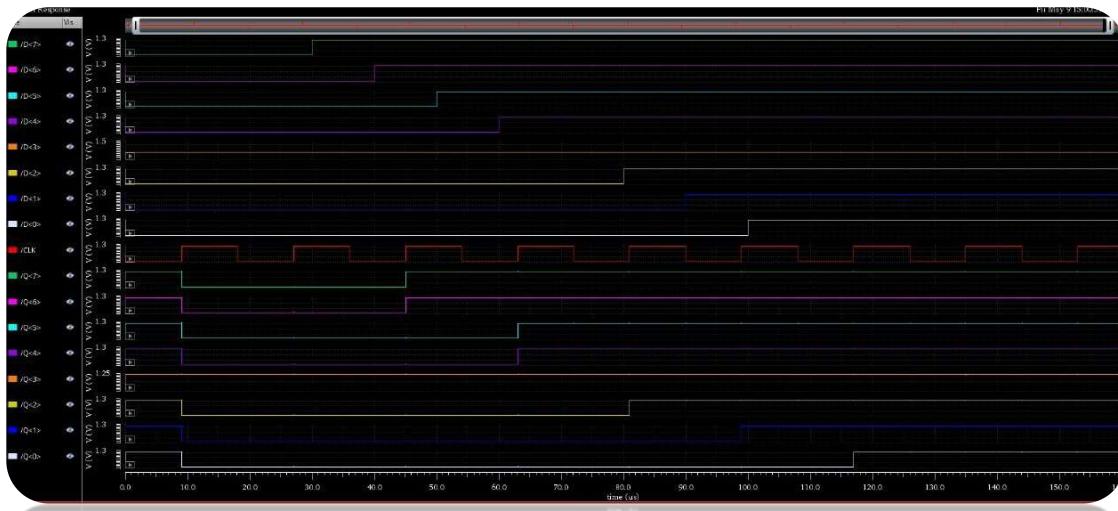

Waveform

Capacitor


Circuit

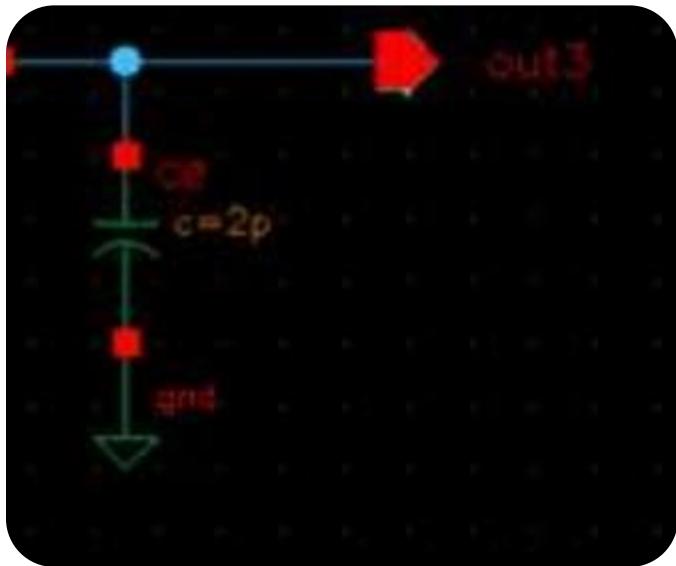


Simulation: Operations Waveforms

Arithmetic unit

Increment a

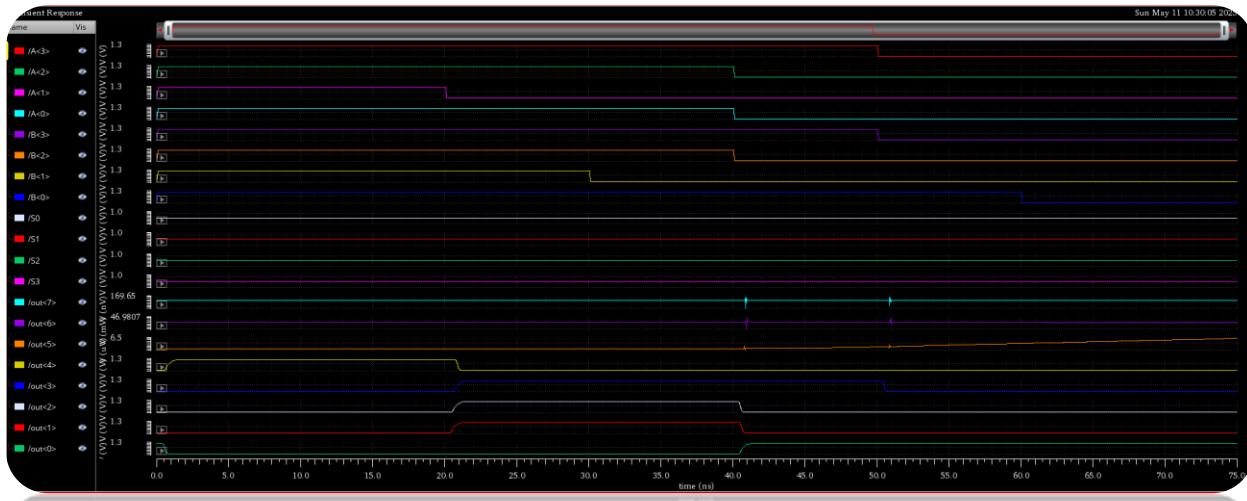


Increment b

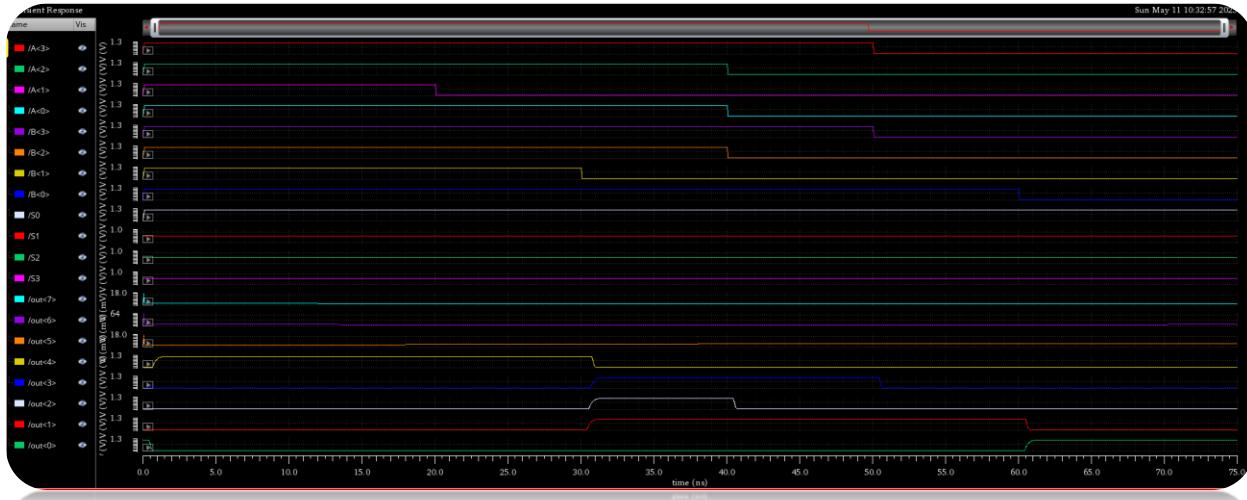


ARITHMETIC AND LOGICAL UNIT DESIGN


Transfer a

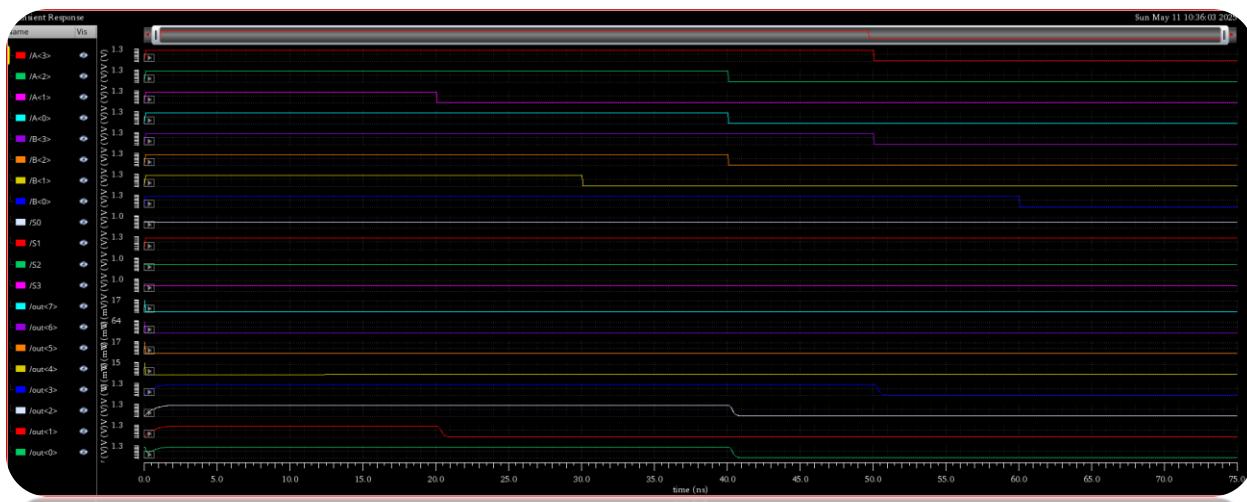

Transfer b

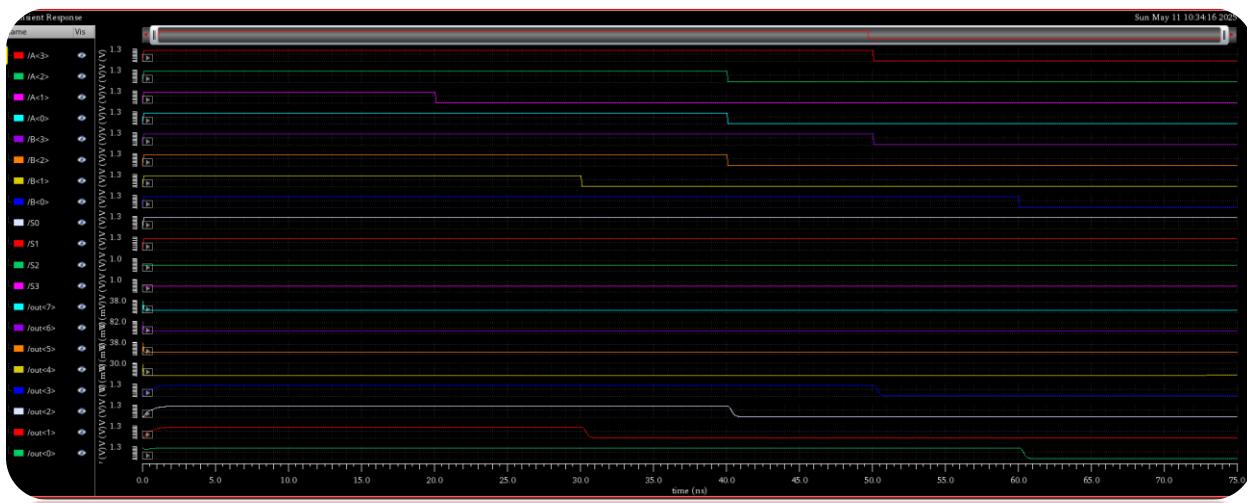


Decrement a

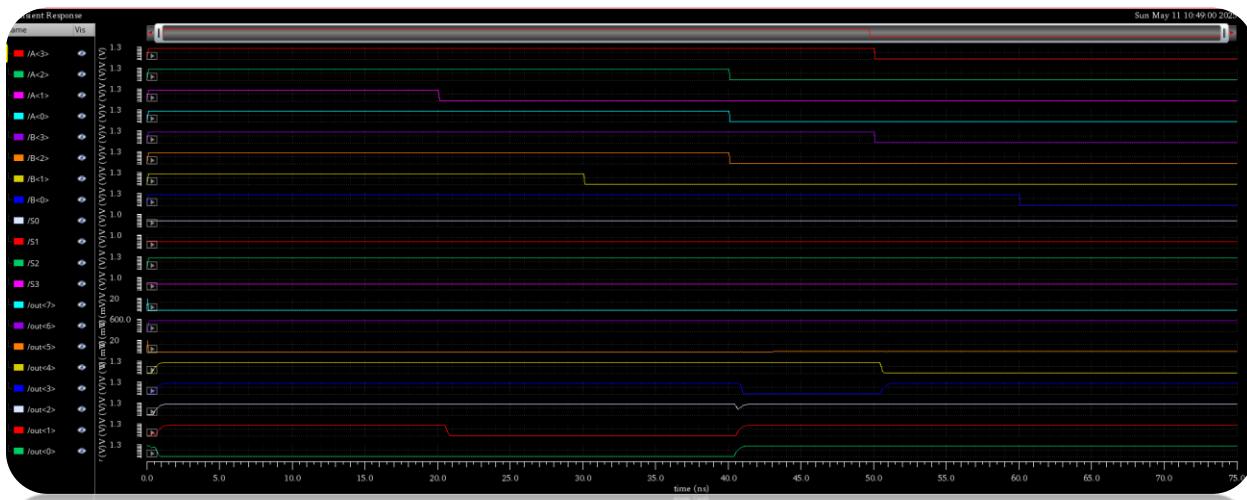


ARITHMETIC AND LOGICAL UNIT DESIGN


Multiply a and b

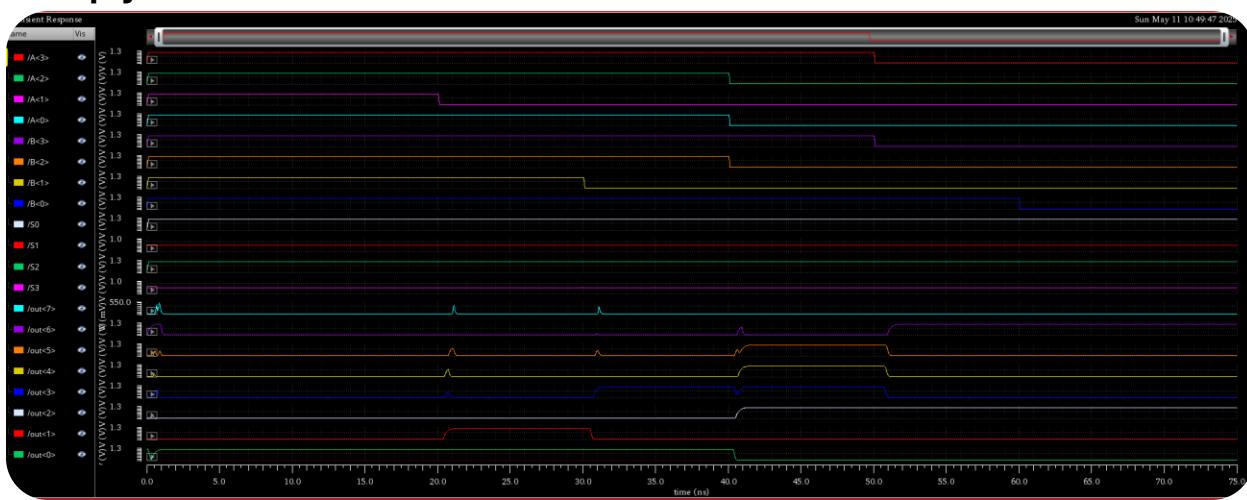

Add a and b

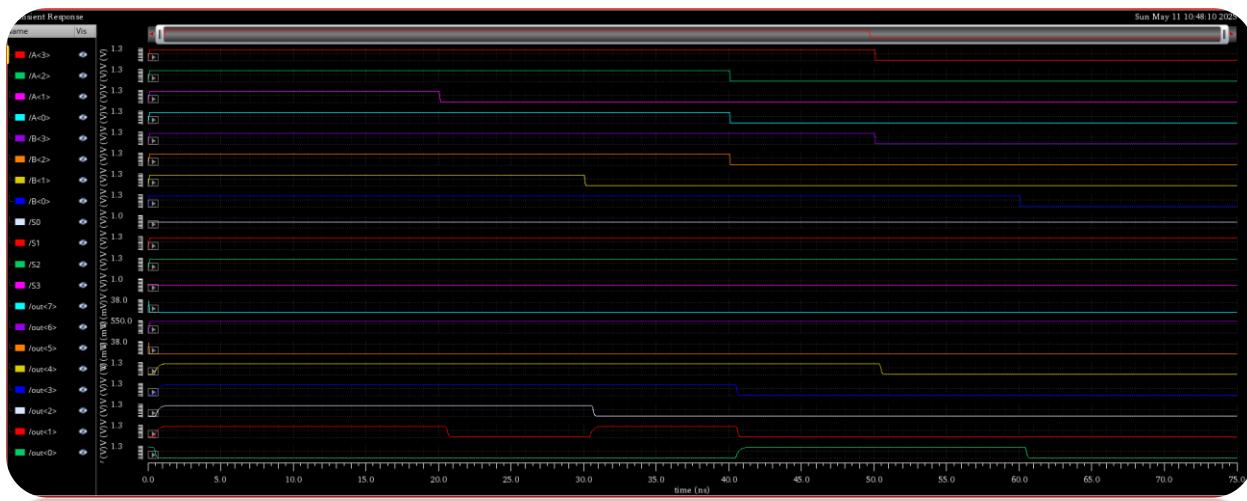


Subtract a and b

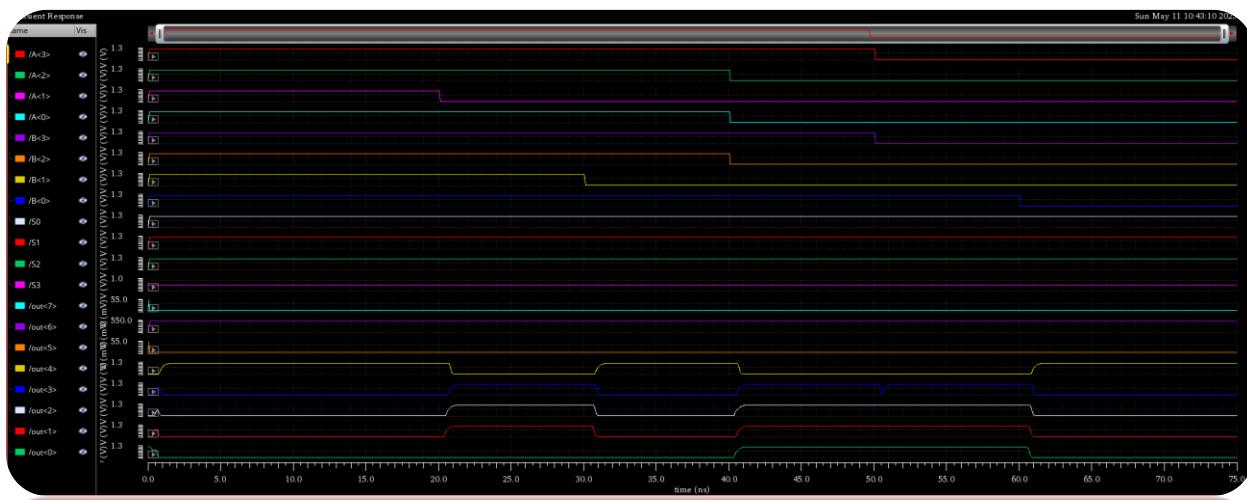


Logical unit

Complement a

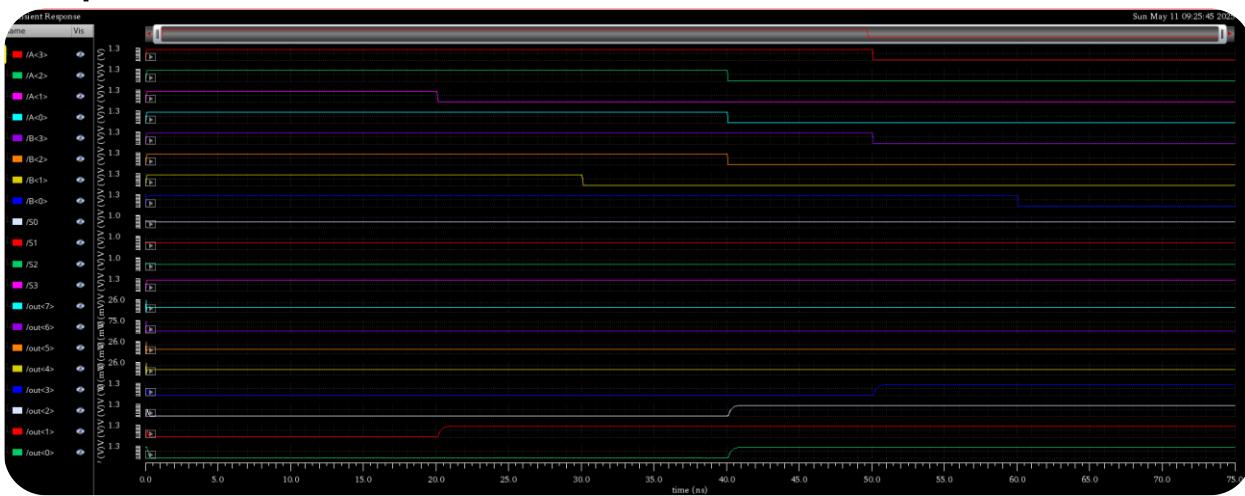


Complement b

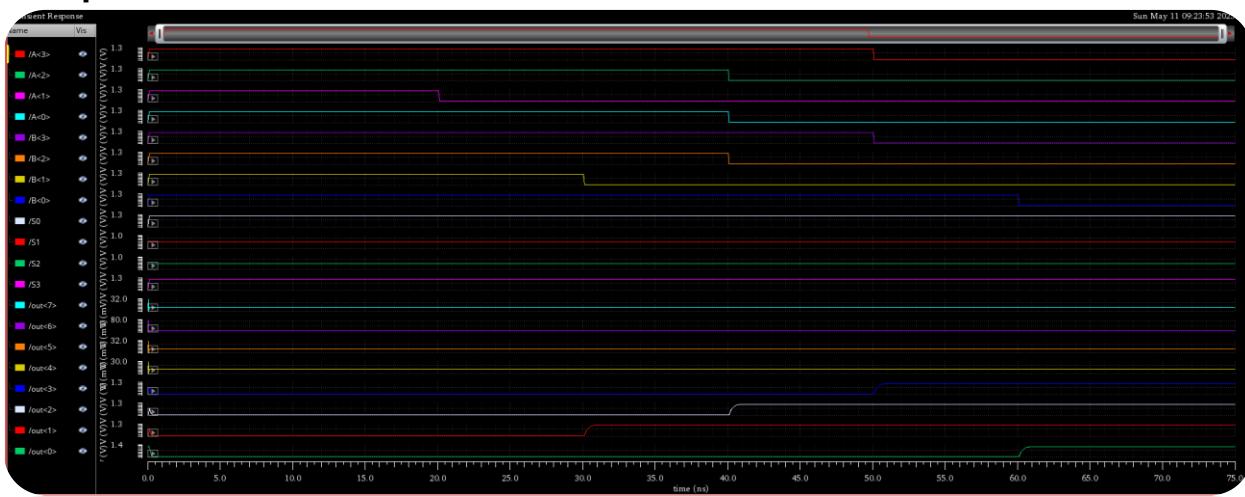


ARITHMETIC AND LOGICAL UNIT DESIGN


AND

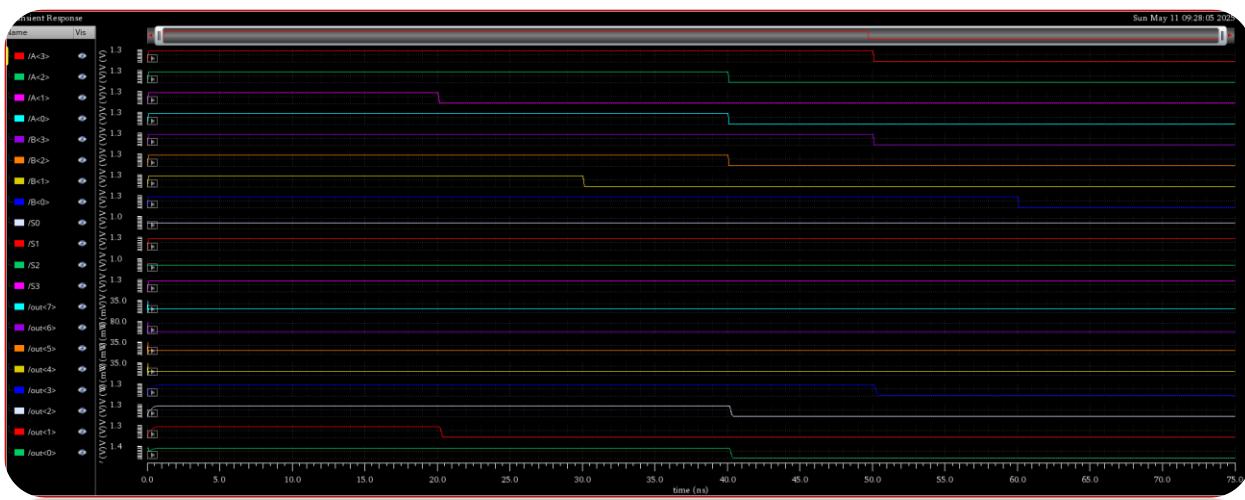

OR

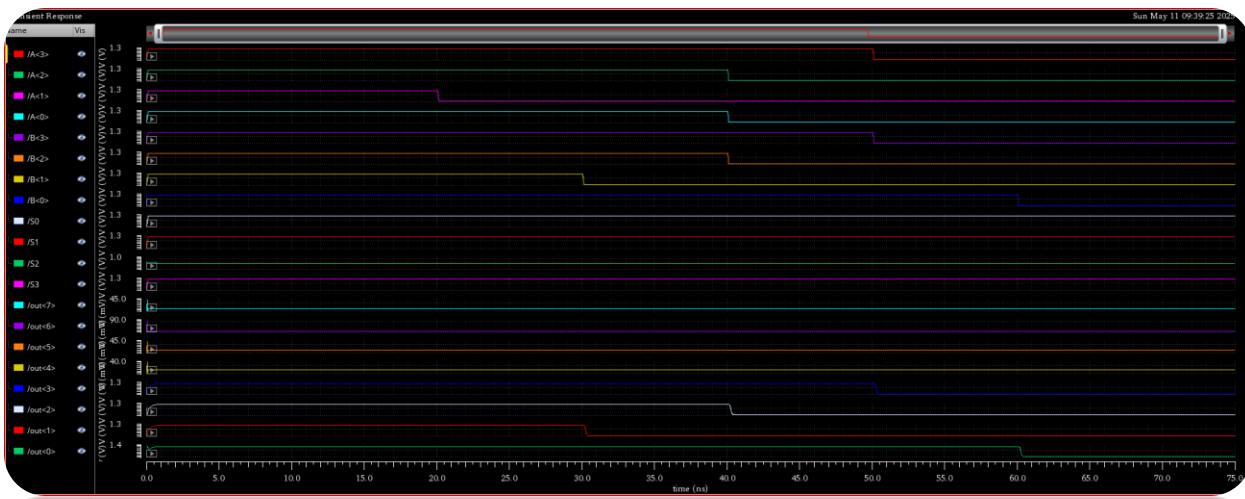


XOR

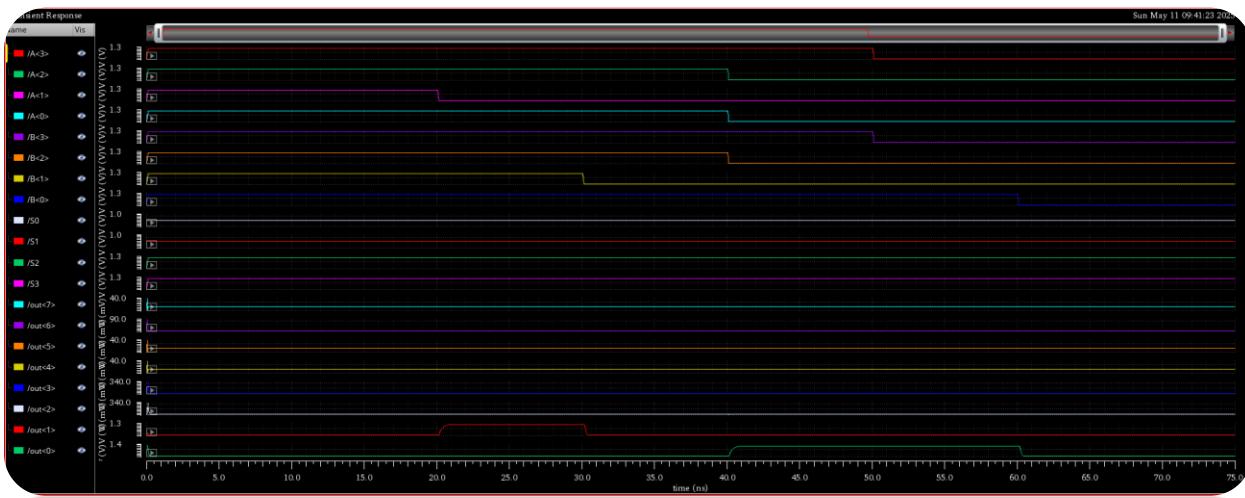


ARITHMETIC AND LOGICAL UNIT DESIGN


XNOR

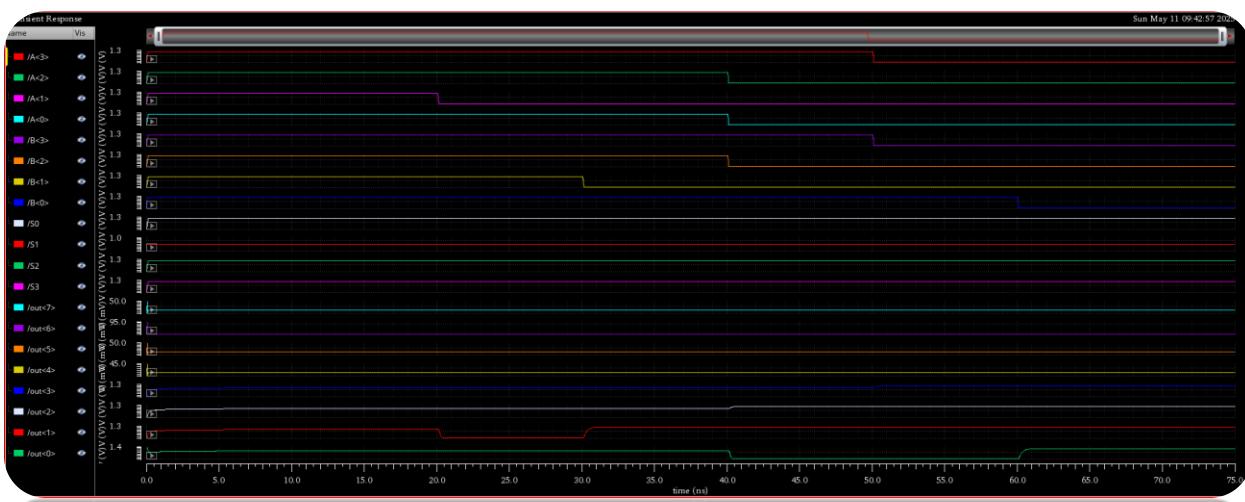

NAND

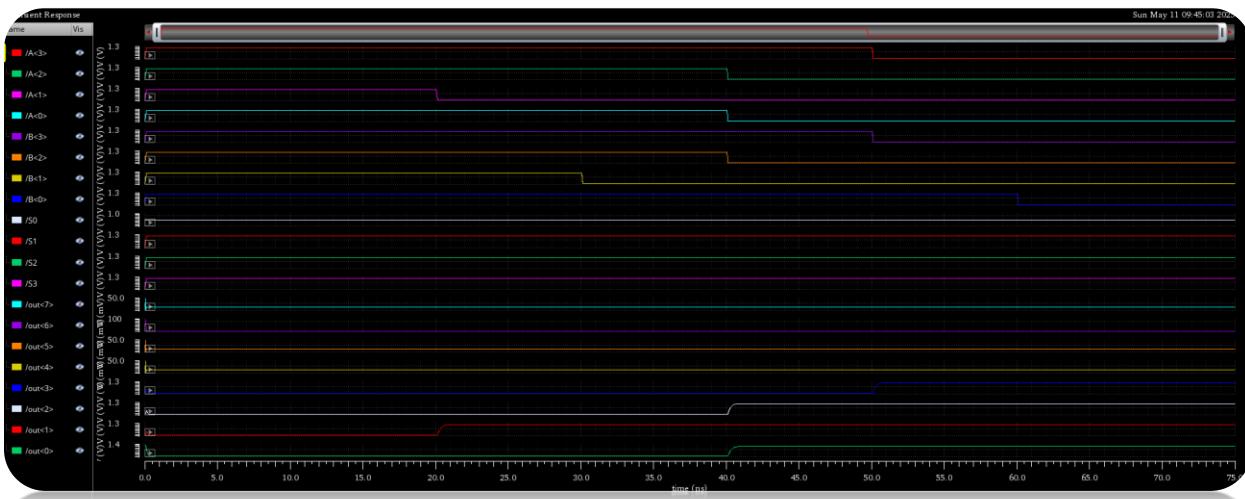

NOR

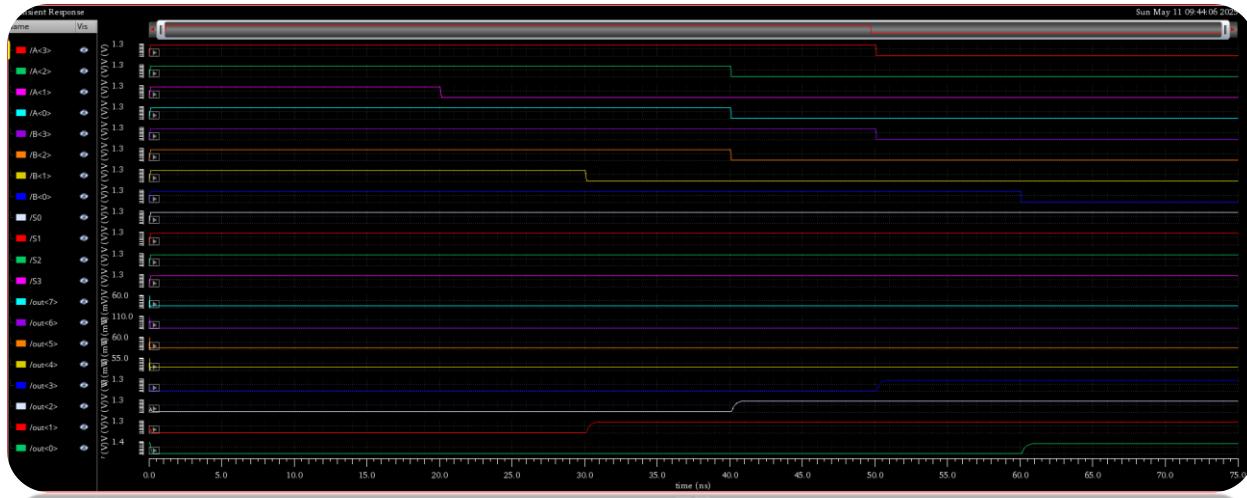


Simulation: Transient simulations with the flip-flops at max f(340 MHz)

Arithmetic unit

Increment a




Increment b

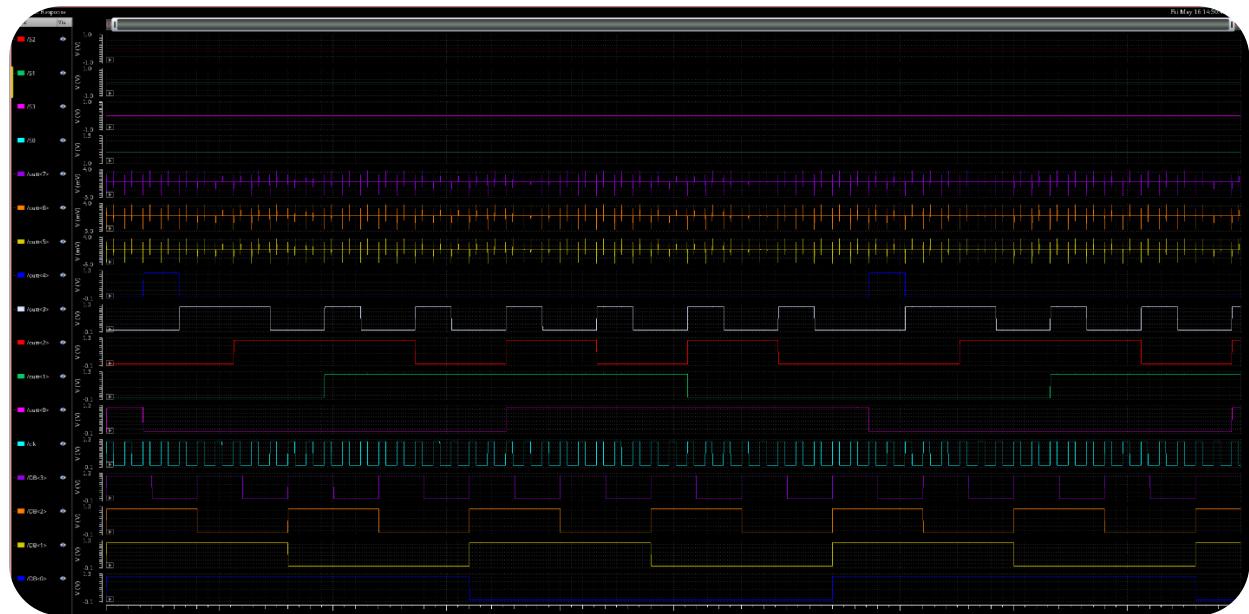

ARITHMETIC AND LOGICAL UNIT DESIGN

Transfer a

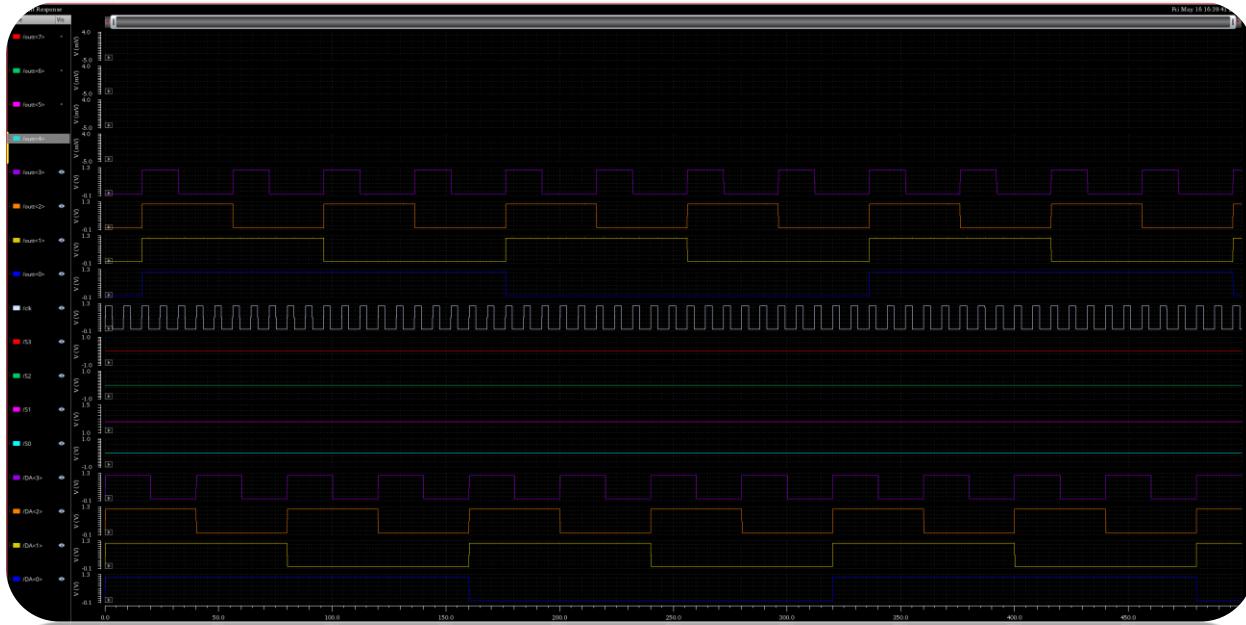


Transfer b



ARITHMETIC AND LOGICAL UNIT DESIGN

Decrement a

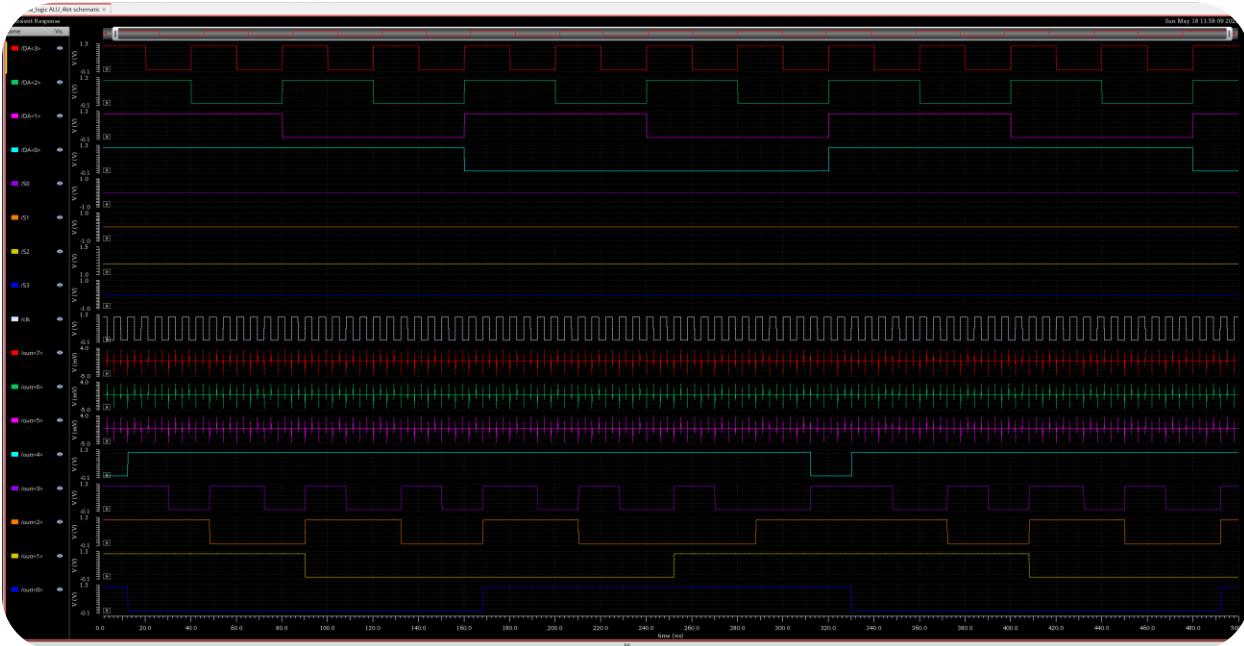


Multiply a and b




ARITHMETIC AND LOGICAL UNIT DESIGN

Add a and b

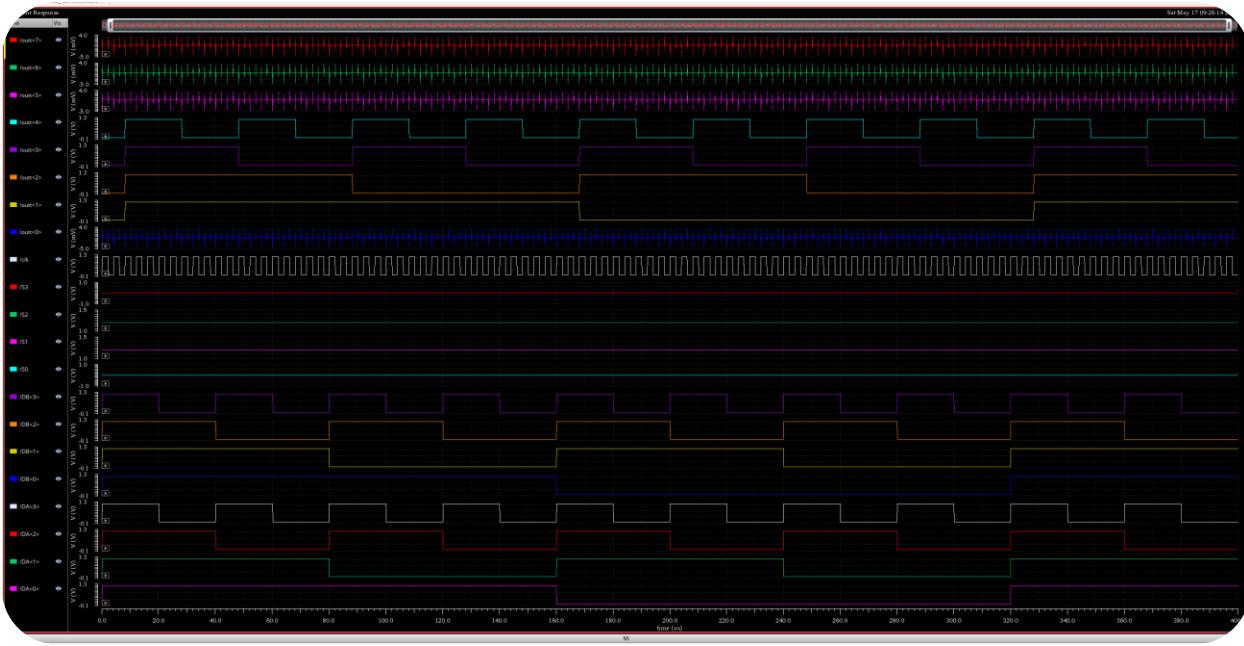


Subtract a and b

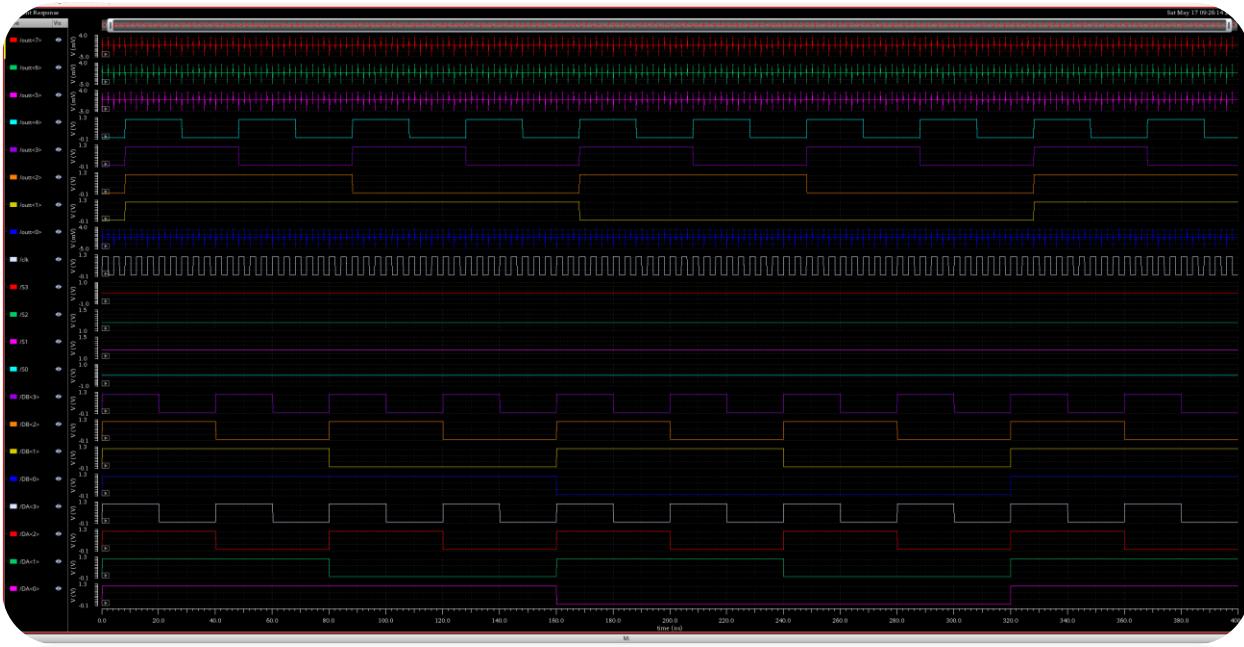


Logical unit

Complement a

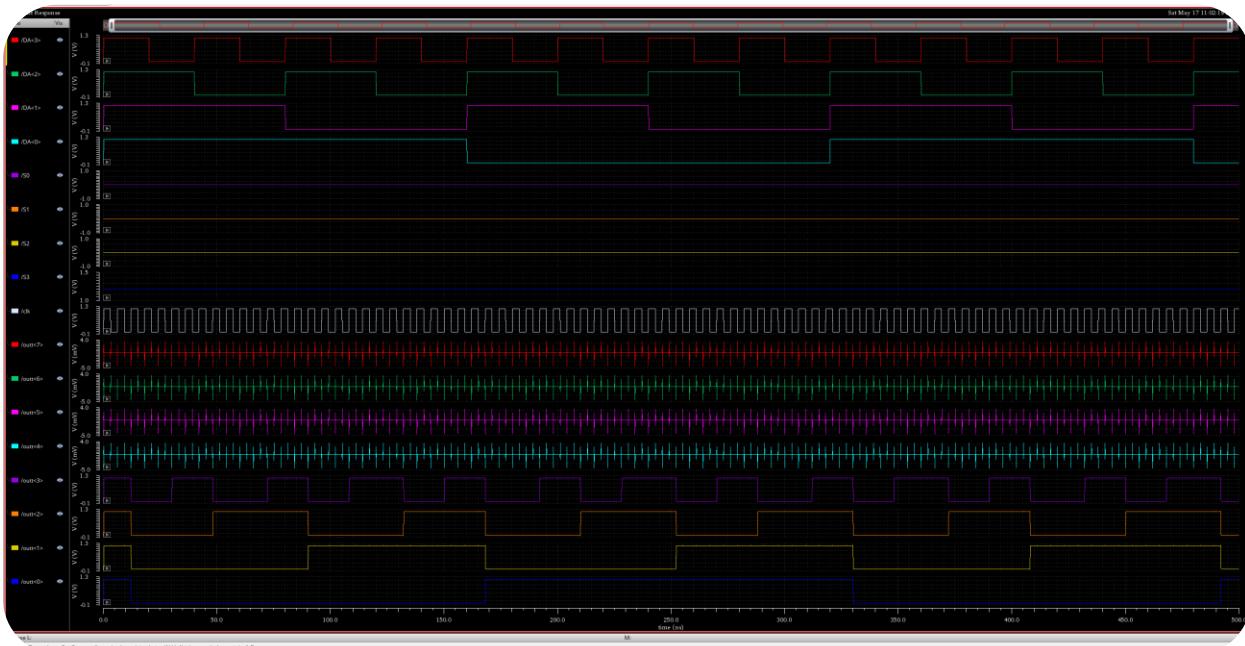

Complement b

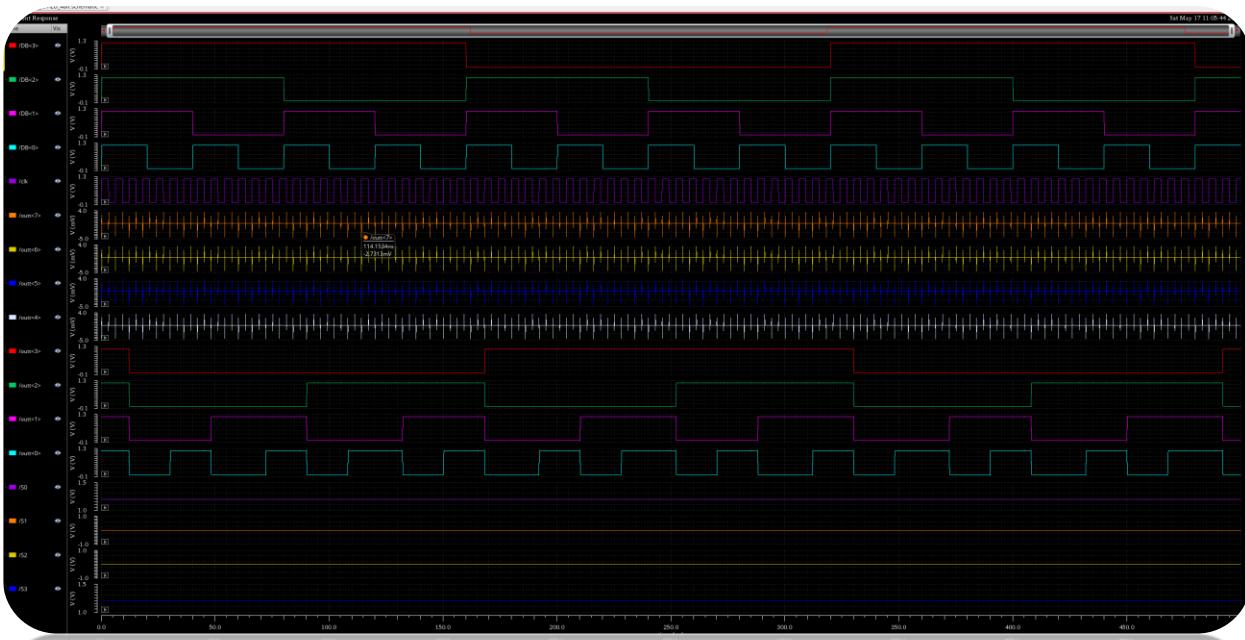


ARITHMETIC AND LOGICAL UNIT DESIGN

AND




OR

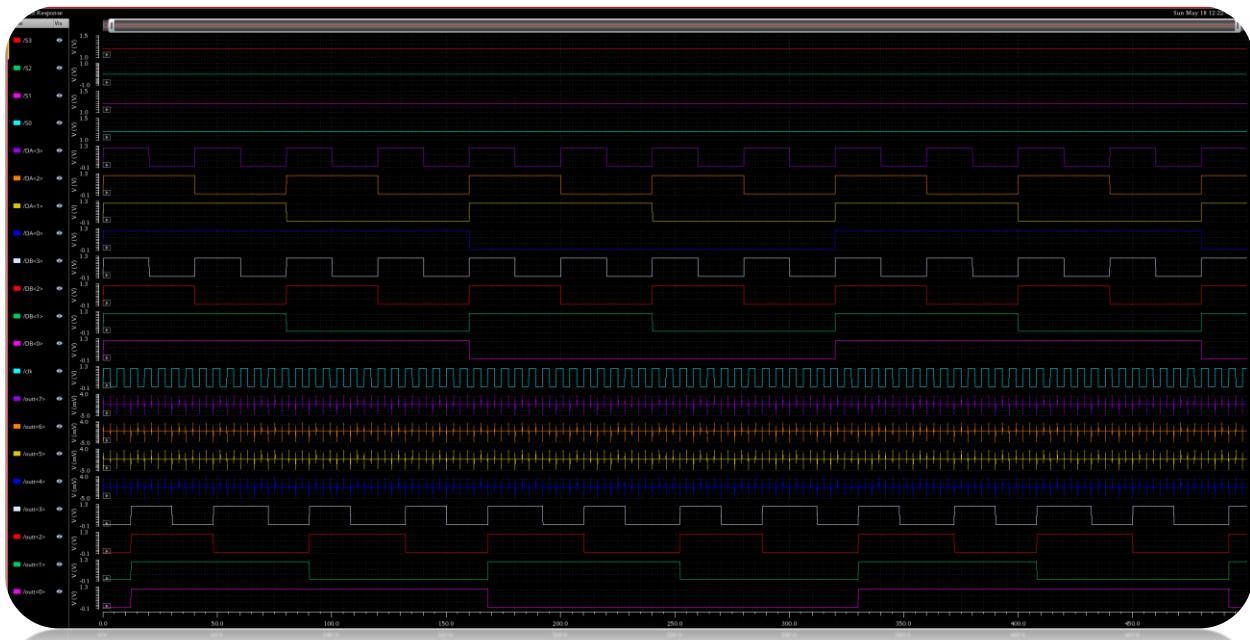


ARITHMETIC AND LOGICAL UNIT DESIGN

XOR

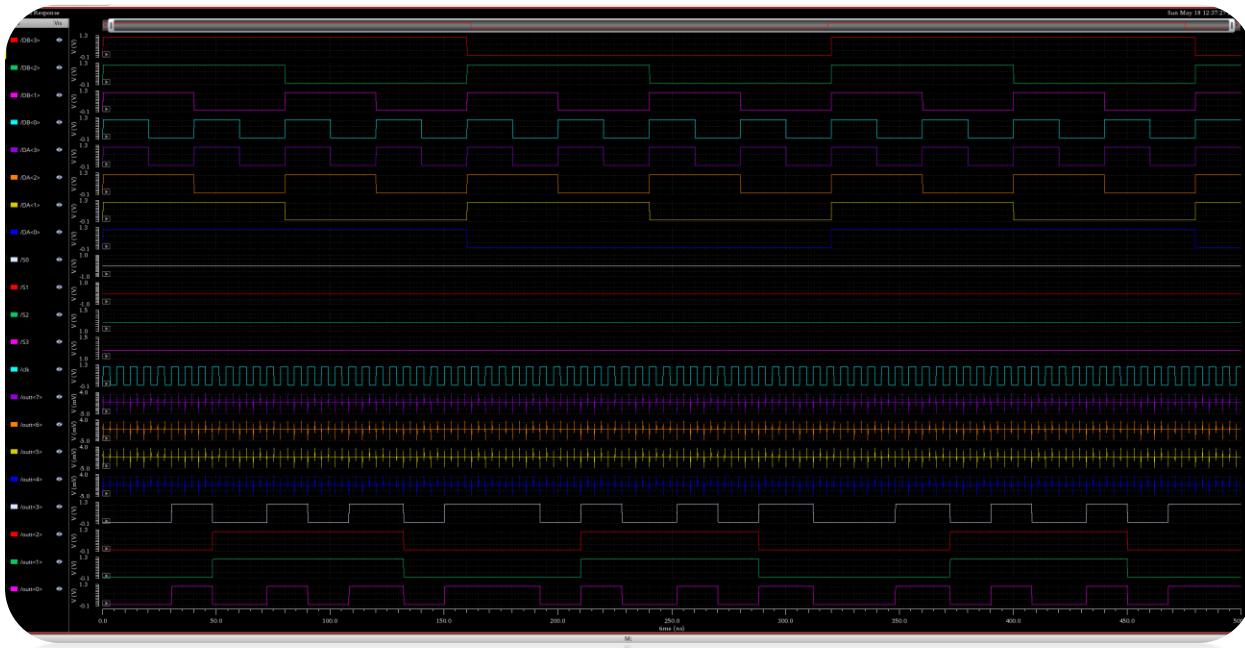


XNOR

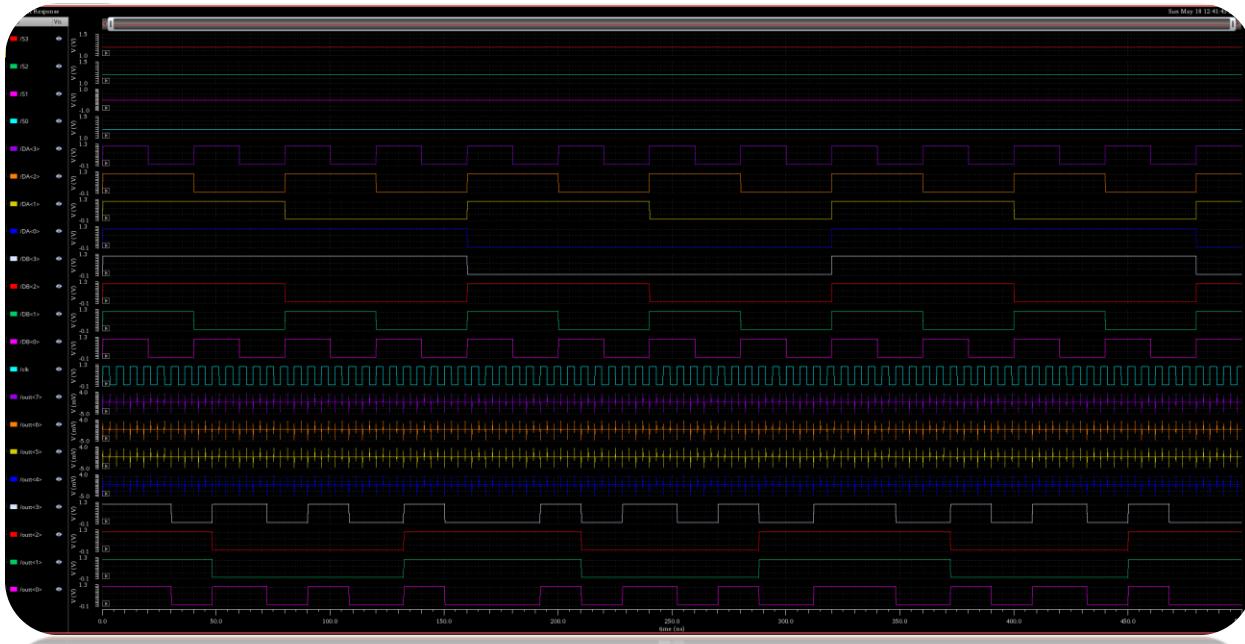


ARITHMETIC AND LOGICAL UNIT DESIGN

NAND

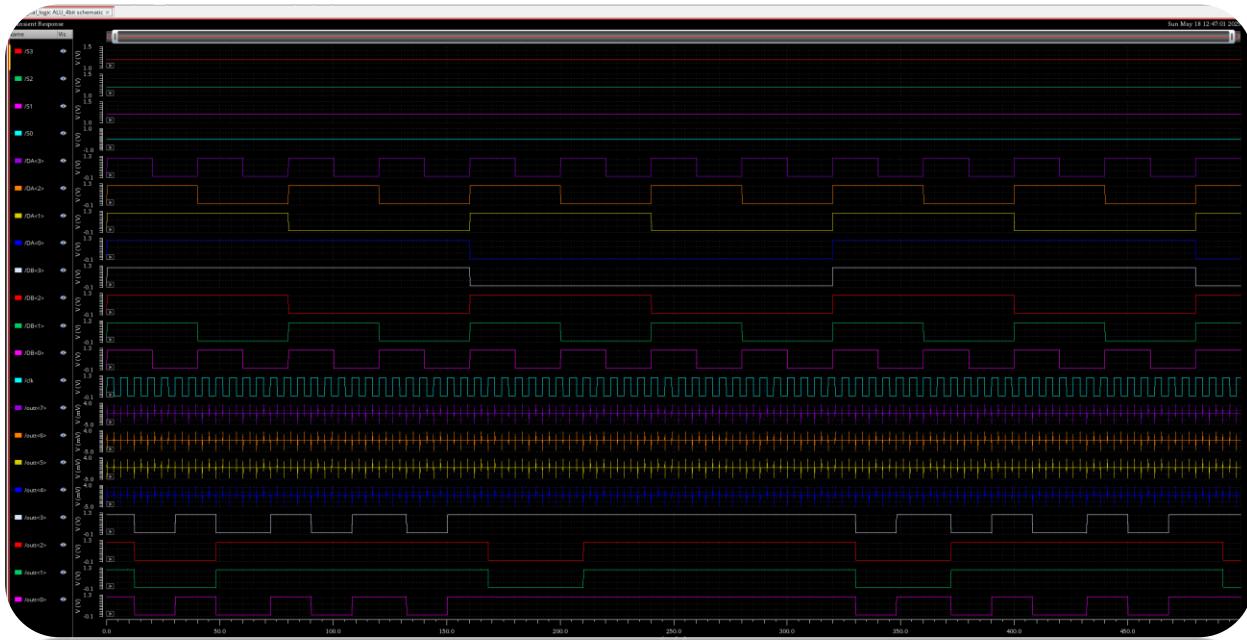


NOR

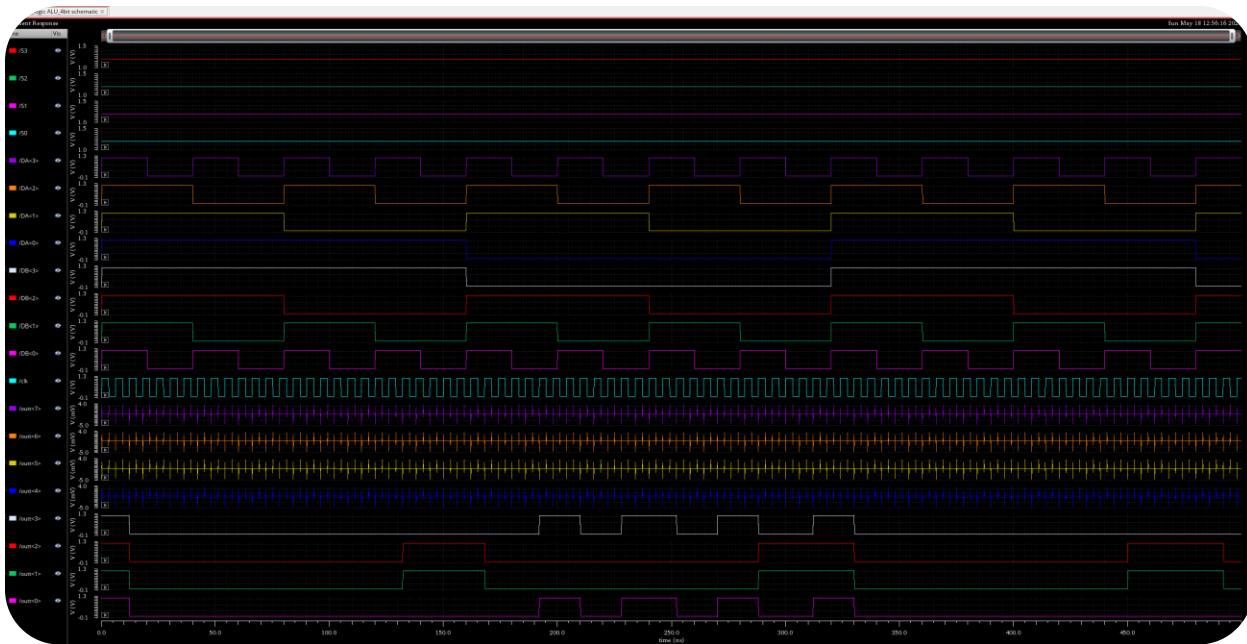


Regeneration stage

A regeneration stage block may be needed for different reasons in this circuit design, as the ALU has a relatively large input capacitance while the previous stage can not drive nor charge this large capacitance on its own so a regeneration stage with a fan-out of 4 had to be added as an intermediary phase between the ALU and previous stage. This regeneration block was made by adding a $4 \cdot \text{inv}$ in series with a $16 \cdot \text{inv}$ using our designed reference inverter mentioned previously. The delay of the regeneration stage on its own is negligible or almost nonexistent (note: I may add/remove to this part when re-assessing calculations)

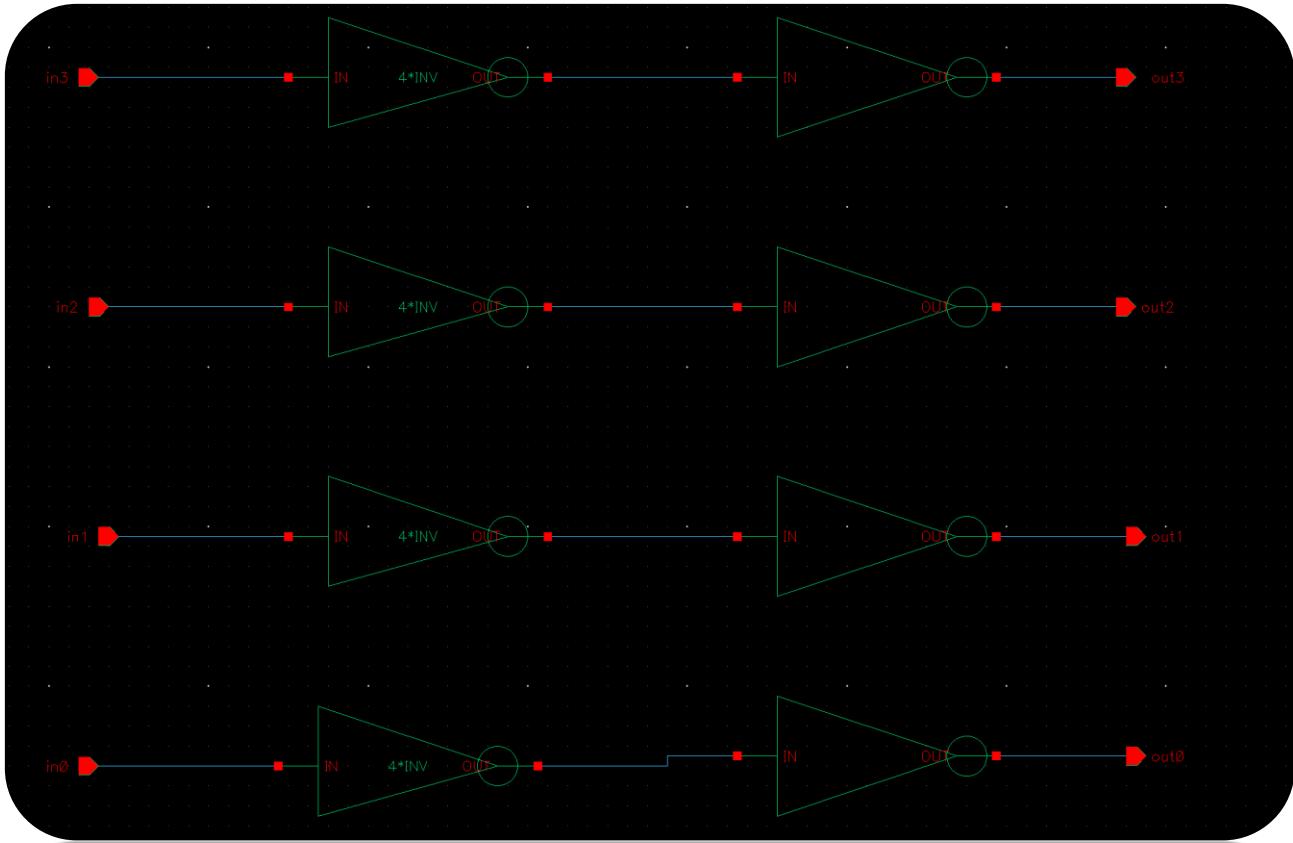


ARITHMETIC AND LOGICAL UNIT DESIGN

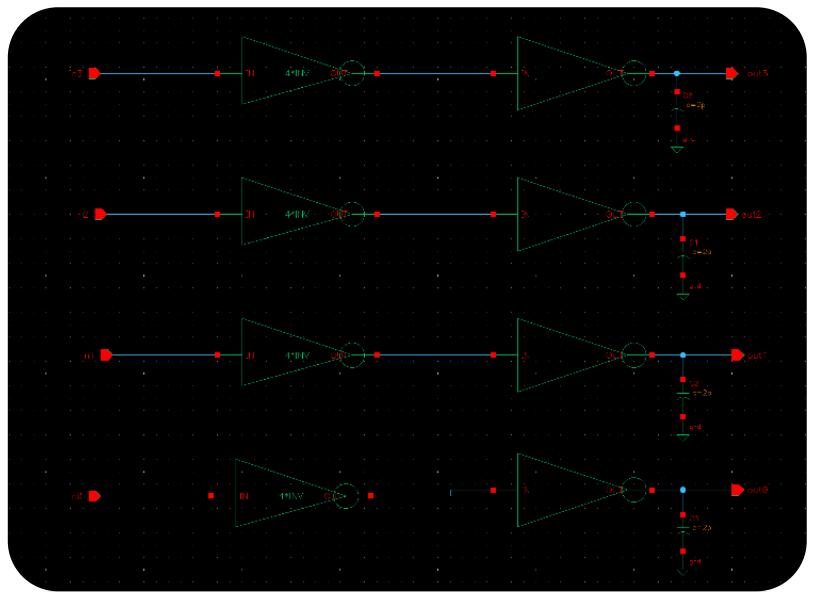After taking the output from the ALU, the wires are connected to two load blocks each having 4 inputs and 4 outputs to accommodate for the total 8 outputs of our ALU. This load block is very similar in design on circuit level to the regeneration block with just the addition of 2 picoFarad capacitors at the output terminals.




Regeneration test bench:

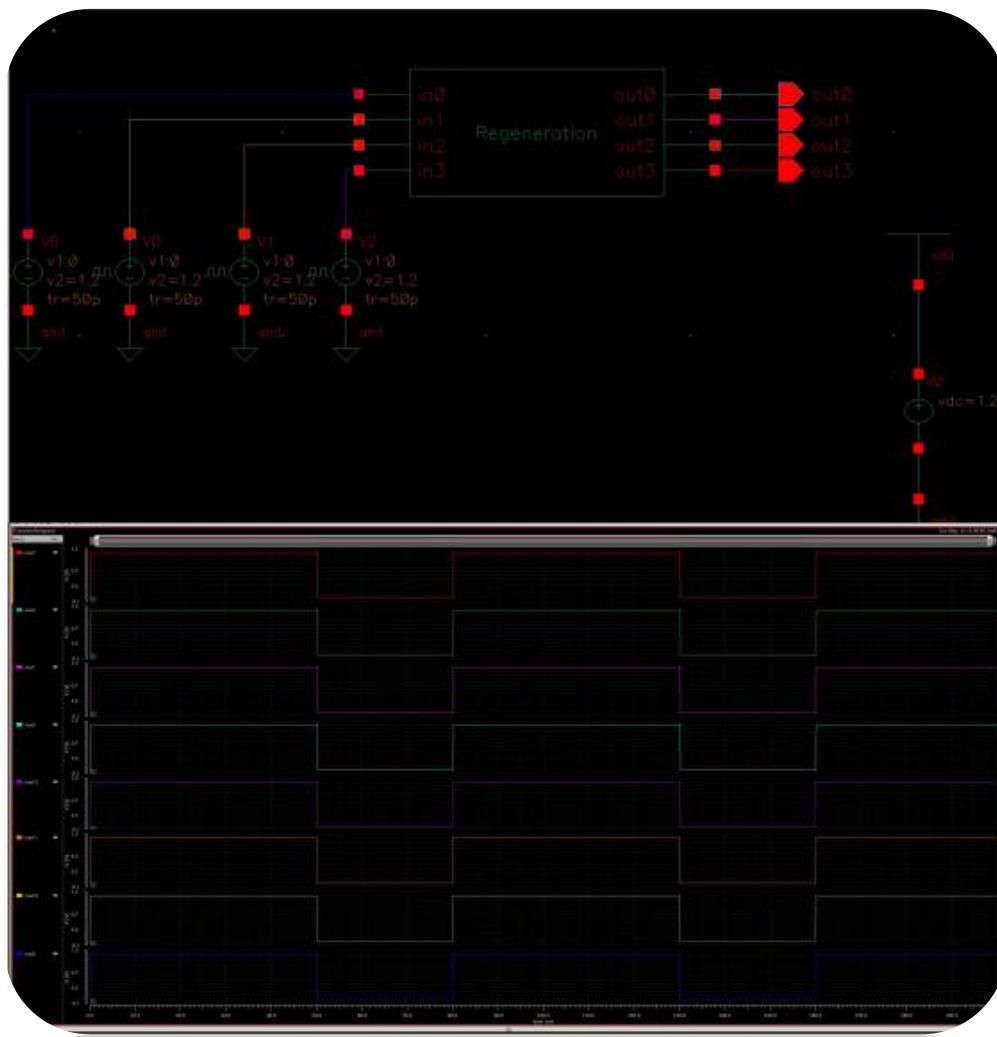


ARITHMETIC AND LOGICAL UNIT DESIGN

Load Test Bench:

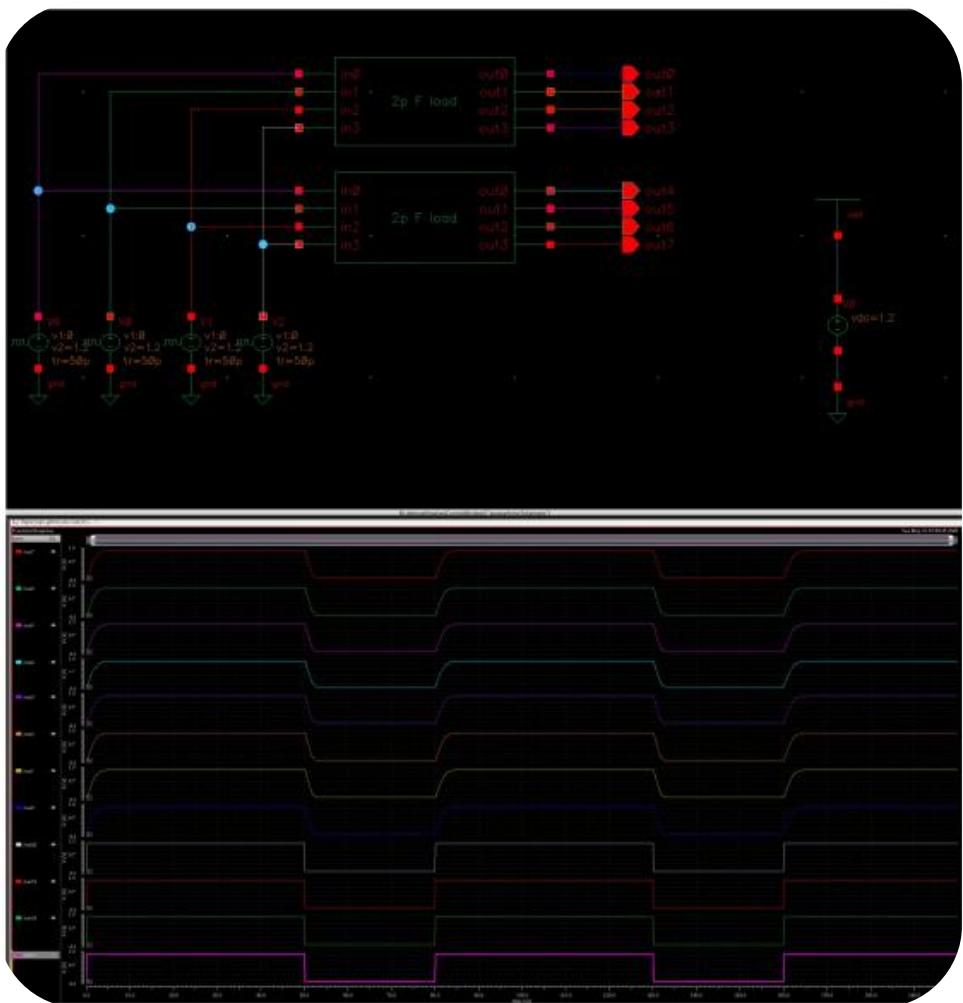

Another waveform with varying inputs:

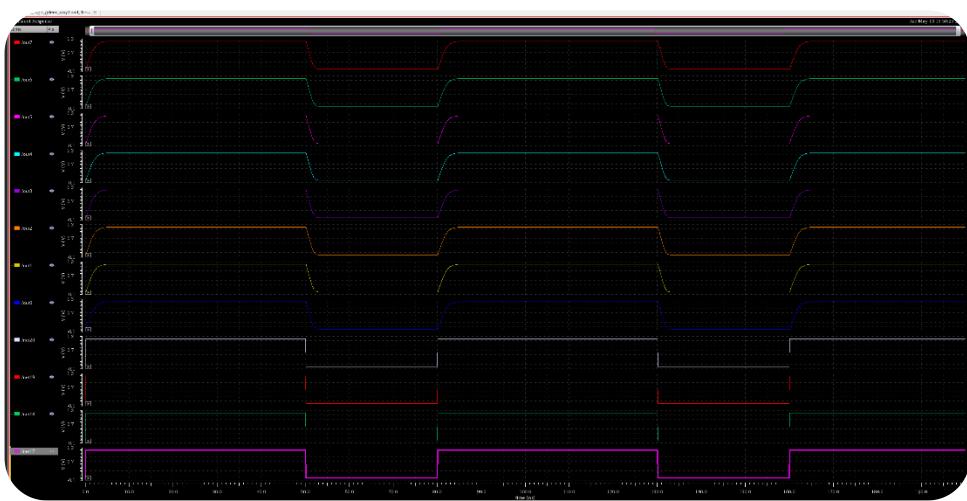In this test bench, each input was adjusted to have different pulse width to test the change of individual inputs separately and its effect on the output.



Calculations

TP logic output bit number 7

$T_{pcq} = 0.1$ nano seconds

$T_{plogic} = 1.85$ nano seconds

$T_{su} = 1$ nano seconds

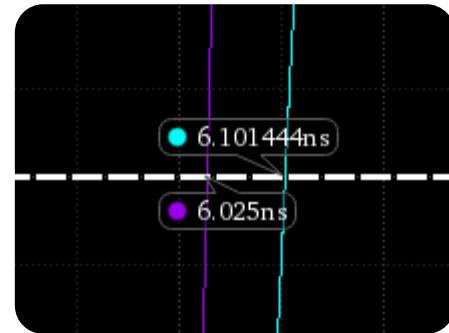


Figure 1: T_{pcq}

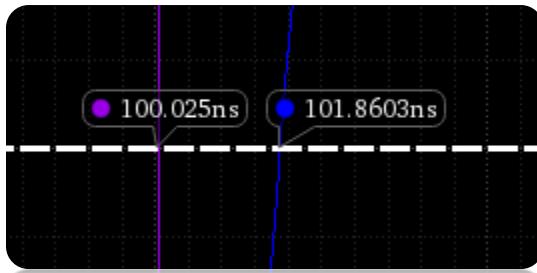


Figure 3: T_{plogic}

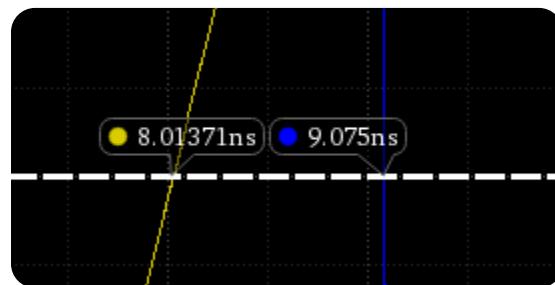


Figure 2: T_{su}

$$T_{clk} \geq t_{pcq} + t_{plog\ ic} + t_{su} = 2.95 \text{ nS}$$



$$F_{max} = 1/T_{CLK} \approx 340 \text{ MHz}$$

For maximum delay, selectors were forced to do the multiplication operation and inputs were configured as that the A input changes from -8 to +7 and input B stays at +7 the whole time as it was found this is the worst case in this ALU design.

T_{pcq} was found as the time between clock reaching 50% and the output waveform reaching the same 50% while the T_{su} was found as the minimum amount of time required for the input to be stable before the clock cycle.

ARITHMETIC AND LOGICAL UNIT DESIGN

Power:

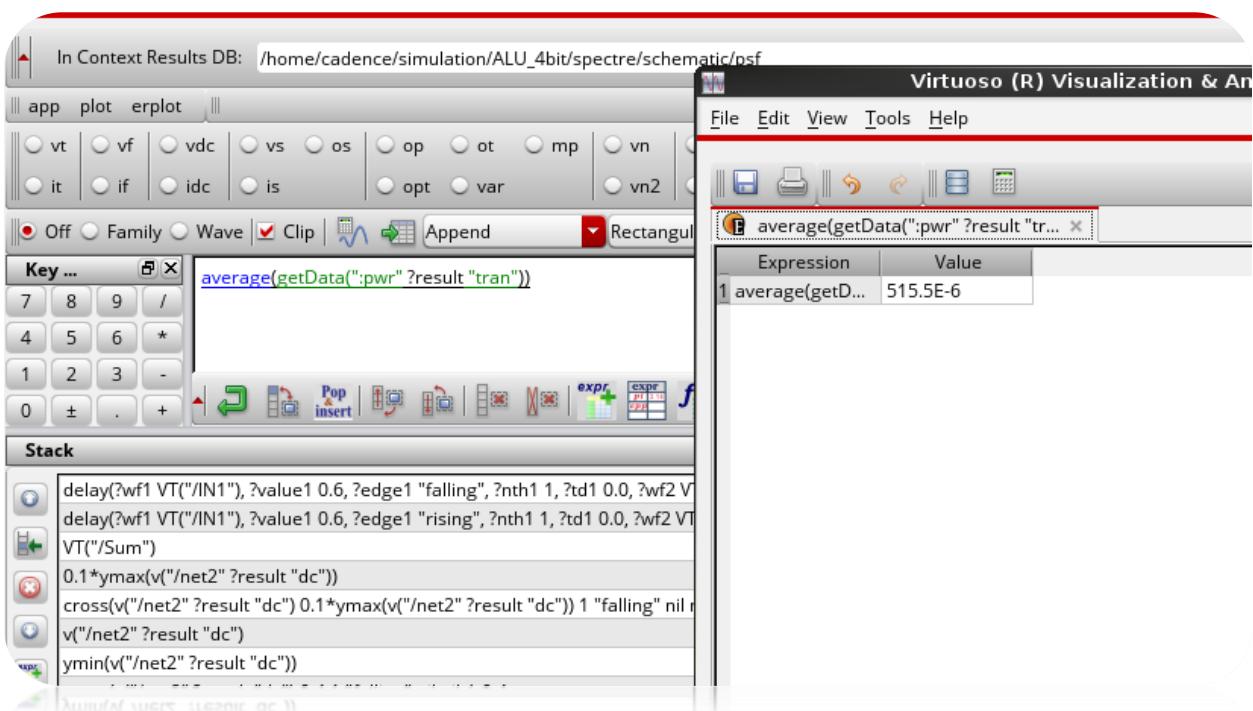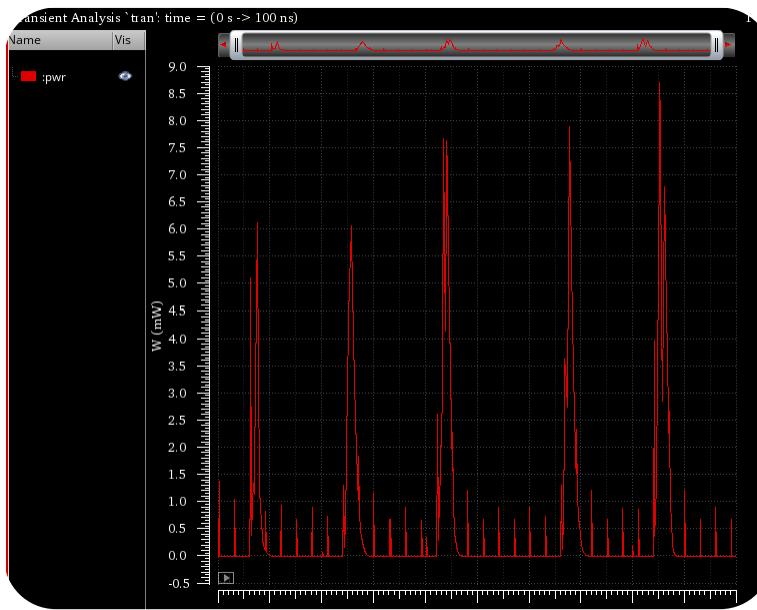

Avg power = 0.515 mW

Bonus: FPGA Implementation of the semicustom implementation

The objective of implementing the ALU design on an **FPGA** is to **validate the hardware functionality** of our Verilog-based ALU design through real-time operation and visualization. This **semi-custom implementation** demonstrates the transition from simulation to a working physical system and provides hands-on verification of design logic.

Target Platform and Tools

- **Target FPGA Board:** Intel **Cyclone IV EP4CE6E22**
 - **Design Tools Used:** Intel Quartus Prime
 - **Source Code:** Verilog HDL
- ▶ **Project files:** [Drive Link](#)



Implementation Details

- **Inputs:**
 - **4 LEDs** on the FPGA are used as **selector inputs** to choose the desired ALU operation (in binary)
 - **Selectors** changes through the counter on Verilog code.
 - Two 4-bit operands **A** and **B** are assigned using input pins through Quartus (set in the Pin Planner).
- **Outputs:**
 - The ALU's output is displayed on the **7-segment display** of the FPGA.
 - The **operation mode** is selected based on the **most significant bit (MSB)** of the 4-bit selector ($\text{SEL}[3]$):
 - $\text{SEL}[3] = 0$: **Arithmetic operations** (e.g., addition, subtraction)
 - $\text{SEL}[3] = 1$: **Logical operations** (e.g., AND, OR, XOR)
 - **For arithmetic operations:**
 - **3 digits** show the **magnitude** of the 4-bit result in **decimal**.
 - **1 digit** indicates the **sign** (positive or negative) of the result.
 - **For logical operations:**
 - The result is displayed as a **4-bit binary** value using the **7-segment display**, with one digit per bit (or grouped as needed).
- **Functionality:**
 - The ALU performs operations such as addition, subtraction, AND, OR, etc., based on the selector input.
 - Real-time results are visible on the 7-segment display, enabling easy debugging and validation.


Verification and Testing

- The implemented design was verified through **physical testing on the FPGA board**.
- A demonstration video showing the ALU in operation is available here:  **Demo Video:** [Drive Link](#)
- Additional screenshots and labeled images of selector configuration and output display will be included below.


$A=0100, B=1000$

$A=4, B=-8$

1. SEL=0000 (Increment A)

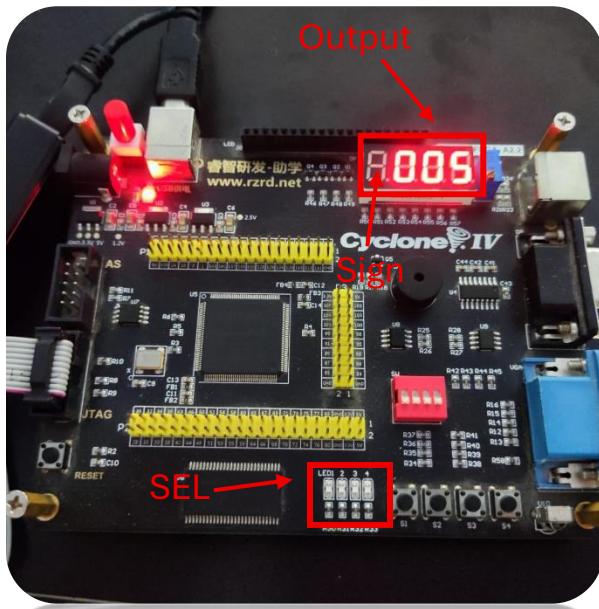


2. SEL=0001 (Increment B)

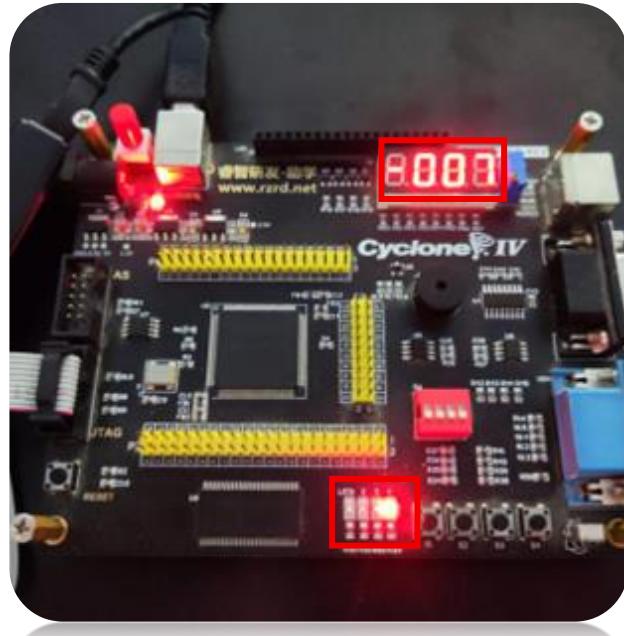


ARITHMETIC AND LOGICAL UNIT DESIGN


3. SEL=0010 (Transfer A)

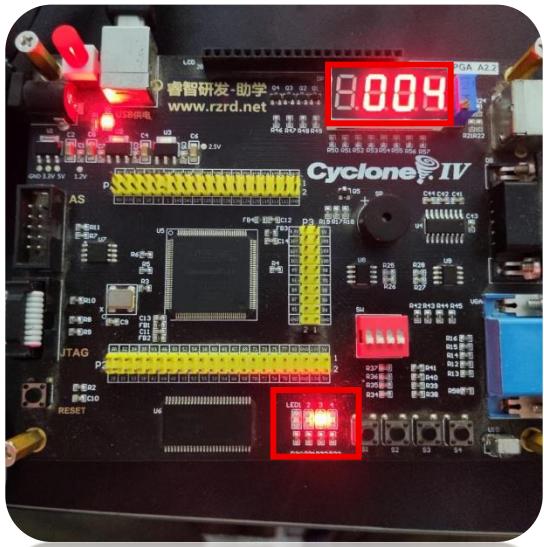


4. SEL=0011 (Transfer B)

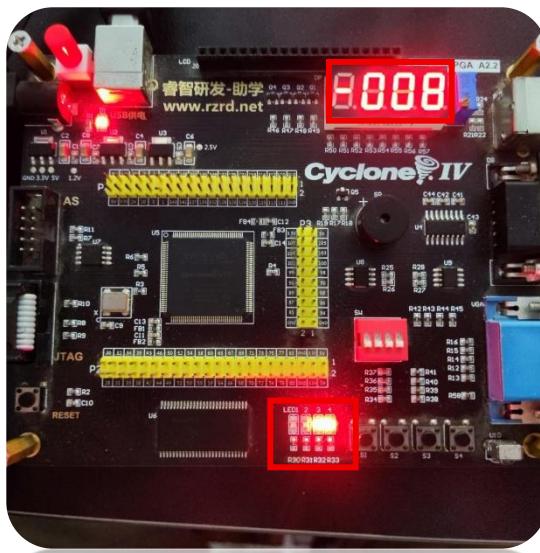

5. SEL =0100 (Decrement A)

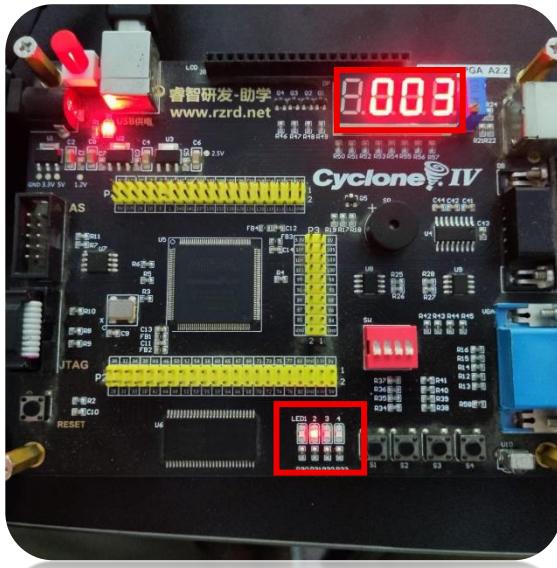


6. SEL= 0101 (Multiply A and B)


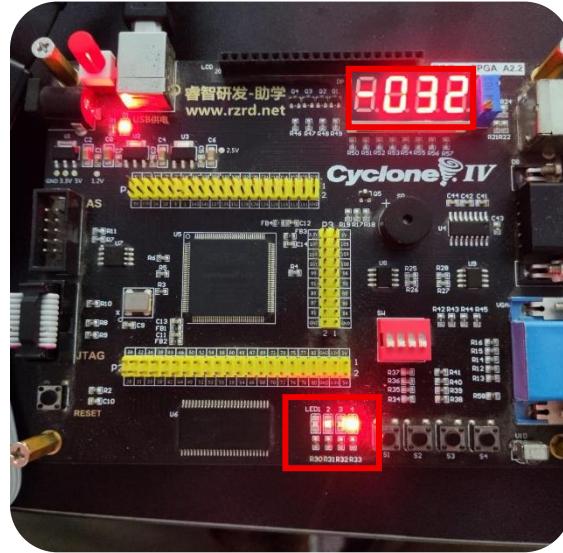


ARITHMETIC AND LOGICAL UNIT DESIGN


7. SEL=0110 (Add A and B)

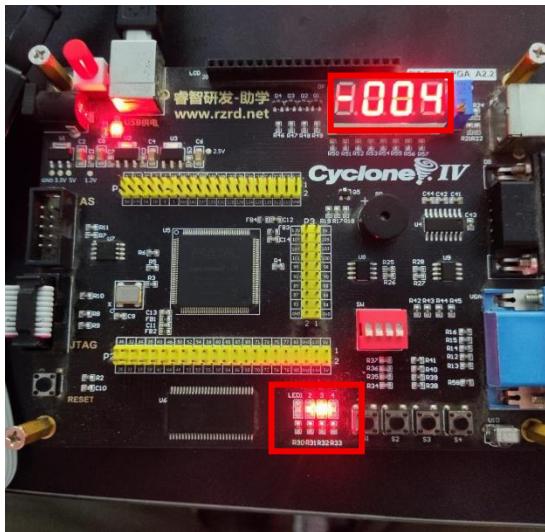

8. SEL=0111 (Subtract A and B)

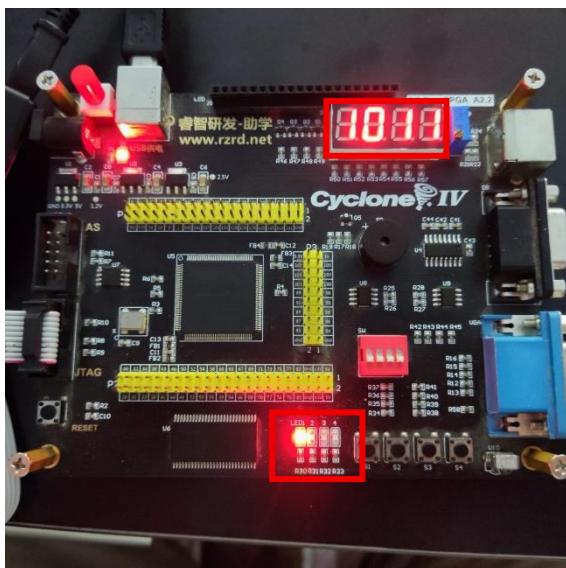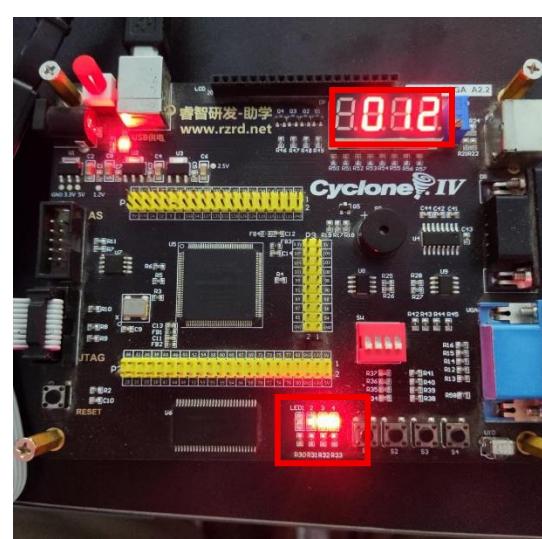


9. SEL=1000 (~A)

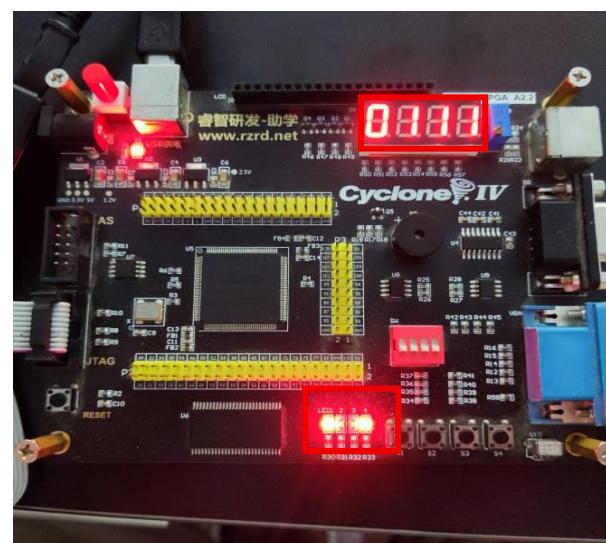


10. SEL=1001 (~B)


ARITHMETIC AND LOGICAL UNIT DESIGN

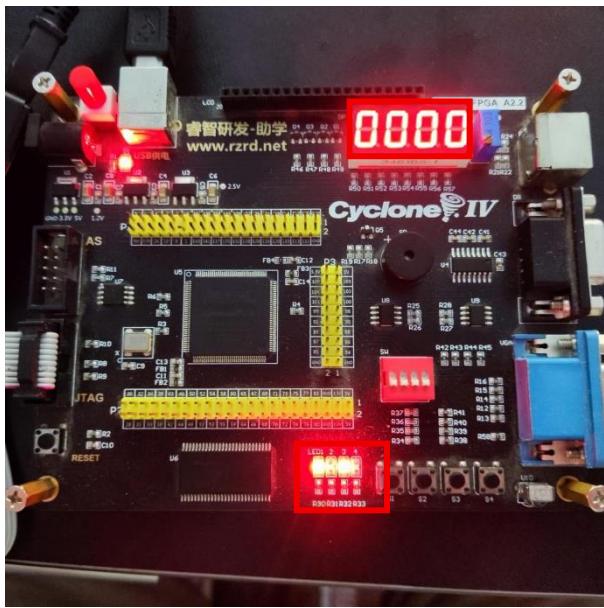


11. SEL=1010 (AND A & B)

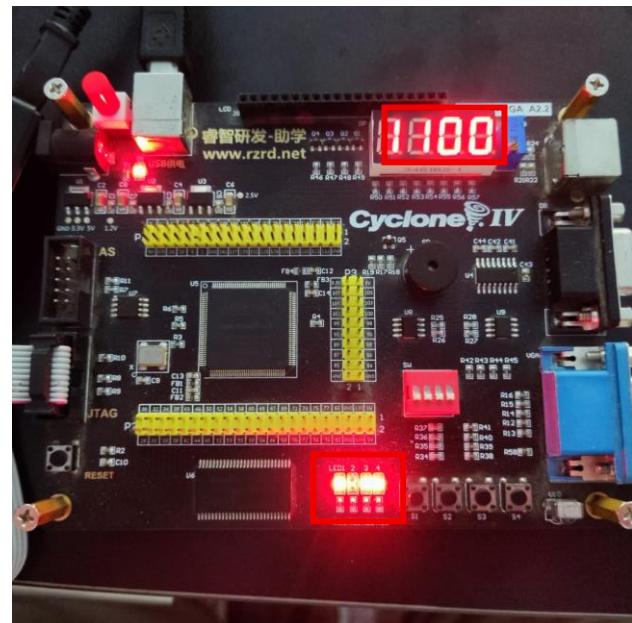


12. SEL=1011(OR A | B)

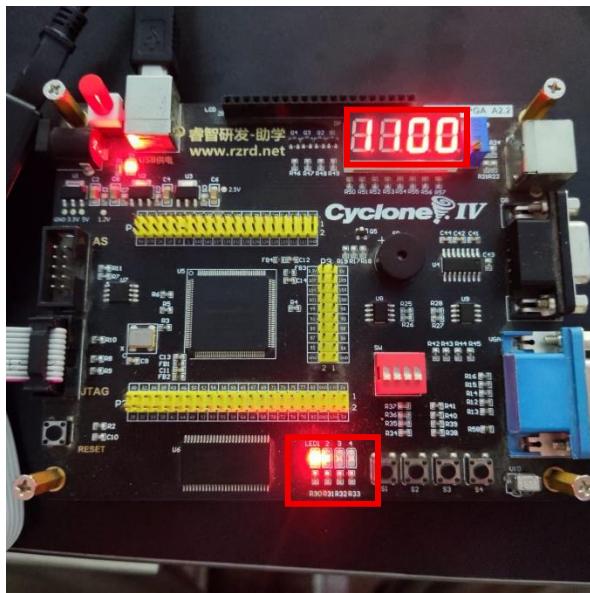


13. SEL=1100 (XOR A[^]B)

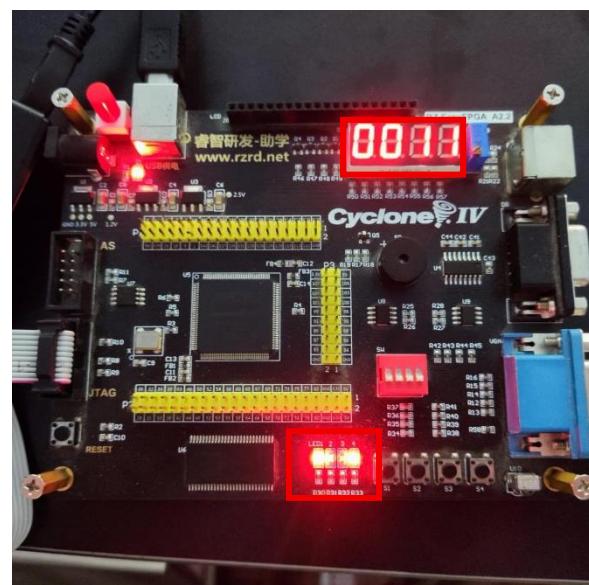

14. SEL=1101 (XNOR ~(A[^]B))

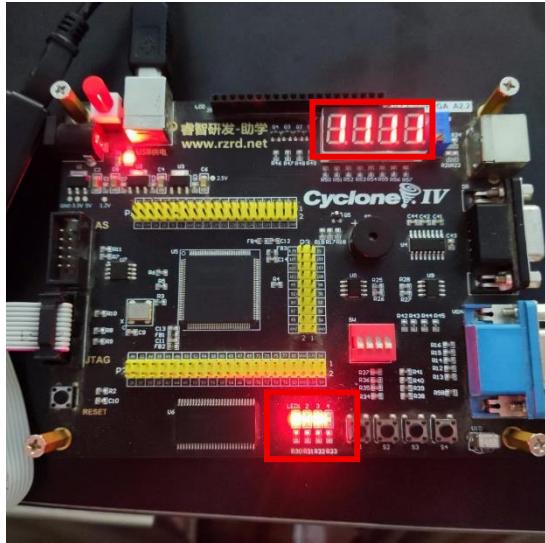

15. SEL=1110 (NAND ~(A&B))

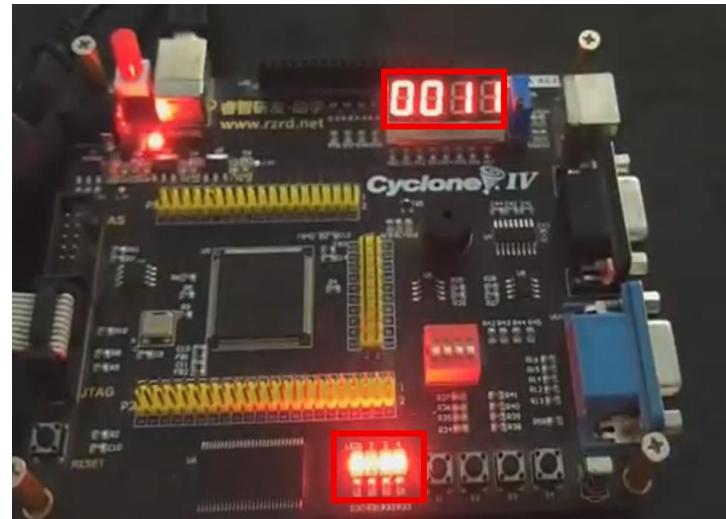

16. SEL=1111 (NOR ~(A|B))

Conclusion of FPGA Section

The FPGA implementation successfully demonstrated the **practical functionality** of the 4-bit ALU design. The use of real hardware allowed us to **verify the correctness of our Verilog code** beyond simulation. Although this design targets small bit-width operations, it reflects a complete digital system pipeline—from logic design to hardware realization. This semi-custom implementation confirms that the design is **functional, reliable, and adaptable** for future extensions on larger FPGAs.



GitHub Repository

You can access the complete Verilog source code, testbenches, and Quartus project files for this ALU design through the GitHub repository below:

[Repository Link](#)

This repository includes:

- Verilog modules for Arithmetic and Logical Unit
- Modeling using C++
- Testbenches for simulation
- FPGA configuration files for Quartus (Cyclone IV)
- Documentation and block diagrams